

## Analog to Digital (A/D) conversion Techniques

- Successive Approximation type
- Voltage to time conversion (Ramp type)
- Voltage to frequency conversion (Integrating type).
- Dual slope Integrating type ADC
- Flash type ADC

## Considerations of A/D and D/A techniques:

- A/D and D/A converters relate analog quantities to digital quantities and vice-versa through an appropriate code.
- Most commonly used code is binary code, in which a no is represented by

$$N = d_n 2^n + d_{n-1} 2^{n-1} + \dots + d_1 2^1 + d_0 2^0$$

↓ MSB
 ↓ LSB

where, co-efficients  $d_n, d_{n-1}, \dots, d_1, d_0$  can either (0 or 1).

Left most bit i.e.  $d_n$  is the 'MSB' & it has a weight (maximum value) which is twice as large as next most significant bit.

## Digital to Analog (D/A) conversion Techniques

- Binary weighted resistor type D/A converter.
- Ladder type:
  1. R-2R ladder type DAC
  2. Inverted R-2R ladder type DAC.

∴ Each binary bit has a weight which is twice the weight of next less significant bit.

• For a n-bit converter,

$$\text{Range of MSB} = \frac{1}{2} \times \text{Range of Converter}$$

$$\text{Range of LSB} = \frac{1}{2^n} \times \text{Range of Converter}$$


Full scale o/p voltage of a n-bit converter is:

$$E_o = E_R \times (d_n 2^{-1} + d_{n-1} 2^{-2} + \dots + d_1 2^{-(n-1)} + d_0 2^{-n})$$

↑ Reference voltage

$$\text{Resolution} = \text{Analog value of LSB} = \frac{\text{Full scale}}{2^n}$$

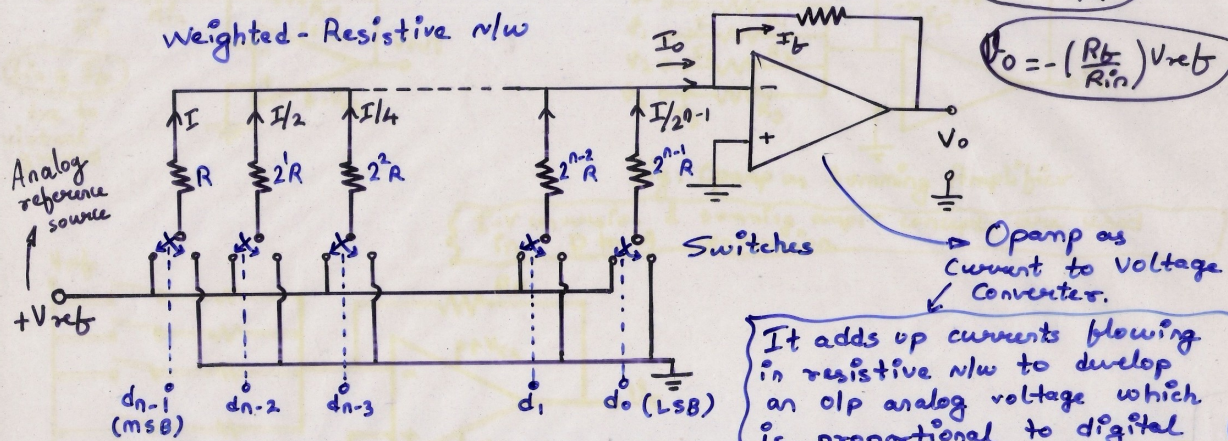
## Binary Weighted Resistor D/A Converter:



- The resistances in the n/w are weighted i.e. if resistance for MSB is R, then resistance of next bit is 2R & so on.
  - If MSB bit only is '1' by closing the switch, while all other bits as '0' then,  $V_o = V_{ref}/2$ .
  - If MSB bit ( $d_{n-1}$ ) and next bit i.e. ( $d_{n-2}$ ) are '1', then  $V_o = \left( \frac{1}{2} + \frac{1}{2^2} \right) V_{ref} = 0.75 V_{ref}$
  - If only LSB bit ( $d_0$ ) is '1', o/p v/tg  $V_o = V_{ref}/2^n$
- $$I_o = (I + I/2 + I/4 + \dots + I/2^{n-1}) = E_R/R \left[ 1 + \frac{1}{2} + \frac{1}{4} + \dots + \frac{1}{2^{n-1}} \right]$$
- This is true if all bits are '1'.


General expression:  $I_o = \frac{V_{ref}}{R} \left[ d_{n-1} + \frac{d_{n-2}}{2} + \frac{d_{n-3}}{4} + \dots + \frac{d_1}{2^{n-2}} + \frac{d_0}{2^{n-1}} \right]$
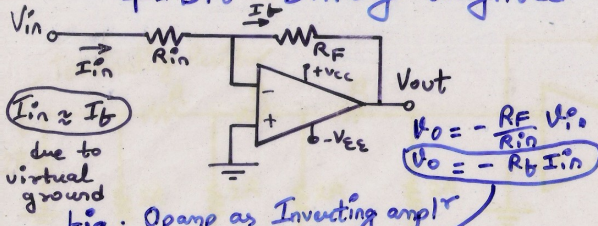
## 4-bit Binary weighted Resistor D to A Converter.



$I_{in} \approx I_f$   
due to virtual ground

fig: Opamp as Inverting amplifier (I-V converter)

 

$V_o = -I_f R_f$   
 $I_{in} \approx I_f$   
 $I_{in} = I_0 + I_1 + I_2 + I_3$   
 $= \frac{V_0}{R_0} + \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$

fig: Opamp as Summing Amplifier  
I-V conversion & summing amplifier concepts are used in D to A conversion.

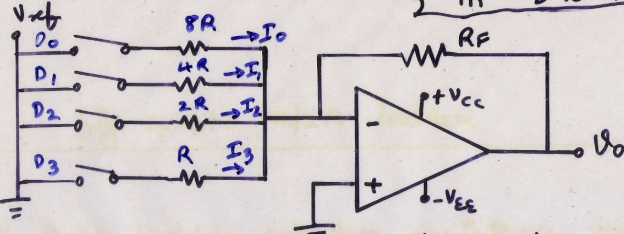


fig: 4-bit Binary weighted D/A converter

• Configuration consists of 4 2P's having weighted resistances  $8R, 4R, 2R$  &  $R$ , corresponding to 4-bit binary 2P's  $D_0, D_1, D_2, D_3$ .  
• Switches are provided for each 2P, so if a sw is open it means '0' & closed means '1'.  
• The '1' or high 2P to binary 2P is obtained from a reference source  $+V_{ref}$ .

From the diagram,  $I_3 = \frac{V_{ref}}{R}$ ;  $I_2 = \frac{V_{ref}}{2R}$ ;  $I_1 = \frac{V_{ref}}{4R}$ ;  $I_0 = \frac{V_{ref}}{8R}$ ;

$I_{in} = I_0 + I_1 + I_2 + I_3 = \frac{V_{ref}}{R} [\frac{1}{8} + \frac{1}{4} + \frac{1}{2} + 1] = \frac{V_{ref}}{R} [0.125 + 0.25 + 0.5 + 1] = \frac{V_{ref}}{R} [1.875]$

For a 4-bit D/A converter:  $I_{in} = V_{ref}/R [D_3 + 2^{-1}D_2 + 2^{-2}D_1 + 2^{-3}D_0]$

Drawback: (Not possible to produce mass weighted resistor DAC)

- Each resistance in n/w has different values i.e. ( $R, 2R, 4R, 8R$  & so on).
- Resistance used for MSB is required to handle a much larger current than LSB resistor.

## R-2R ladder type D/A Converter

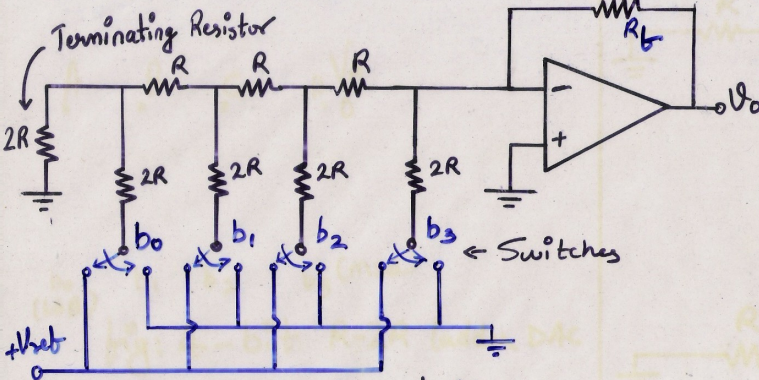


fig: 4-bit R/2R ladder

o/p of 4-bit R-2R ladder is

$$V_o = -V_{ref} \left[ \frac{R_f}{R} \right] \left[ \frac{b_3}{2} + \frac{b_2}{4} + \frac{b_1}{8} + \frac{b_0}{16} \right]$$

Resolution =  $V_{fs}/(2^n - 1)$

n = no of digital inputs

$V_{fs}$  → Value of analog o/p when digital 2P is 1111.

Digital inputs				Analog o/p
$b_3$	$b_2$	$b_1$	$b_0$	$V_o$
0	0	0	0	0
0	0	0	1	1/16
0	0	1	0	2/16
0	0	1	1	3/16
0	1	0	0	4/16
0	1	0	1	5/16
0	1	1	0	6/16
0	1	1	1	7/16
1	0	0	0	8/16
1	0	0	1	9/16
1	0	1	0	10/16
1	0	1	1	11/16
1	1	0	0	12/16
1	1	0	1	13/16
1	1	1	0	14/16
1	1	1	1	15/16

For n-bit binary 2P, o/p of R-2R ladder is,  
 $V_o = V_{ref} [2^{n-1}b_{n-1} + 2^{n-2}b_{n-2} + \dots + 2b_1 + b_0]$

• In R-2R ladder, only two resistance values are used i.e. ( $R$  and  $2R$ ). Hence it is suited for integrated circuit fabrication.

• Here, o/p voltage is a weighted sum of digital binary 2Ps.

• Since resistive ladder is a linear n/w, superposition principle can be used for finding total analog voltage for a particular digital 2P.

• Here, o/p voltage is linearly proportional to 2P binary bits and range can be adjusted by changing the reference voltage  $V_r$ .

### R-2R Ladder Explored


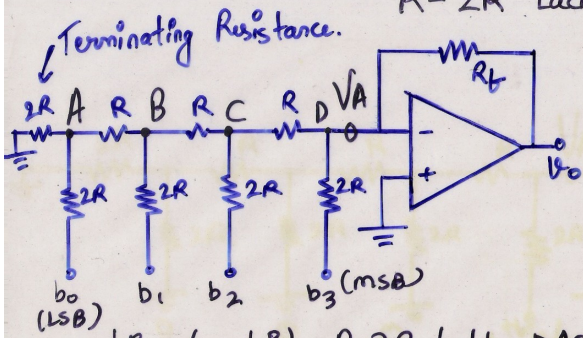


fig: 4-bit R-2R ladder DAC

 

From this observation, we conclude that resistance looking back from any node towards terminating resistance is  $2R$ .

 


fig: Resistance looking at point A w.r.t ground

 


fig: Resistance looking at point B w.r.t ground


 


fig: Resistance looking at point C w.r.t ground.


### R-2R Ladder Continue -----

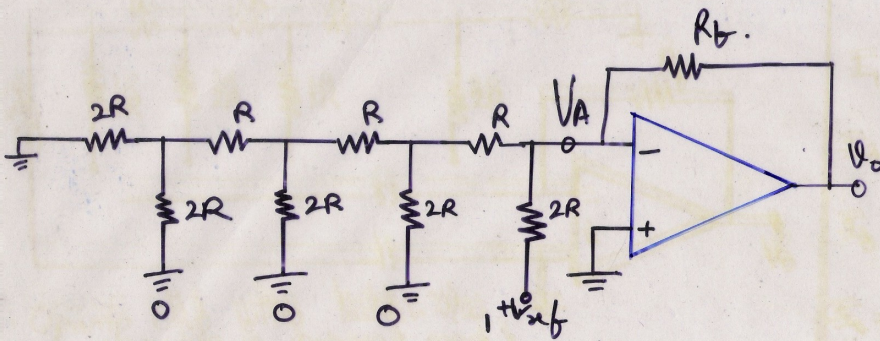

Applying Superposition we have

$$V_A = \left( \frac{2R}{2R+2R} \right) V_{ref}$$

$$V_A = \frac{V_{ref}}{2}$$

 


Note: for digital 1/0 0100 i.e next MSB bit high

$$V_A = \frac{V_{ref}}{4}$$

and so on

Hence a '1' in MSB position provides an O/P voltage of  $+V_{ref}/2$
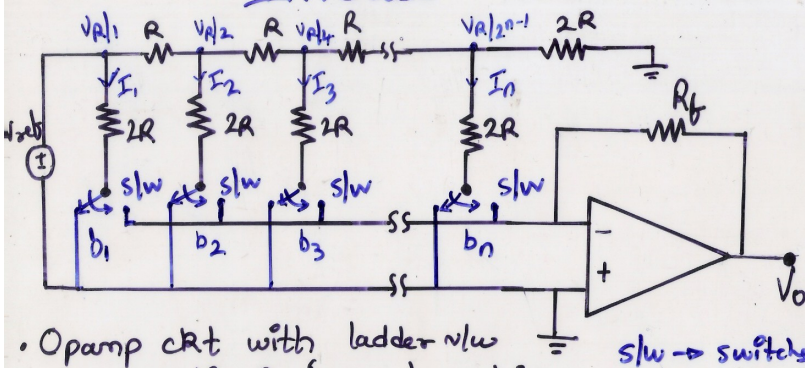
## Inverted R-2R Ladder type D/A converter



- Opamp circuit with ladder network is operating in 'current mode'
- In inverted, R-2R ladder type D/A converter, each bit of binary word connects the corresponding switch either to ground or to inverting input terminal of opamp which is at virtual ground.
- Since both the positions of switches are at ground potential, current flowing through resistances are constant and it is 'Independent' of switch position.
- All ladder node voltages remains constant with changing input bits.

From diagram,

$$I_1 = \frac{V_R}{2R}$$

$$I_2 = \frac{V_R/2}{2R} = \frac{V_R}{4R} = \frac{I_1}{2}$$

$$I_3 = \frac{V_R/4}{2R} = \frac{V_R}{8R} = \frac{I_1}{4}$$

$$I_4 = \frac{V_R/8}{2R} = \frac{V_R}{16R} = \frac{I_1}{8}$$

$$I_n = \frac{V_R/2^{n-1}}{2R} = \frac{I_1}{2^{n-1}}$$

$$V_o = -I_T R_f$$

$$V_o = -R_f [I_1 + I_2 + I_3 + \dots + I_n]$$

$$= -R_f \left[ b_1 \cdot \frac{V_R}{2R} + b_2 \cdot \frac{V_R}{4R} + \dots + b_n \frac{V_R}{2^n R} \right]$$

$$V_o = -V_R \left[ \frac{R_f}{R} \right] [b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n}]$$