
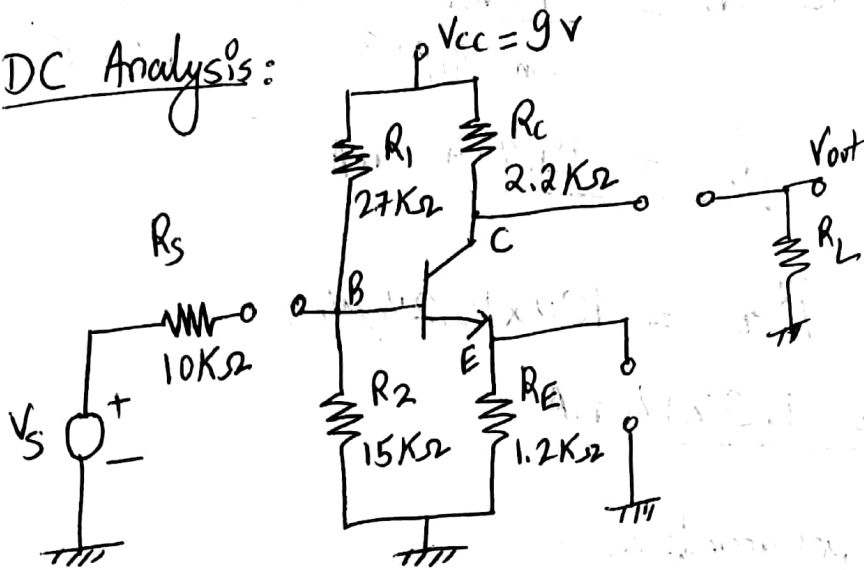


Q1. Given: $\beta = 100$, $V_A = 100V$

1. DC Analysis:

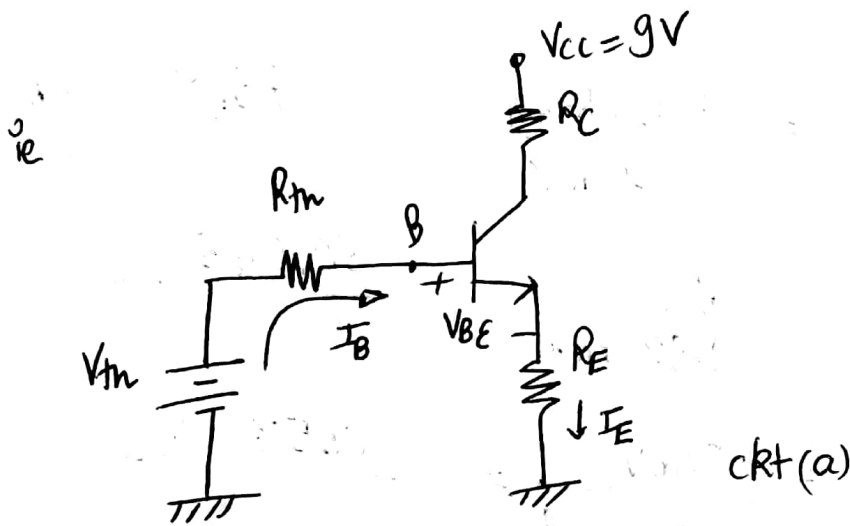

In dc analysis, we consider all capacitors to be open-ckt (Since $X_C \approx \infty$ high)



Assuming $V_{BE} = 0.7V$ & applying Thevenin's equivalent at the Base terminal.

$$\rightarrow V_{th} = \frac{R_2}{R_1 + R_2} \times V_{cc} = \frac{15K}{27K + 15K} \times 9 = 3.214V \quad (1m)$$

$$\rightarrow R_{th} = R_1 \parallel R_2 = 27K \parallel 15K = 9.643K\Omega \quad (1m)$$

KVL to B-E loop of ckt(a) gives,

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (1+\beta) I_B R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta) R_E} = \frac{3.214 - 0.7}{9.643K + 101 \times 1.2K}$$

$$I_B = 19.214 \mu A$$

$$I_C = \beta I_B = 100 \times 19.214 \mu A$$

$$I_{CQ} = 1.9214 mA$$

2m

2. Small-signal parameters: -

$$a) g_m = \frac{I_{CQ}}{V_T} = \frac{1.9214 mA}{26mV} = 73.9 \frac{mA}{V} \quad (1m)$$


$$b) r_o = \frac{V_A}{I_{CQ}} = \frac{100}{1.9214 mA} = 52.045 K\Omega \quad (1m)$$

$$c) r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{26mV}{19.214 \mu A} = 1.353 K\Omega \quad (1m)$$

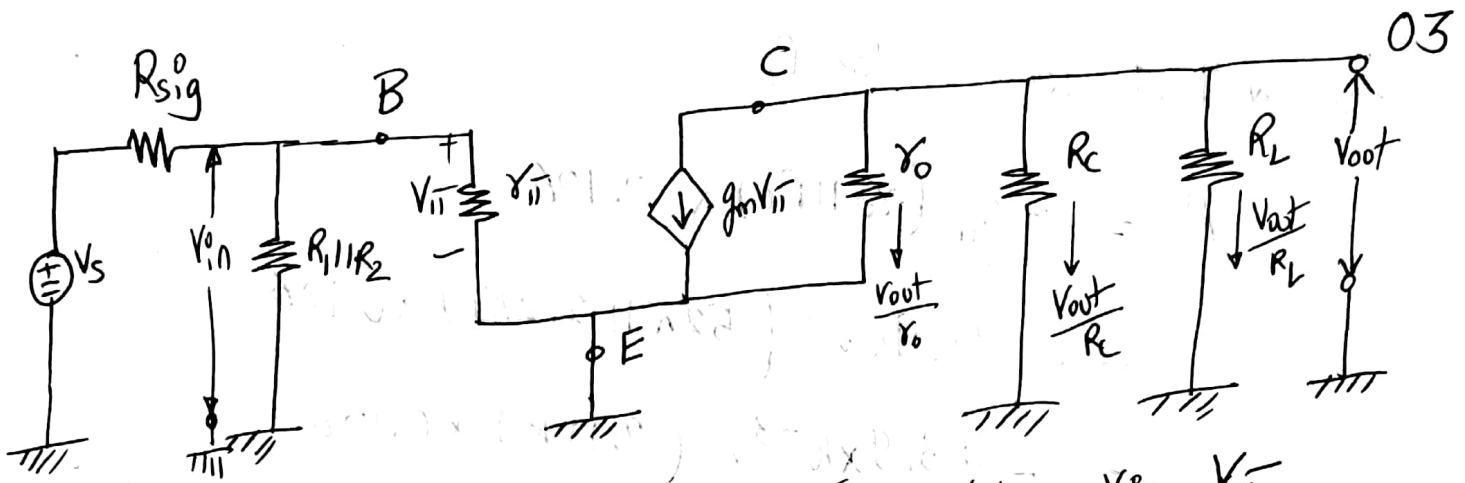3. Small-signal AC analysis: -

Next, we draw small-sig equivalent.

Consider, constant sources & capacitors to be short-ckt & replace BJT by its hybrid- π model.



From ckt, $V_{in} = V_{be}$

KCL at node C,

$$g_m V_{in} + \frac{V_{out}}{r_o} + \frac{V_{out}}{R_C} + \frac{V_{out}}{R_L} = 0$$

$$g_m V_{in} = -V_{out} \left(\frac{1}{r_o} + \frac{1}{R_C} + \frac{1}{R_L} \right)$$

$$\text{i.e. } \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_C \parallel R_L)$$

$$\text{Now, } A_v = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s} = -g_m (r_o \parallel R_C \parallel R_L) \times \frac{V_{in}}{V_s}$$

$$\frac{V_{in}}{V_s} = \frac{R_1 \parallel R_2 \parallel r_{in}}{R_1 \parallel R_2 \parallel r_{in} + R_{sig}} \quad \text{--- by V.D.R}$$

$$= \frac{27K \parallel 15K \parallel 1.353K}{(27K \parallel 15K \parallel 1.353K) + 10K} = 0.106$$

$$A_v = -g_m (r_o \parallel R_L \parallel R_C) \times 0.106$$

$$= -73.9 \times 10^{-3} (52K \parallel 2.2K \parallel 2K) \times 0.106$$

$$= -73.9 \times 10^{-3} (1.027K) \times 0.106$$

$$\boxed{A_v = -8.04} \quad \text{with load resistor } R_L \text{ --- } (3m)$$

A_v without load resistor R_L

04

$$\begin{aligned} A_v &= -g_m (\gamma_o \parallel R_c) \times 0.106 \\ &= -73.9 \times 10^{-3} (52K \parallel 2.2K\Omega) \times 0.106 \\ &= -73.9 \times 10^{-3} \times (2.11K) \times 0.106 \end{aligned}$$

$$\boxed{A_v = -16.528} \quad \text{without } R_L \quad \text{--- (2m)}$$

$$\begin{aligned} \rightarrow R_i^o &= R_1 \parallel R_2 \parallel \gamma_{ii} = \frac{27K\Omega \parallel 15K\Omega \parallel 1.353K\Omega}{\text{---}} \\ &= 9.643K \parallel 1.353K\Omega \end{aligned}$$

$$\boxed{R_i^o = 1.1865K\Omega} \quad \text{--- (2m)}$$

$$\begin{aligned} \rightarrow R_i^o \text{ including source resistance} &= R_i^o + R_{sig} = 1.1865K + 10K\Omega \\ &= \underline{11.865K\Omega} \end{aligned}$$

$$\begin{aligned} \rightarrow R_o &= \gamma_o \parallel R_c \parallel R_L \\ &= (52K \parallel 2.2K \parallel 2K) \\ &= (2.11K \parallel 2K) \end{aligned}$$

$$\boxed{R_o = 1.027K\Omega} \quad \text{--- (1m)}$$

OR

Q1. Given: $\beta = 100$, $V_{BE(on)} = 0.7V$, $V_A = \infty$, $V_{CC} = 5V$
 $I_{EQ} = 0.5mA$, $V_{CEQ} = 2.5V$, $A_v = -8$

Solⁿ: Consider voltage gain A_v to be $\left(\frac{V_o}{V_{in}}\right)$ which excludes source resistance R_s

Since, the given configuration is with R_E unbypassed, gain formula is


$$A_v = - \frac{R_c}{\frac{1}{g_m} + R_E}$$

$$\because \frac{1}{g_m} \ll R_E$$

$$A_v \approx - \frac{R_c}{R_E}$$

$$-8 = - \frac{R_c}{R_E}$$
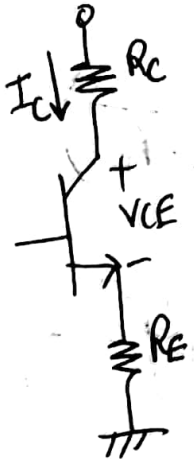
$$\text{ie } \boxed{R_c = 8 R_E} \quad \text{--- (i)}$$



KVL to CE loop, gives

$$I_c = I_e$$

$$V_{CC} - I_c R_c - V_{CE} - I_c R_E = 0$$

$$\text{ie } I_c (R_c + R_E) = V_{CC} - V_{CE}$$

$$R_c + R_E = \frac{(5 - 2.5)}{0.5mA} = 5000$$

$$\text{ie } 8R_E + R_E = 5000 \quad (\text{From i})$$

$$\underline{R_E \approx 555.55 \Omega}$$

Selecting L.S.V of R_E ,
(Low side value)

06

Select $R_E = 510 \Omega$ (std), $\frac{1}{4}W$ ----- (5m)

From (i), $R_C = 8R_E = 8 \times 510 \approx 4.08 K\Omega$

Select $R_C = 4.2 K\Omega$ (std), $\frac{1}{4}W$ ----- (2m)
H.S.V

→ Calculation of R_1 & R_2 :-

For bias-stable circuit

$$R_{th} \approx 0.1(1+\beta)R_E$$

$$\approx 0.1 \times 101 \times 510$$

$R_{th} \approx 5.15 K\Omega$ ----- (1m)

OR let Stability factor $S=10$

$$S = \frac{1+\beta}{1+\beta \left(\frac{R_E}{R_{th}+R_E} \right)}$$

$$10 = \frac{1+100}{1+100 \left(\frac{510}{R_{th}+510} \right)}$$

ie $R_{th} \approx 5.094 K\Omega$

Both techniques for finding results.

R_{th} yields almost similar

Consider $R_{th} \approx 5.15 K\Omega$ & moving ahead with calculations.

07

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.5mA}{100} = 5\mu A$$


KVL to B-E loop gives,

$$V_{th} - I_B R_{th} - V_{BE} - (1+\beta)I_B R_E = 0$$

$$\begin{aligned} \text{ie } V_{th} &= V_{BE} + I_B (R_{th} + (1+\beta)R_E) \\ &= 0.7 + 5\mu A (5.15K + 101 \times 510) \end{aligned}$$

$$\boxed{V_{th} = 0.9833}$$

----- (2m)

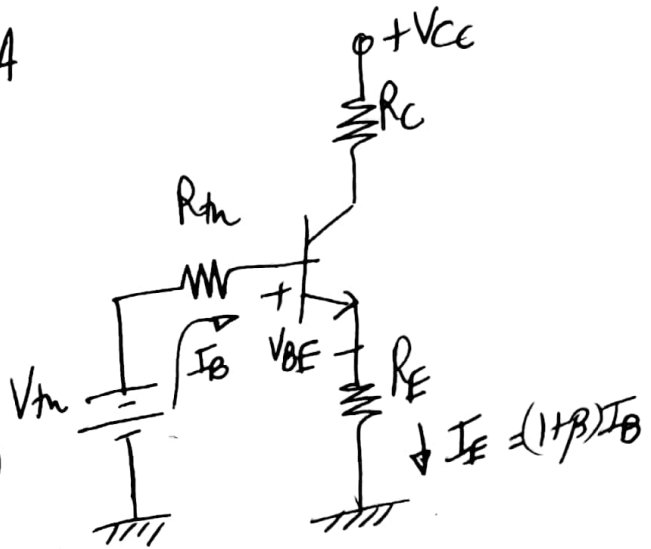

Also, $V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{R_{th}}{R_1} V_{CC}$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

ie $\frac{V_{th}}{V_{CC}} = \frac{R_{th}}{R_1} \Rightarrow R_1 = \frac{5.15K \times 5}{0.9833} = 26.187K\Omega$


Select $\boxed{R_1 = 27 K\Omega, \frac{1}{4}W}$ H.S.V ----- (3m)

Now; $\frac{V_{th}}{V_{CC}} = \frac{R_2}{R_1 + R_2}$ ie $\frac{0.9833}{5} = \frac{R_2}{27K + R_2}$
 ie $\underline{R_2 = 6.6 K\Omega}$

Select $\boxed{R_2 = 6.2 K\Omega (std), \frac{1}{4}W}$ L.S.V ----- (2m)

2a) To find g_m :

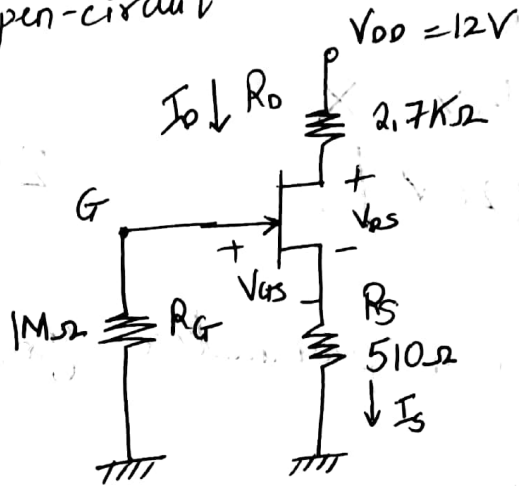For DC Analysis, $f=0$, $X_c = \frac{1}{2\pi f c} = \infty$ i.e. Capacitors behaves as open-circuit



$$I_{DSS} = 10\text{mA}$$

$$V_p = -6\text{V}$$

Solⁿ:- From the above ckt, we have

$$V_G = 0$$

$$V_S = I_S R_S = I_D R_S \quad \text{--- (} I_S = I_D \text{)}$$

$$\rightarrow V_{GS} = V_G - V_S = 0 - I_D R_S$$

$$V_{GS} = -I_D (510) \quad \text{--- (1)}$$

Assuming JFET is working in saturation region,

$$\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = 10\text{mA} \left(1 + \frac{V_{GS}}{6}\right)^2 \quad \text{--- (2)}$$

Put (2) in (1), we have

$$\text{i.e. } V_{GS} = -5.1 \left(1 + \frac{V_{GS}}{6} + \frac{V_{GS}^2}{36}\right)$$

$$V_{GS} = -5.1 - 1.7V_{GS} - 0.1416 V_{GS}^2$$

$$\text{ie } 0.1416 V_{GS}^2 + 2.7V_{GS} + 5.1 = 0$$

$$V_{GS} = -2.126 \text{ V } \checkmark \quad \left(\begin{array}{l} \text{we select this value,} \\ \text{since } V_{GS} < V_P \end{array} \right)$$

OR

$$V_{GS} = -16.94 \text{ V } \times$$

$$\therefore \boxed{V_{GS} = -2.126 \text{ V}}$$

(3m)

→ Small-signal hybrid- π parameter (g_m):-

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$= \frac{2 \times 10 \text{ mA}}{6} \left(1 - \frac{(-2.126)}{(-6)} \right)$$

$$= 3.33 \text{ mA} (0.6456)$$

$$\boxed{g_m = 2.15 \frac{\text{mA}}{\text{V}}}$$


(1m)

2b) JFET is a voltage-controlled device.

Justification

(3m)

Circuit B

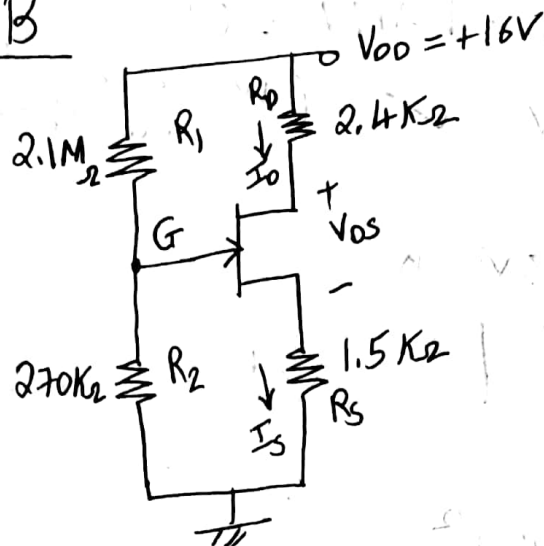

$I_{DSS} = 8\text{mA}$
 $V_p = -4\text{V}$

i) Analytical method :-

Above circuit is voltage-divider bias

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{270\text{K}}{2.1\text{M} + 270\text{K}} \times 16$$

→ $V_G = 1.823\text{V}$; $V_S = I_D R_S$

→ $V_{GS} = V_G - I_D R_S = 1.823 - I_D (1.5\text{K})$ — (1)

Assuming transistor is working in saturation region,

→ $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = 8\text{mA} \left(1 + \frac{V_{GS}}{4}\right)^2$ — (2)

Put (2) in (1), we get

ie $V_{GS} = 1.823 - 12 \left(1 + \frac{V_{GS}}{4} + \frac{V_{GS}^2}{16}\right)$

$V_{GS} = 1.823 - 12 - 6V_{GS} - 0.75V_{GS}^2$

$$\rightarrow 0.75 V_{GS}^2 + 7V_{GS} + 10.177 = 0$$

$$V_{GS} = -1.8V \quad \checkmark \quad \left(\begin{array}{l} \text{we select this value,} \\ \text{since } V_{GS} < V_P \end{array} \right)$$

04.

$$\text{OR}$$

$$V_{GS} = -7.53V \quad \times$$

$$\therefore \boxed{V_{GS} = -1.8V} \quad \text{---} \quad (3M)$$

$$\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= 8mA \left(1 - \frac{(-1.8)}{(-4)} \right)^2$$

$$= 8mA \times 0.3025$$

$$\boxed{I_D = 2.42mA} \quad \text{---} \quad (2M)$$

K.V.L applied to Drain to source loop, gives

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0 \quad (I_D = I_S)$$

$$\text{ie } V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$= 16 - 2.42mA (2.4k\Omega + 1.5k\Omega)$$

$$\boxed{V_{DS} = 6.562V} \quad \text{---} \quad (2M)$$

Circuit B

05

Graphical method:-

$$\rightarrow V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{270K\Omega}{270K\Omega + 2.1M\Omega} \times 16 = \underline{1.82V}$$

$$\rightarrow V_S = I_D R_S$$

$$\rightarrow \boxed{V_{GS} = 1.82 - I_D (1500)} \quad \text{--- (1) } \quad \text{(1m)}$$

↳ load line equation

In above equation,

$$\text{i) Put } I_D = 0 \rightarrow \underline{V_{GS} = 1.82V}$$

$$\text{1st point} \equiv (1.82V, 0) \quad \text{(1/2m)}$$

$$\text{ii) Put } V_{GS} = 0 \rightarrow I_D = \frac{1.82}{1500} = \underline{1.213mA}$$

$$\text{2nd point} \equiv (0, 1.213mA) \quad \text{(1/2m)}$$

Joining above two points gives us load line
Coordinates

To plot transfer curve, we require few readings of I_D & V_{GS} .

$\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$ --- (1)

$\rightarrow V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$ --- (2)

i) If $V_{GS} = 0.5V_P \rightarrow I_D = \frac{1}{4} I_{DSS}$ --- From (1)

ii) If $I_D = \frac{I_{DSS}}{2} \rightarrow V_{GS} = 0.3V_P$ --- From (2)

V_{GS}	I_D
0	I_{DSS}
$0.3V_P$	$I_{DSS}/2$
$0.5V_P$	$I_{DSS}/4$
V_P	0

ie

V_{GS}	I_D
0	8mA
-1.2V	4mA
-2V	2mA
-4V	0

(1M)

Using the values of V_{GS} & I_D to plot transfer curve.

\rightarrow The interaction of load line curve and transfer curve gives us the Q-point.

ie $V_{GSQ} = -1.8V$ & $I_{DQ} = 2.3mA$

$V_{DS} = V_{DD} - I_D (R_D + R_S) = 16 - 2.3mA (2.4K + 1.5K)$
 $V_{DS} = 7.03V$ (1M)

