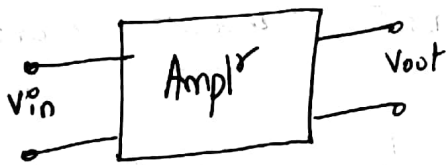


# BJT amplifiers

01  
18/10/19

Module 4.1:- Understanding concepts of amplification with reference to input/output characteristics

Amplifier requirements:-




- 1) Gain should be high  
eg voltage gain of a voltage amplifier  $\rightarrow$  high
- 2) I/P impedance
- 3) O/P impedance
- 4) Linearity (O/P should be linear w.r.t I/P)

• BJT as a device should amplify  $\rightarrow$  small time-varying signals.

$\swarrow$  This condition must be satisfied for BJT amplifiers to be Linear


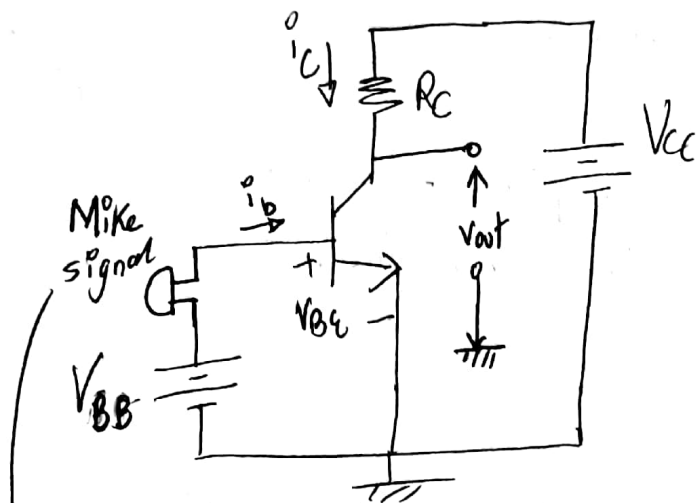
• Next, we need to superimpose small AC sig with DC? why DC biasing is required  $\rightarrow$  so that BJT wakes up & works in proper mode i.e. active region  $\rightarrow$  so that it is used as amplifier



It acts a small-time varying I/P  $v_{in}$  ( $v_{mike} \approx v_{msinot}$ )


→ BJT act as : voltage-dependent current source

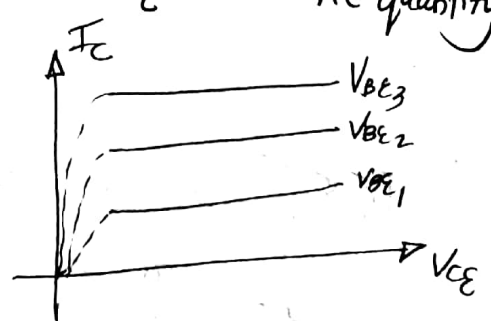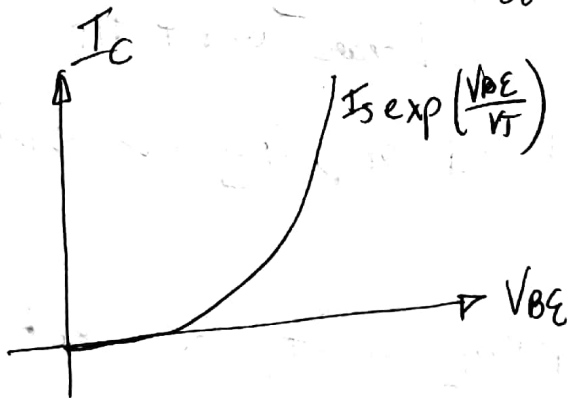→ "converts" a voltage to a current  
 $(V_{BE})$  ——— DC quantity  
 or  $V_{be}$   $i_C$  ——— AC quantity



Biasing: Provide proper voltage ( $V_{BE}$ ) & current ( $I_C$ ) so that the transistor can amplify (in the absence of signals)

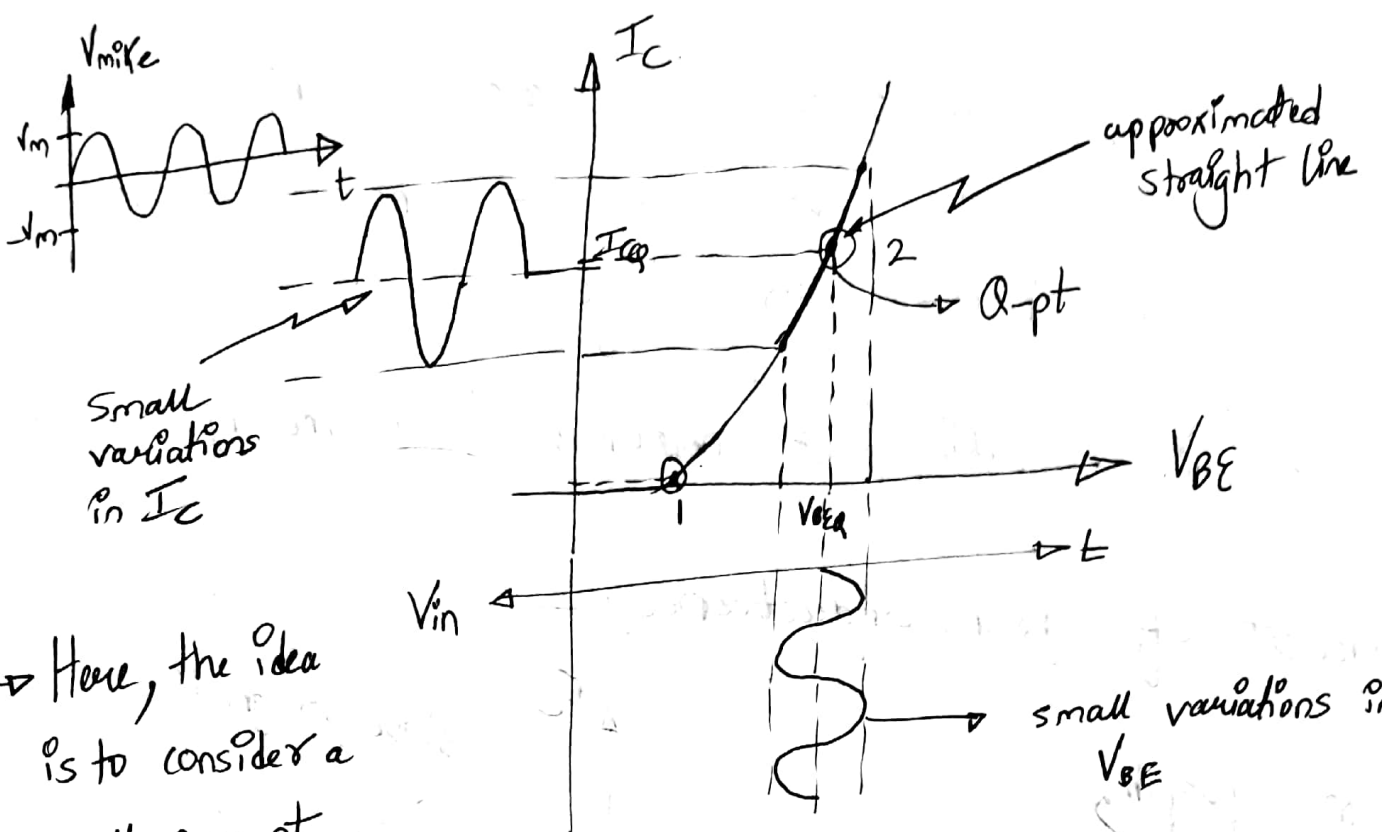Operating point : The bias values chosen for  $V_{BE}, I_C, V_{CE}, \dots$  etc.



→ Here, the idea is to consider a small segment of exponential curve to be


**Linear**

→ straight line

→ So our slp limit should be within this

Linear segment

→ Hence, called as small slg

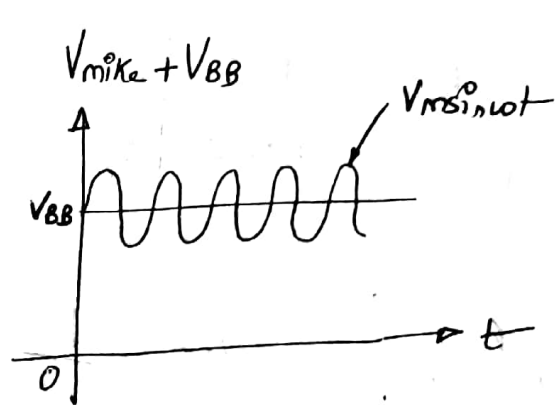

$I_S$  - reverse satn current  
eg  $10^{-15} A$

Observations:-

- 1) At point A, in absence of slg, variations in collector current are very small ( $\approx I_S$ ) i.e BJT is not biased & will not work in active region
- 2) At point B, BJT is biased in active region, since it has sufficient value of  $I_C$  &  $V_{BE}$


3) A bjt can acts as voltage-dependent current source  $\rightarrow$  since  $I_C$  changes in response to its base-emitter voltage.

4) The operating point determine how the bjt responds.

Concept of transconductance :-

from graph,

$$g_m = \left. \frac{dI_C}{dV_{BE}} \right|_{\text{opt}}$$

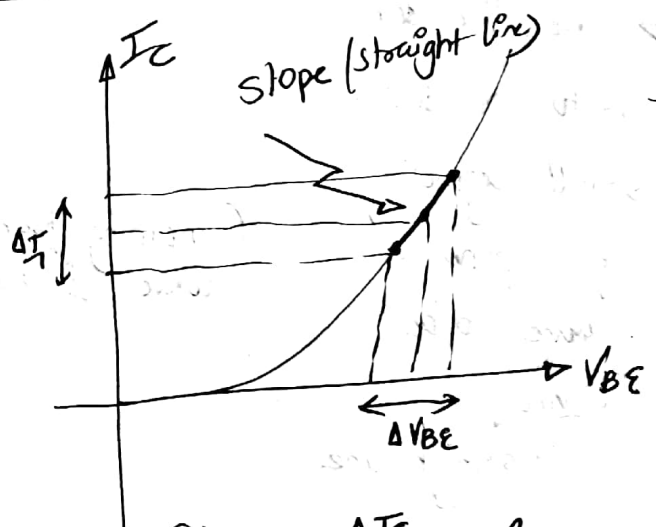

$$\text{Slope} = \frac{\Delta I_C}{\Delta V_{BE}} = g_m$$

slope of  $I_C$  vs  $V_{BE}$  characteristics

unit:  $\frac{1}{\Omega}$  or  $\frac{mA}{V}$

$$g_m = \frac{dI_C}{dV_{BE}}$$

$$= \frac{d}{dV_{BE}} \left( I_S \exp \frac{V_{BE}}{V_T} \right)$$

$$= \frac{I_S}{V_T} \exp \frac{V_{BE}}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$

$$\Delta I_C = \Delta V_{BE} g_m$$

Small changes in  $I_C$

small changes in  $V_{BE}$


slope

a constant

It suggest that base-to emitter voltage in a BJT controls the collector current

( $V_T = 26mV @ 27^\circ C$ )

$$g_m = \frac{I_{CQ}}{V_T}$$

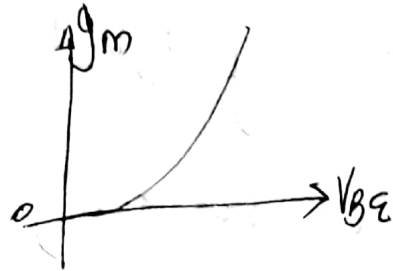

1) With no bias  $\Rightarrow I_C = 0 \Rightarrow g_m = 0$




2) For amplification, we need a certain  $g_m \Rightarrow$  certain  $I_{CQ} \rightarrow$  certain  $V_{BE}$

Small-signal operation:-

$\hookrightarrow$  The signal coming into the ckt is "small"  
 $\rightarrow$  The signal perturbs the bias (operating) point by only a small amount  $\hookrightarrow$  comparable to  $V_T$  value.

Small-sig parameter ( $r_{\pi}$ ) :-

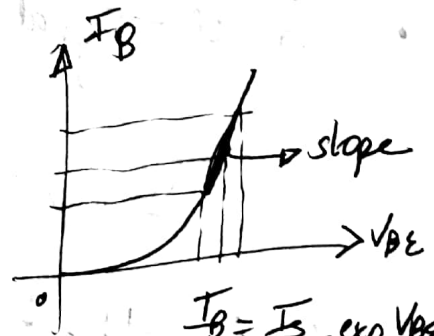Consider  $\Delta I_B$  characteristics of



bit


$$r_{\pi} = \frac{1}{\text{slope}} = \frac{\Delta I_B}{\Delta V_{BE}} \Big|_{V_{BE} = \text{constant}}$$

$$\text{ie } \frac{dI_B}{dV_{BE}} = \frac{d}{dV_{BE}} \left( \frac{I_S}{\beta} \exp \frac{V_{BE}}{V_T} \right) = \frac{I_S}{\beta \times V_T} \exp \left( \frac{V_{BE}}{V_T} \right)$$

$$\text{ie } \frac{dI_B}{dV_{BE}} = \frac{I_B}{V_T} \quad \text{ie } \boxed{\frac{dV_{BE}}{dI_B} = r_{\pi} = \frac{I_{BQ}}{V_T}}$$

Small-sig hybrid- $\pi$  model of bjt :-

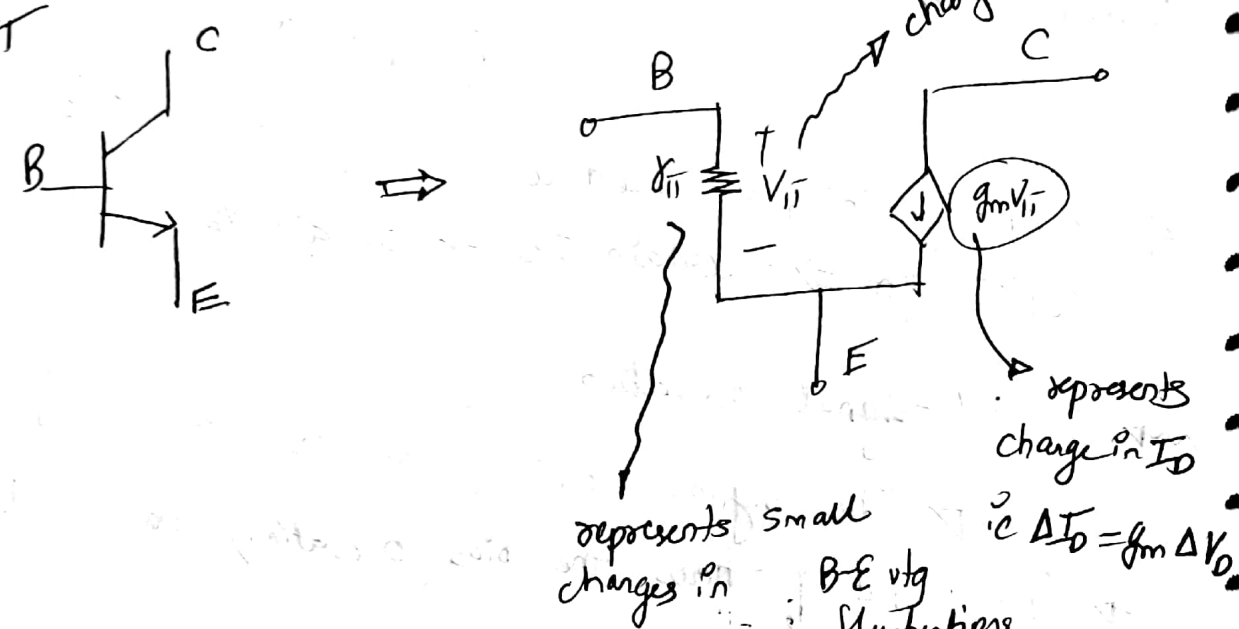
Now, we are ready to draw small-signal model of BJT




Small-signal model  $\rightarrow$  (represents only fluctuating quantities)

$\downarrow$  represent only changes in parameters

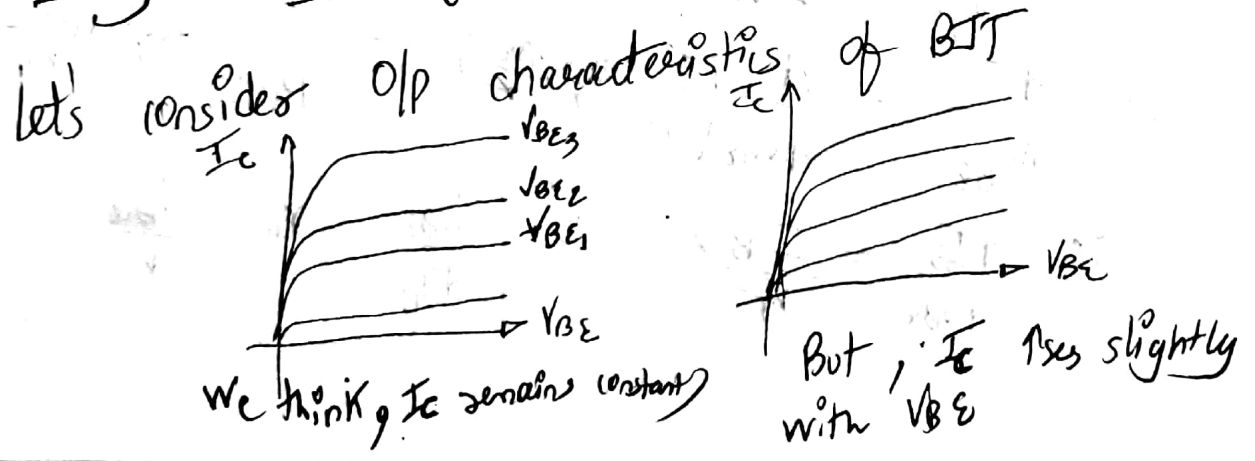Early effect (small-sig o/p resistance/impedance) (x<sub>o</sub> DR x<sub>d</sub>)



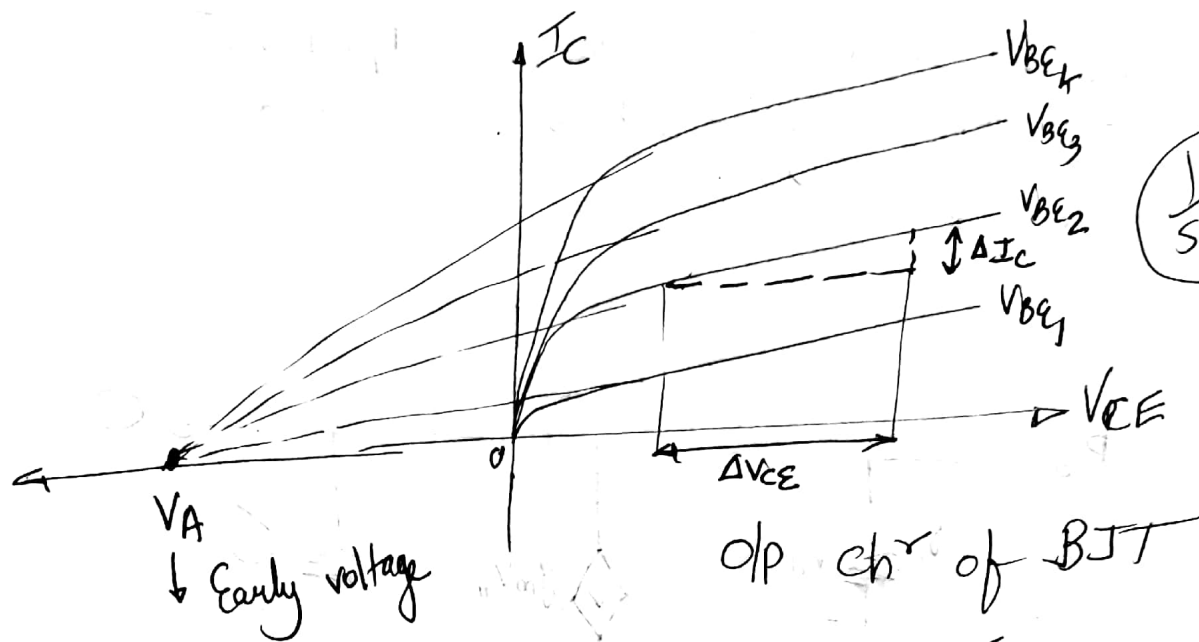

$\frac{1}{\text{slope}} = r_o \text{ or } r_d$

- In above graph, if we extrapolate  $I_c$  curve to -ve axis of  $V_{ce}$ , these family of curves meet at a point called "Early voltage"  $V_A$ .
- In reality,  $I_c$  ↑ses slightly with  $V_{ce}$  due to early effect.

$$I_c = \left( I_s \exp \frac{V_{BE}}{V_T} \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$V_A$ : Early voltage

$$\text{slope} = \frac{dI_c}{dV_{CE}} = \left( \frac{I_s}{V_A} \exp \frac{V_{BE}}{V_T} \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$\text{ie } \frac{dI_c}{dV_{CE}} = \frac{I_{CQ}}{V_A}$$

$$\text{ie } r_o = r_d = \frac{dV_{CE}}{dI_c} = \frac{V_A}{I_{CQ}}$$


$$\text{ie } r_o = r_d = \frac{V_A}{I_{CQ}}$$

• We need to include in small-sig model.

←  $r_o$ , Small-sig op resistance of a bjt biased in forward active region.

Complete small signal model of npn BJT including early effect is given below

08

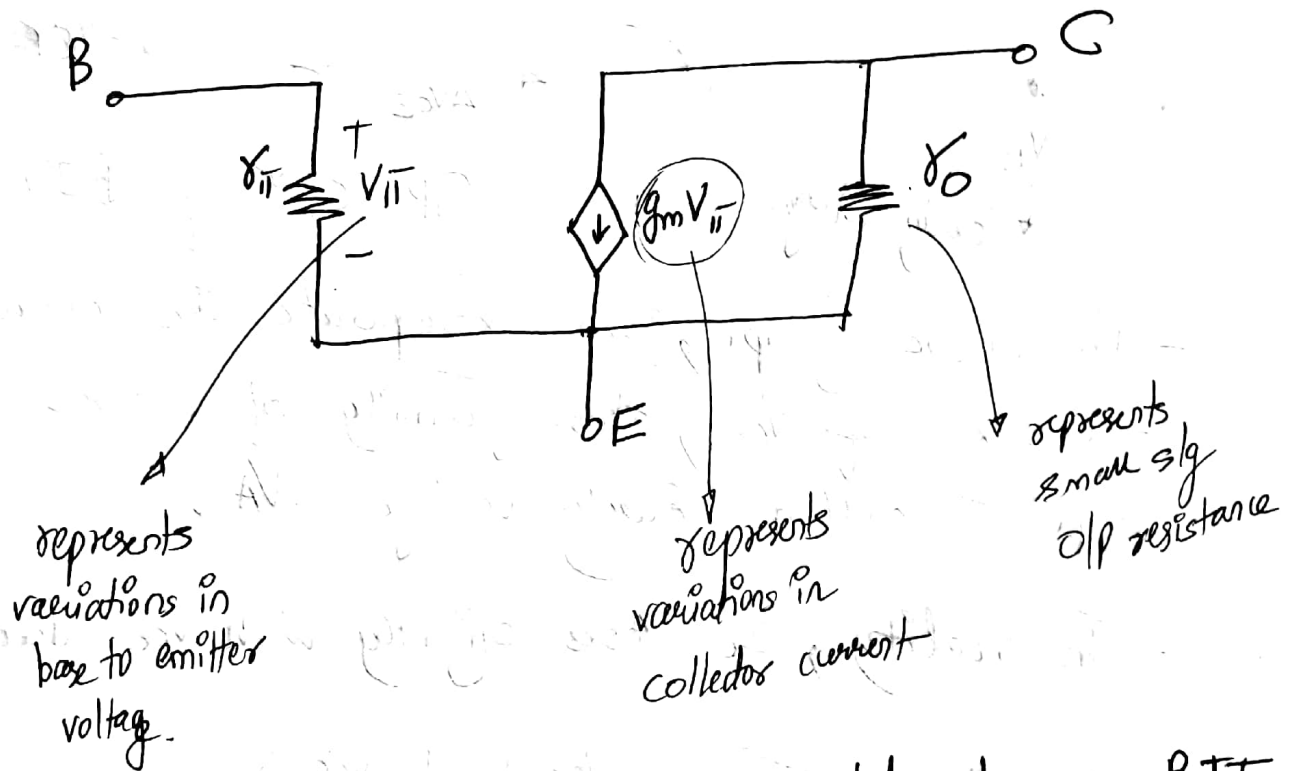

Small-signal hybrid- $\pi$  model of npn BJT

→ Small-signal parameters :-

1. 
$$r_{\pi} = \frac{\beta_{ac} V_T}{I_{BQ}}$$

3. 
$$r_o = \frac{V_A}{I_{CQ}}$$


2. 
$$g_m = \frac{I_{CQ}}{V_T}$$



# AC Analysis of BJT amplifier:-

09  
18/10/19


## 1. Common emitter amplifier:-

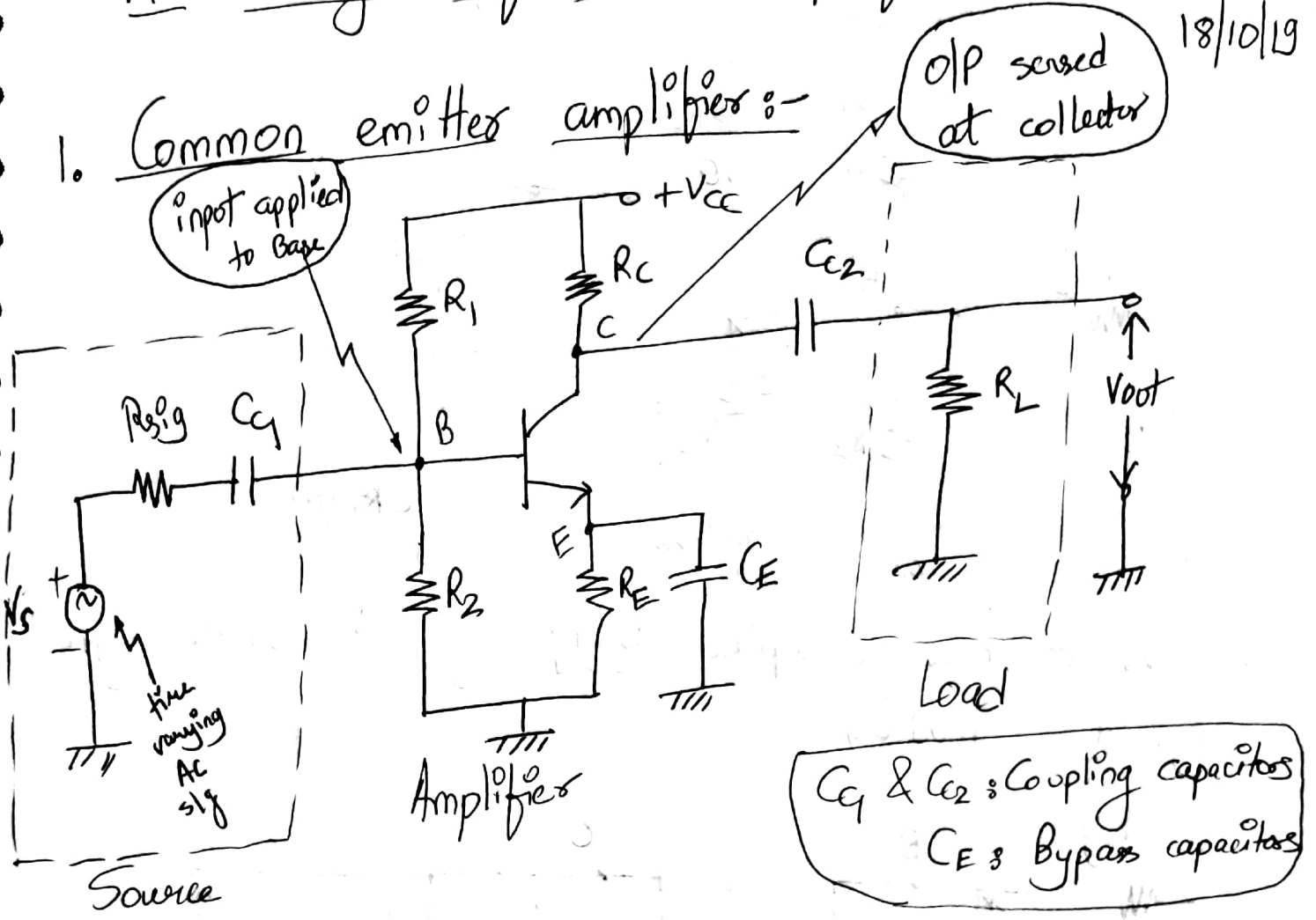

### Observations


1. In CE amplifier, i/p signal is applied to the "base" terminal and o/p is sensed at the "Collector" terminal.
2. For AC analysis, all the capacitors are replaced by a short circuit  $\rightarrow$  as the capacitive impedances ( $X_c = \frac{1}{2\pi fC}$ ) are very low at mid-frequencies.
3. DC supply is also replaced by a short circuit for small signal (AC) analysis.

→ AC equivalent circuit is,

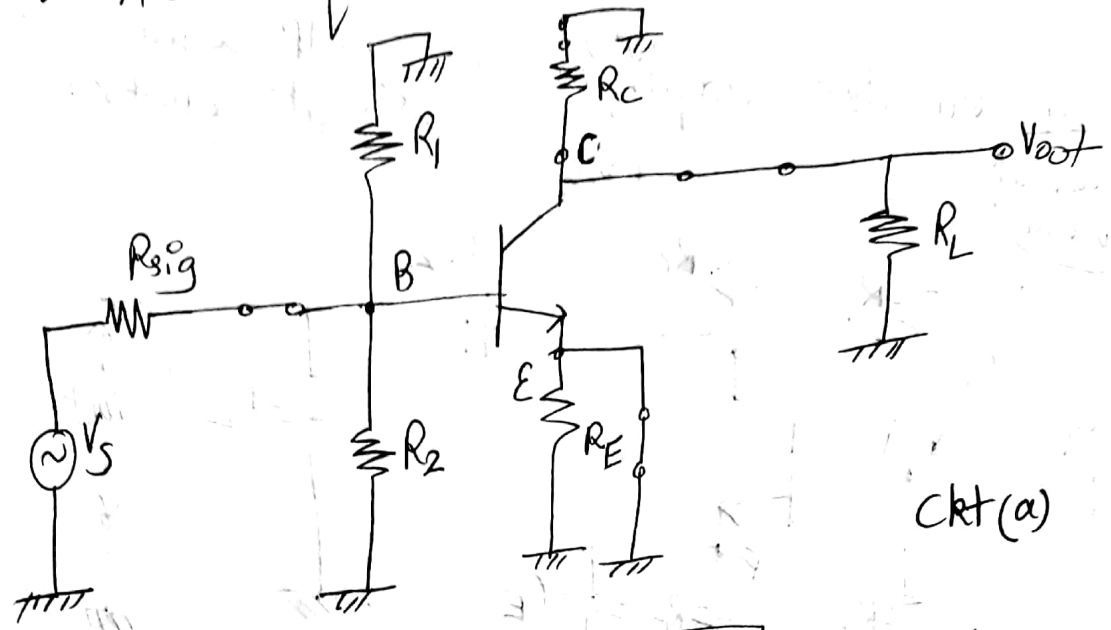

Ckt (a)

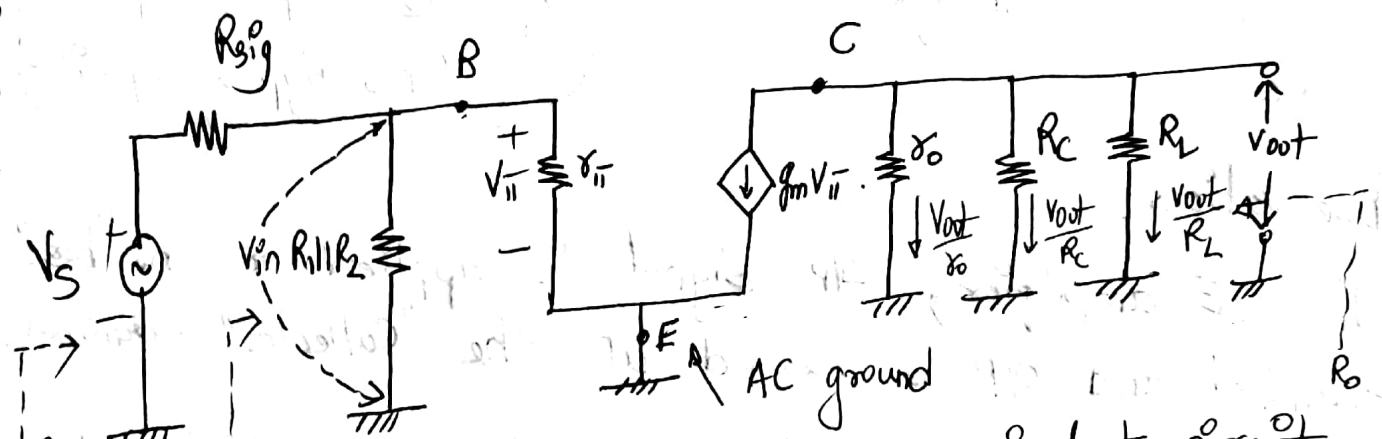→ Now, we have to replace BJT by its small-signal hybrid- $\pi$  model,



Ckt (b): Small-signal equivalent circuit

Analysis:

1) To find  $A_v$ : voltage gain expression

From ckt b,  $V_{in} = V_{\pi}$

KCL at Collector terminal,

$$g_m V_{in} + \frac{V_{out}}{r_o} + \frac{V_{out}}{R_c} + \frac{V_{out}}{R_L} = 0$$

$$g_m V_{in} = -V_{out} \left( \frac{1}{r_o} + \frac{1}{R_c} + \frac{1}{R_L} \right)$$

$$\rightarrow A_v = \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_c \parallel R_L)$$

Small-sig voltage gain of amplifier

-ve sign indicates that I/P & o/p are out-of phase

$$\text{Now, } A_{v_s} = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s} = A_v \times \frac{V_{in}}{V_s}$$

$$\text{From ckt (b), } A_{v_s} = A_v \frac{V_{in}}{V_s}$$



$$\rightarrow \frac{V_{in}}{V_s} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sig}} \quad \text{--- by V.D.R}$$

$$\text{ie } A_{v_s} = A_v \times \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sig}}$$

## 2) Input impedance/resistance ( $Z_i/R_i$ ):

12

From ckt (b),

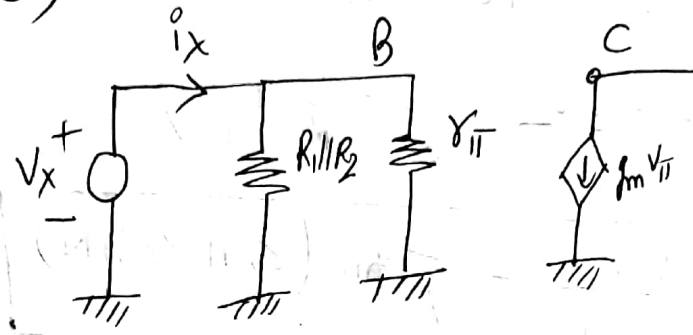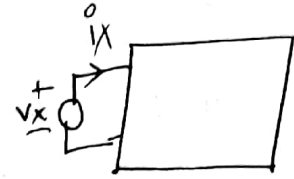


Since, B-C junction is reverse-biased & open-ckt, no current flows from B to C in ckt above,

∴ Current  $i_x$  flows into  $(R_1 || R_2)$  branch &  $r_{\pi}$  branch

$$\frac{V_x}{i_x} = R_1 || R_2 || r_{\pi}$$

∴  $R_i = R_1 || R_2 || r_{\pi}$

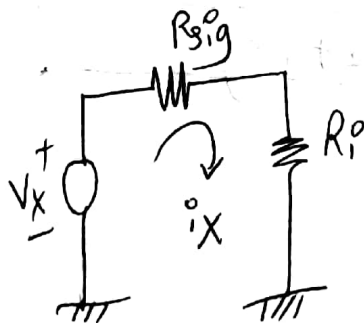Now, if we include source resistance  $R_{sig}$ , we have




$$R_{is} = \frac{V_x}{i_x} = R_{sig} + R_i$$

∴  $R_{is} = R_{sig} + R_1 || R_2 || r_{\pi}$
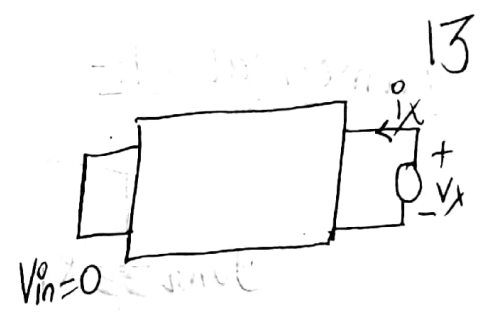
### 3. o/p impedance/resistance : $(Z_o/R_o)$

For o/p resistance calculation,  
we short-ckt o/p source.




ie  $V_{in} = 0$  ie  $V_s = 0$   
ie Since  $V_{in} = V_{ii} \Rightarrow V_{ii} = 0$

$g_m V_{ii} = 0$


It means that  
a current source  
being zero

Referring ckt (B), we get

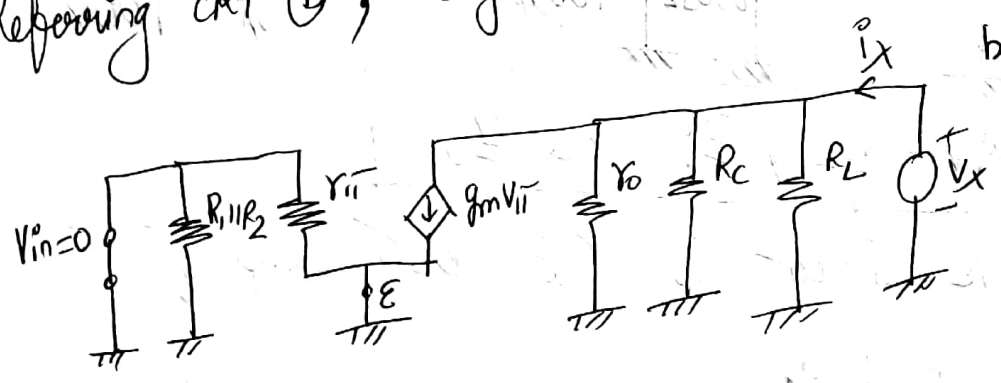

it is replaced  
by open-ckt


Above ckt reduces to

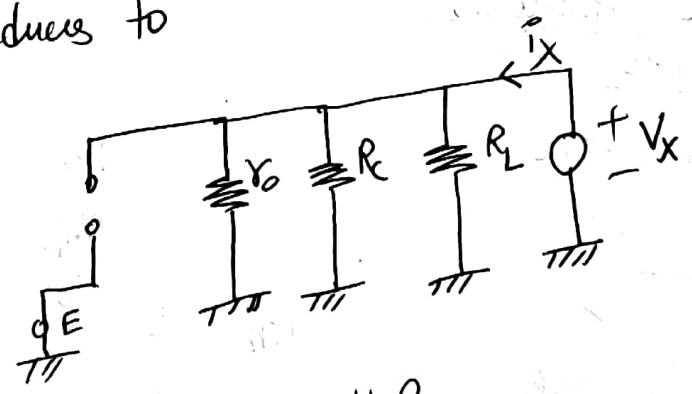

ie  $\frac{V_x}{i_x} = R_o \parallel R_c \parallel R_L$

ie  $R_o = R_o \parallel R_c \parallel R_L$

# Numerical 01:-

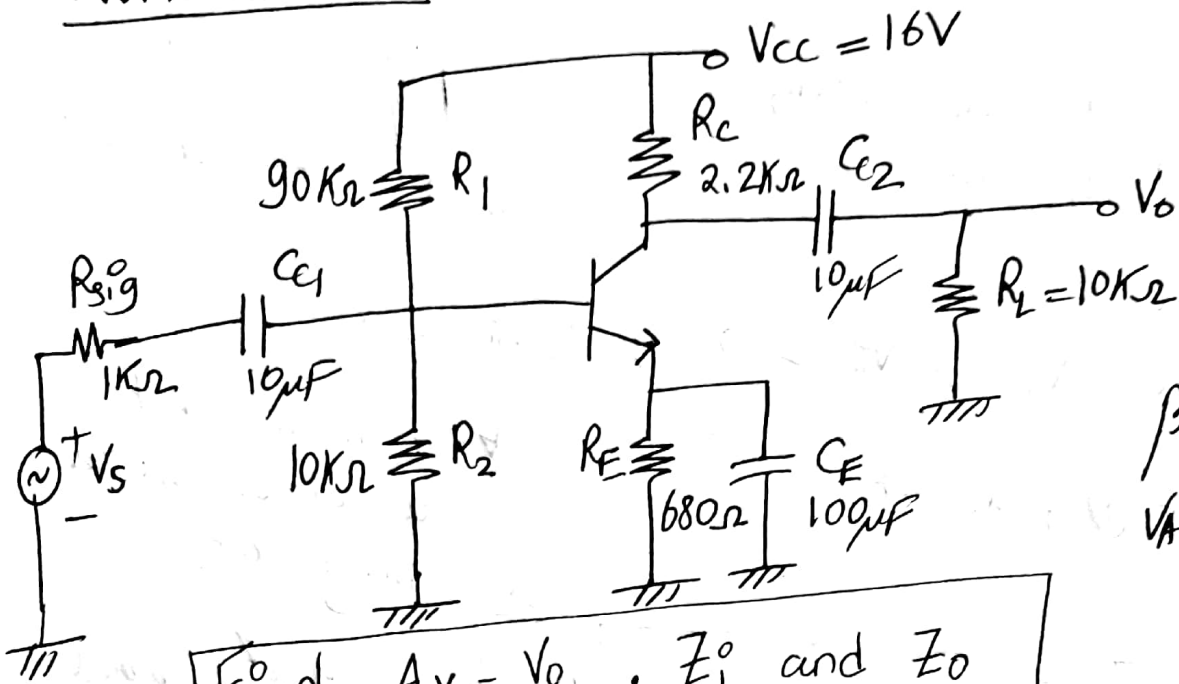


$\beta = 210$   
 $V_A = 100V$

Find  $A_v = \frac{V_o}{V_s}$ ,  $Z_i$  and  $Z_o$

Sol<sup>n</sup>:

1] Above circuit is CE BJT amplifier

2] DC Analysis

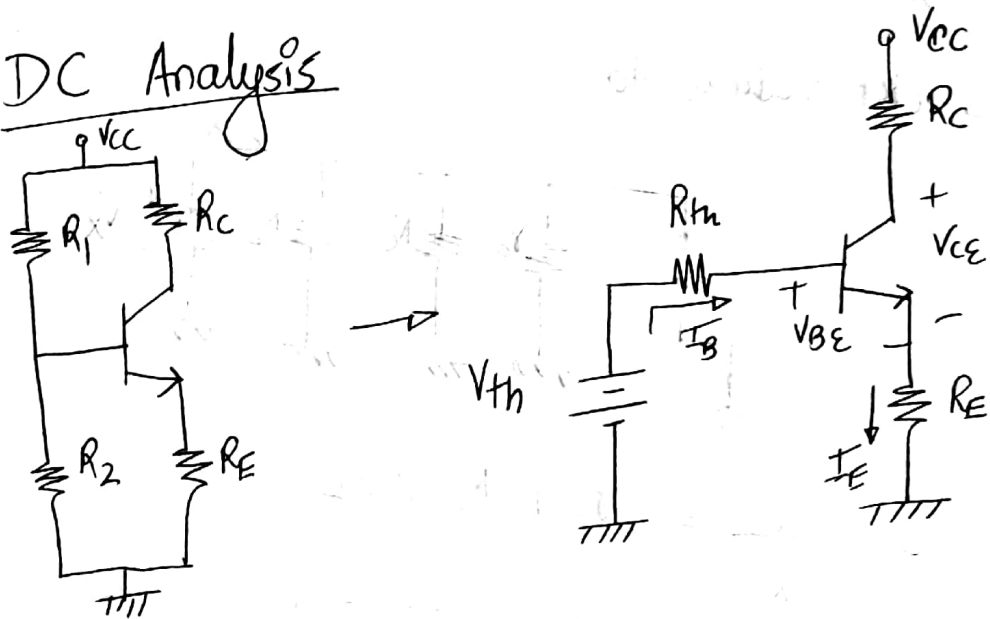

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{cc} = \frac{10K}{10K + 90K} \times 16 = 1.6V$$

$$R_{th} = R_1 \parallel R_2 = 10K \parallel 90K = 9K\Omega$$

KVL to B-E loop gives,

$$V_{th} - I_B R_{th} - V_{BE(on)} - I_E R_E = 0$$

$$I_E = (1 + \beta) I_B$$

$$\rightarrow V_{th} - I_B R_{th} - V_{BE(on)} - (1 + \beta) I_B R_E = 0$$

$$\rightarrow I_B = \frac{V_{th} - V_{BE(on)}}{R_{th} + (1 + \beta) R_E}$$

Assume  $V_{BE(on)} = 0.7V$

$$I_B = \frac{1.6 - 0.7}{9K + 211 \times 680} = \underline{5.9 \mu A}$$

$$\rightarrow I_{CQ} = \beta I_B = \underline{1.2395 mA}$$

$$\rightarrow I_{EQ} = I_{CQ} + I_B = \underline{1.2454 mA}$$

3] Small-signal parameters:-


$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.2395 mA}{26 mV} = 47.67 \frac{mA}{V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{1.2395 mA} = 80.68 K\Omega$$

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{26 mV}{5.9 \mu A} = 4.4 K\Omega$$

#### 4] Small-sig equivalent circuit:-

16

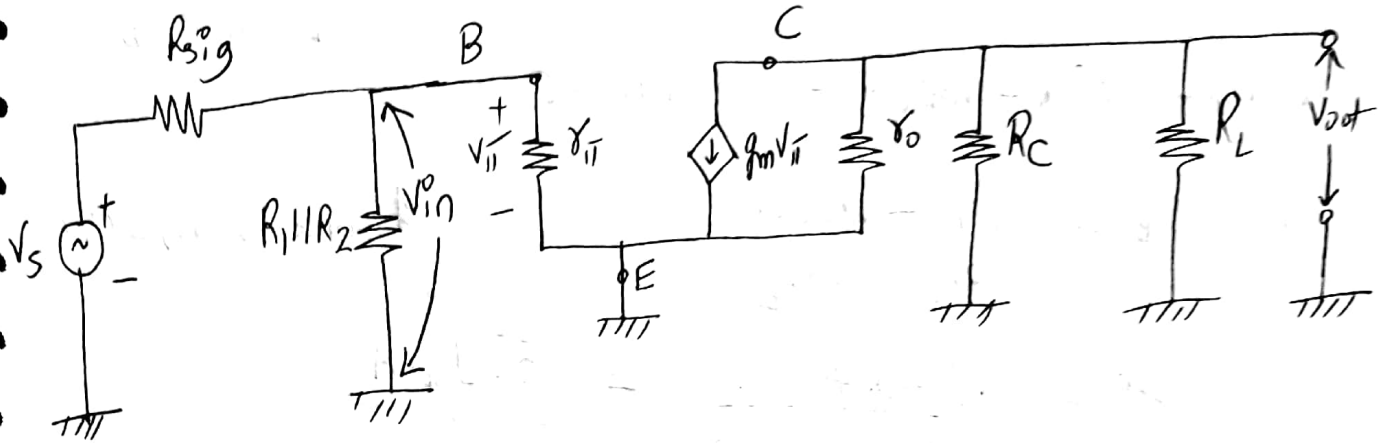

→ I/P impedance  $Z_i = R_1 \parallel R_2 = 90K \parallel 10K\Omega$

$$Z_i = 9K\Omega$$

$Z_{is} \text{ with } R_{sig} = R_{sig} + Z_i = 1K\Omega + 9K\Omega = 10K\Omega$

→ O/P impedance  $Z_o = r_o \parallel R_C \parallel R_L$   
 $= 80.68K \parallel 2.2K\Omega \parallel 10K\Omega$   
 $= 80.68K \parallel 1.8K\Omega$

$$Z_o = 1.76K\Omega$$

→ Voltage gain  $A_v = \frac{V_o}{V_{in}}$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_s} = A_v \times \frac{V_{in}}{V_s}$$



$$A_v = \frac{V_o}{V_{in}}$$

$$= -g_m (r_o \parallel R_L \parallel R_C)$$

$$= -47.67 \times 10^{-3} \times 1.76 \text{ K}\Omega$$

$$\boxed{A_v = -83.89}$$

$$A_{v_s} = A_v \times \frac{V_{in}}{V_s}$$

$$\frac{V_{in}}{V_s} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sig}} = \frac{9 \text{ K}}{9 \text{ K} + 1 \text{ K}} = 0.9$$


$$A_{v_s} = \frac{V_o}{V_s} = A_v \times 0.9 = -83.89 \times 0.9$$

$$\boxed{A_{v_s} = -75.5}$$

----- voltage gain of given CE amplifier


→ -ve sign indicates 180° out of phase between I/P and O/P signals.
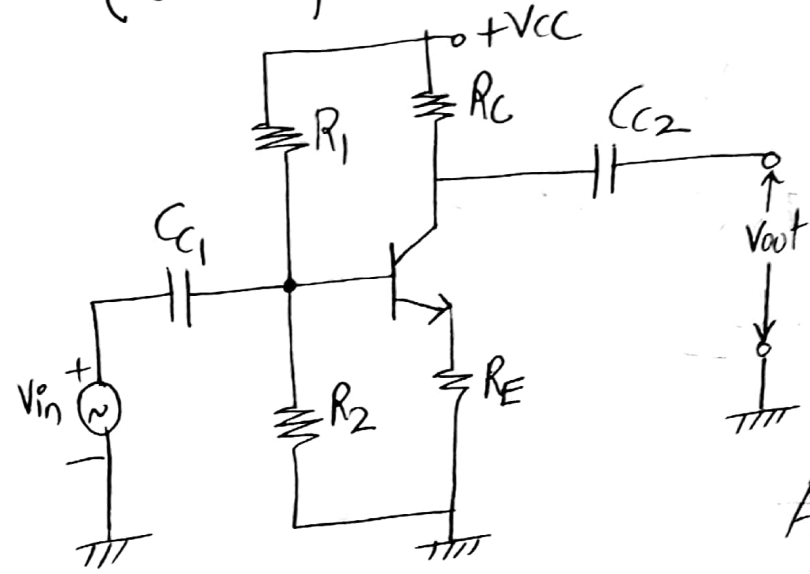
## 2. Degenerated Common-emitter amplifier : (CE ampl<sup>r</sup> with $R_E$ unbypassed)



Assume  $r_o = \infty$  for analysis


### AC analysis:-

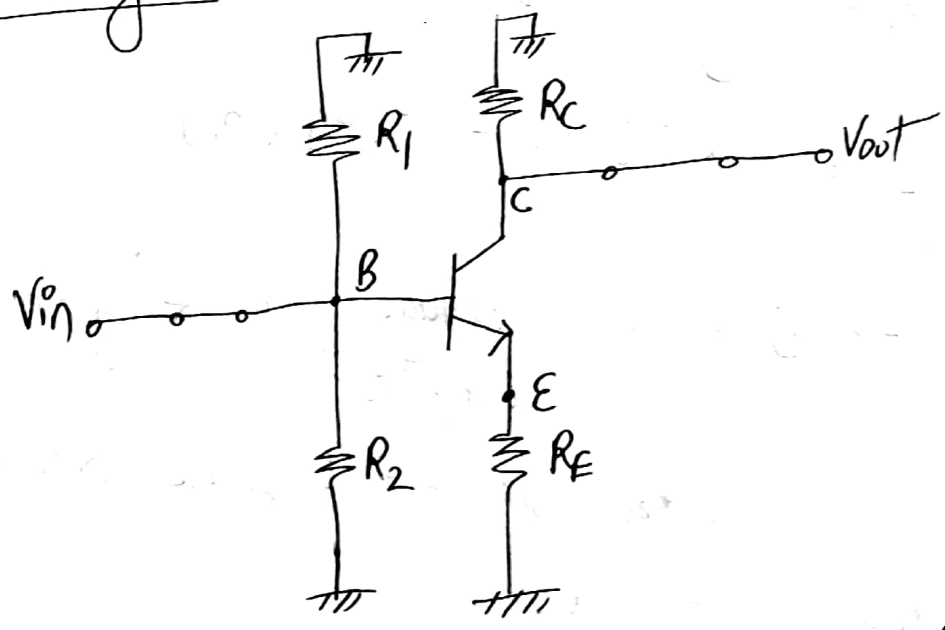

Next, we replace BJT by its small sig hybrid- $\pi$  model

Small-signal Voltage gain:  $A_v = \frac{V_{out}}{V_{in}}$

19

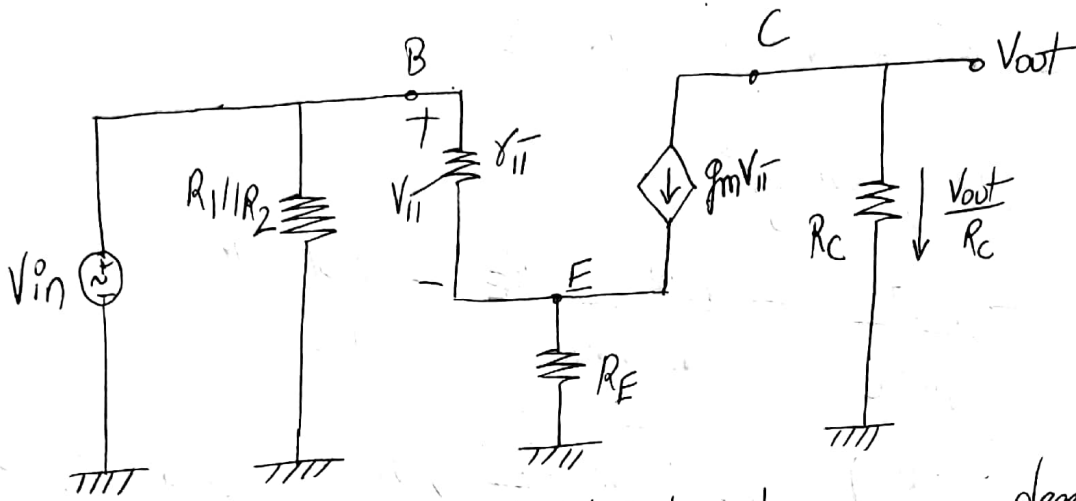

(kt a) Small-sig equivalent ckt of a degenerated CS stage

KCL at 'C' node,  $g_m V_{be} + \frac{V_{out}}{R_C} = 0$

ie  $V_{be} = -\frac{V_{out}}{g_m R_C}$  — (1)

KCL at 'E' node,

$\left( \frac{V_{be}}{r_{\pi}} + g_m V_{be} \right) R_E = \text{voltage drop on } R_E$   
current through  $R_E$

ie  $\left[ \frac{-V_{out}}{g_m R_C} \times \frac{1}{r_{\pi}} + g_m \left( \frac{-V_{out}}{g_m R_C} \right) \right] R_E = \text{voltage drop on } R_E$  — (2)

KVL in B-E loop, gives

$$V_{in} = V_{ii} + \text{voltage drop on } R_E$$

From (1) & (2), we get

$$V_{in} = -\frac{V_{out}}{g_m R_C} - \frac{V_{out}}{g_m r_{ii} R_C} R_E - \frac{V_{out}}{R_C} R_E$$

$$\boxed{g_m r_{ii} = \beta} \quad ? \rightarrow \left\{ \begin{array}{l} g_m = \frac{I_C}{V_T} ; r_{ii} = \frac{V_T}{I_B} \\ g_m r_{ii} = \frac{I_C}{I_B} = \beta \end{array} \right.$$

$$V_{in} = -\frac{V_{out}}{g_m R_C} - \frac{V_{out}}{\beta R_C} R_E - \frac{V_{out}}{R_C} R_E$$

$$V_{in} = -\frac{\beta V_{out} + g_m R_E V_{out} + \beta g_m R_E V_{out}}{\beta g_m R_C}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{-\beta g_m R_C}{\beta + (1+\beta) g_m R_E}}$$

Let's, simplify it further

Multiply & divide by  $\beta g_m$

$$\frac{V_{out}}{V_{in}} = - \frac{R_C}{\frac{1}{g_m} + \frac{(1+\beta) R_E}{\beta}}$$

$$\text{But } \frac{1+\beta}{\beta} \approx 1$$

$$\text{ie } A_v = \frac{V_{out}}{V_{in}} \approx - \frac{R_C}{\frac{1}{g_m} + R_E}$$


----- small sig voltage gain of degenerated CS amplifier

→ The voltage gain of degenerated CS amplifier has certainly reduced, but it is more stable

→ let's verbalize the above result,


$$A_v = - \frac{\text{resistance tied between Collector \& gnd}}{\frac{1}{g_m} + \text{resistance tied betn emitter \& gnd.}}$$

Input Impedance:

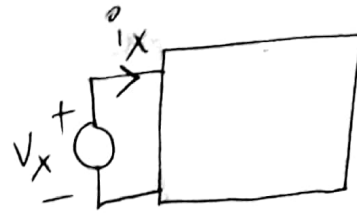


$$Z_i = \frac{V_x}{i_x}$$

let's draw ckt(a),

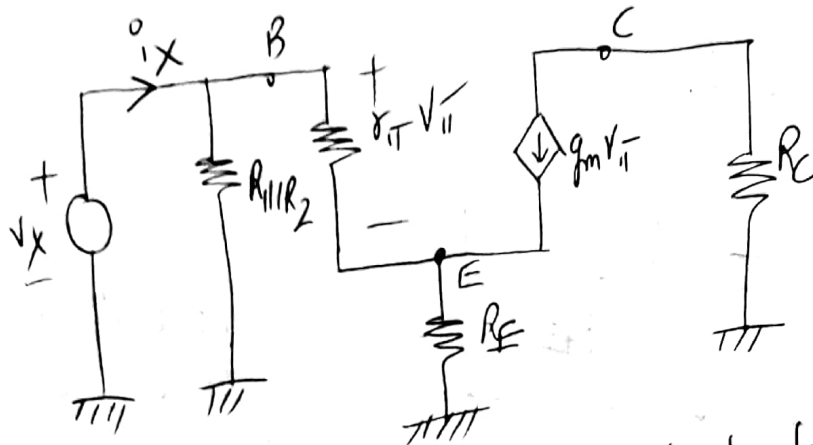

let's just push  $(R_1 || R_2)$  branch to left of source  $V_x$  for simplicity in analysis

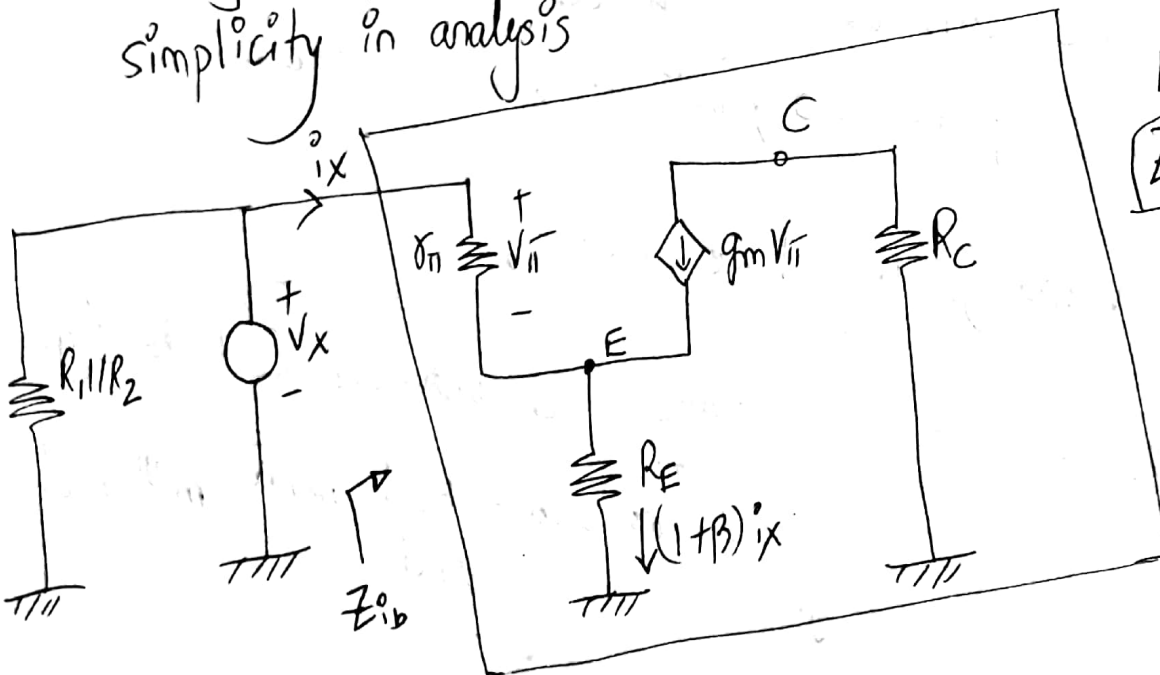

Now,

$$Z_i = Z_{ib} || R_1 || R_2$$

From ckt,  $V_{\pi} = i_x r_{\pi}$

$$\rightarrow g_m V_{\pi} = g_m i_x r_{\pi} = \beta i_x = i_c$$

$$\text{current through } R_E = i_E = (1 + \beta) i_x$$

KVL to B-E loop gives,

$$V_x = V_{\pi} + V_{RE}$$

$$V_x = i_x \delta_{\pi} + (1+\beta) i_x R_E$$

$$V_{RE} = i_E R_E = (1+\beta) i_x R_E$$



$$V_x = i_x [\delta_{\pi} + (1+\beta) R_E] \rightarrow \frac{V_x}{i_x} = \delta_{\pi} + (1+\beta) R_E$$

$$Z_{iB}^o = \frac{V_x}{i_x} = \delta_{\pi} + (1+\beta) R_E$$


ie  $Z_o = R_1 || R_2 || [\delta_{\pi} + (1+\beta) R_E]$  ----- high  $\Gamma_P$  impedance

\* Output impedance  $Z_o$

Redrawing ckt(a) with  $V_{in} = 0$

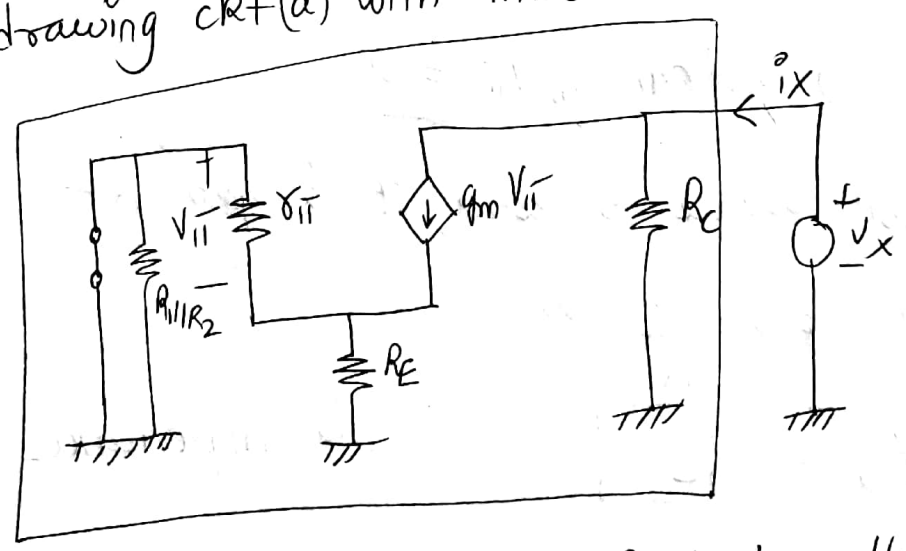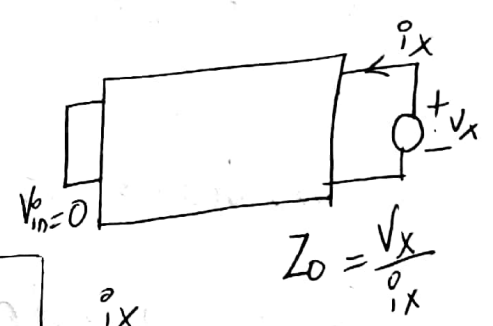

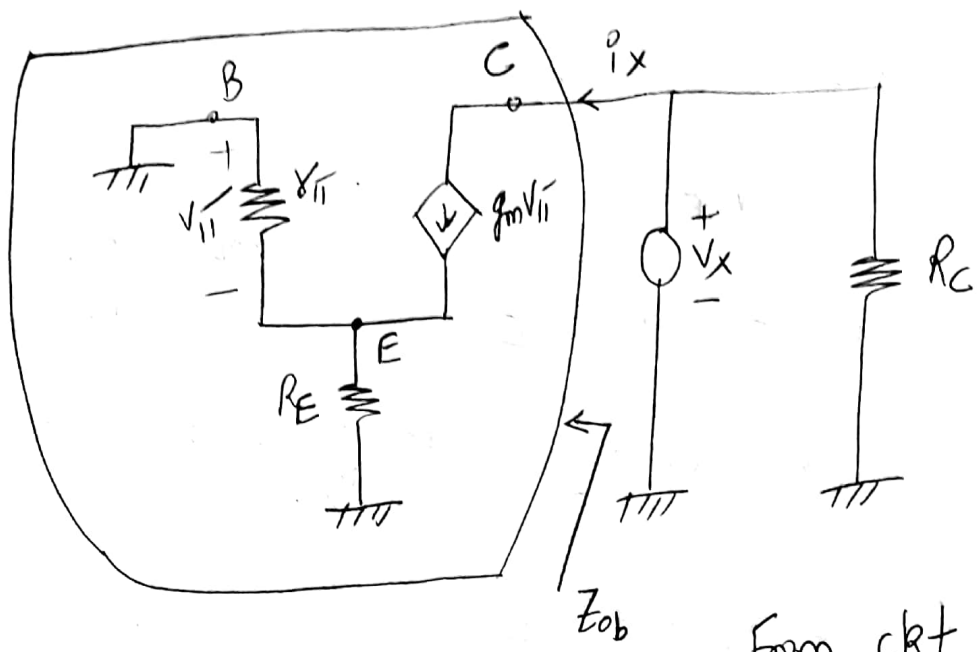Next we push  $R_C$  to the right of voltage source  $V_x$  for simplicity,



$$Z_0 = Z_{ob} || R_C$$

From CKT  $V_{RE} = -V_{ii}$

KCL at 'E' node gives,

$$\frac{V_{ii}}{r_{\pi}} + g_m V_{ii} = \frac{-V_{ii}}{R_E}$$

This implies  $V_{ii} = 0$

If  $V_{ii} = 0$ ; then  $g_m V_{ii} = 0$

ie current source is zero, it is open CKT


$$\text{ie } Z_{ob} = \frac{V_x}{i_x} = \infty$$

∴  $Z_0 = R_C$  ----- O/p impedance



Why gain of CE amplifier is negative?

25

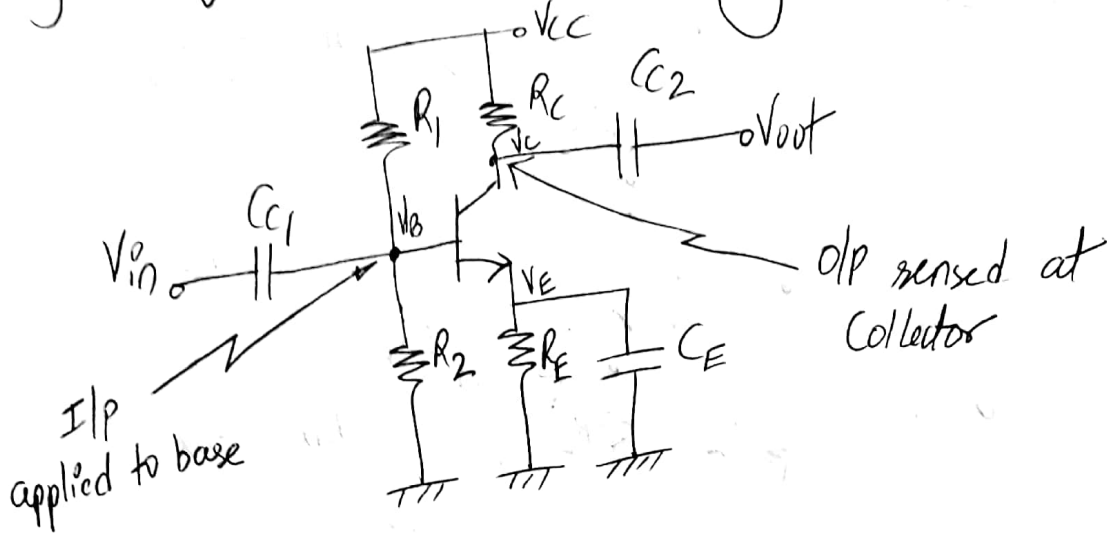

let say's  $V_{in}^{(ac)}$  ↑ses, then  $V_B$  ↑ses (as  $V_B + V_{in}^{(ac)}$  is at B)


Now,  $V_E^{(DC)}$  is a constant, since capacitor  $C_E$  blocks DC values

ie  $V_{BE} = (V_B - V_E)$  ↑ses which means  $I_B$  ↑ses

Now,  $I_C = \beta I_B$ ; if  $I_B$  ↑ses  $\rightarrow I_C$  ↑ses


Also,  $V_C = V_{CC} - I_C R_C$ ; if  $I_C$  ↑ses then  $V_C$  ↓ses  
ie  $V_{out}$  ↓ses

In summary in CE amplr:

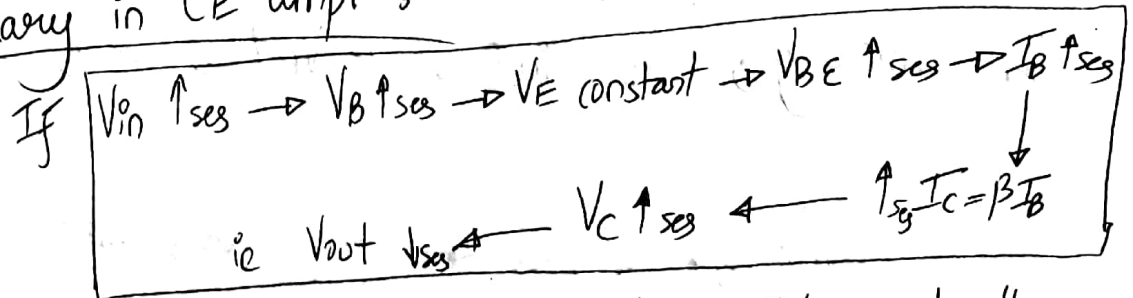

ie I/P and o/p signals are out of phase with each other, hence voltage gain is -ve in CE amplr.
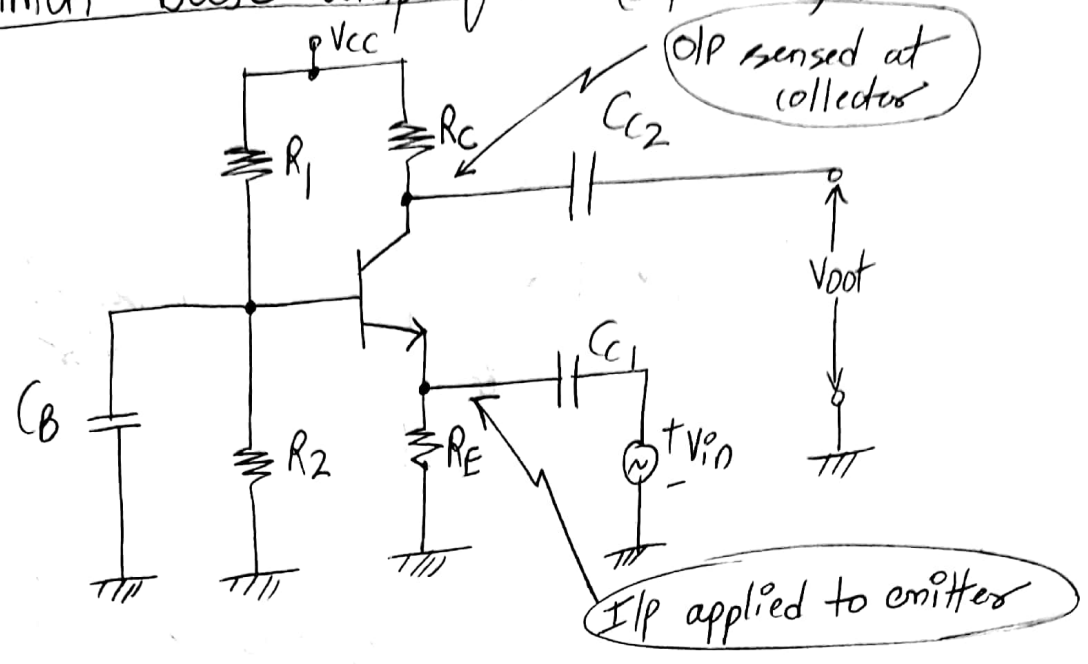
### 3] Common Base amplifier (npn BJT) :-



let says,  $V_{in}$  ↑ sees i.e.  $V_E$  ↑ sees (as  $V_E + V_{in}$  is at E terminal)  
 (DC) (AC)

$V_B$  is a constant, as  $C_B$  blocks DC value  
 (DC)

i.e.  $V_{BE} = (V_B - V_E) ↓$  sees  $\rightarrow I_B ↓$  sees


$I_C = \beta I_B$  ; if  $I_B ↓$  sees  $\rightarrow I_C ↓$  sees

Also,  $V_C = V_{CC} - I_C R_C$  i.e. If  $I_C ↓$  sees  $\rightarrow V_C ↓$  sees  
 i.e.  $V_{out} ↓$  sees

In summary, As  $V_{in} ↑$  sees  $\rightarrow V_E ↑$  sees  $\rightarrow V_B$  constant  $\rightarrow V_{BE} ↓$  sees  
 $\rightarrow I_B ↓$  sees  $\rightarrow I_C ↓$  sees  $\rightarrow V_C ↓$  sees  $\rightarrow V_{out} ↓$  sees


i.e. I/P & O/P signal in a CB amplifier are in phase with each other.

# AC Analysis:-

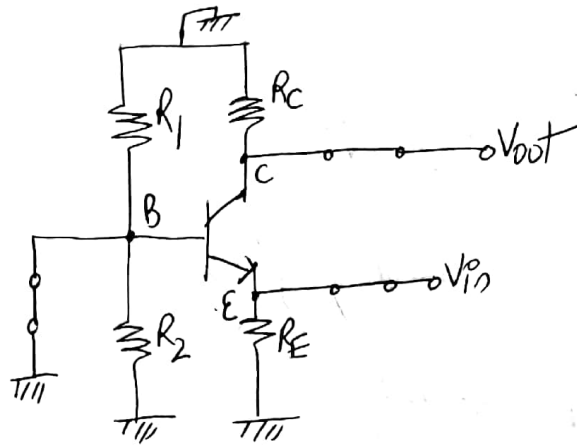


Assume  
 $V_A = \infty$   
 $r_o \rightarrow \infty$

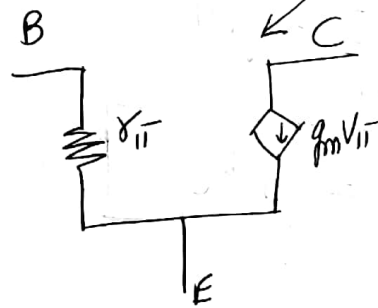Next, we replace BJT by its small-signal hybrid model,



Small-signal voltage gain:  $A_v = \frac{V_{out}}{V_{in}}$

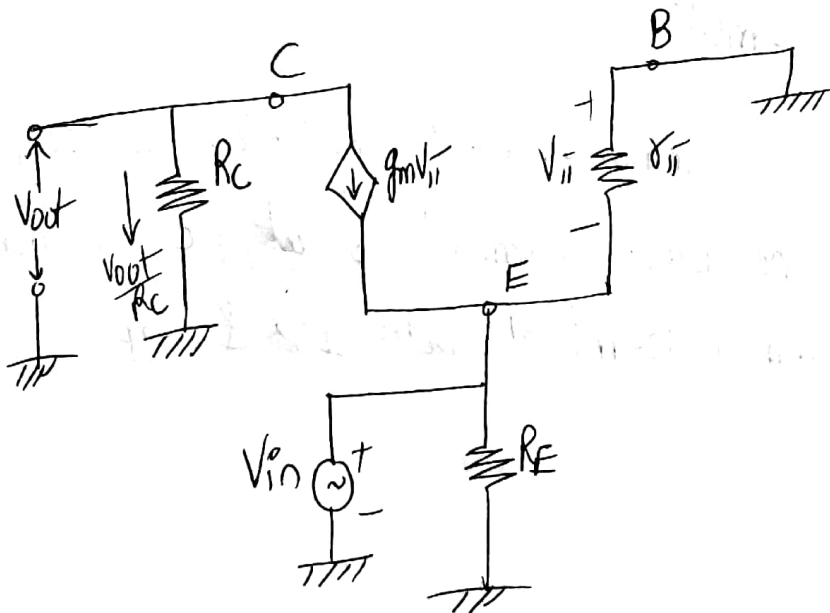we interchange B & C terminals for simplicity



ckt (b) : Small-sig equivalent ckt of CB amplifier

From ckt(b),  $V_{ii} = -V_{in}$

KCL at 'c' node, gives

$$g_m V_{ii} + \frac{V_{out}}{R_c} = 0$$

$$i_e - g_m V_{in} = -\frac{V_{out}}{R_c}$$

$$i_e \frac{V_{out}}{V_{in}} = g_m R_c$$


$$i_e \boxed{A_v = +g_m R_c}$$

----- Small -sig voltage gain


→ The +ve sign in gain formula indicates no phase difference betn the input and o/p signals. in a Common Base ampl<sup>r</sup>

→ It is called "Common-base" amplifier since, in AC analysis, the base terminal is at ac ground & act as common terminal betn I/P & o/P.

Input impedance:  $Z_i^o$

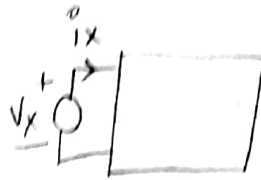

Redrawing ckt(b),

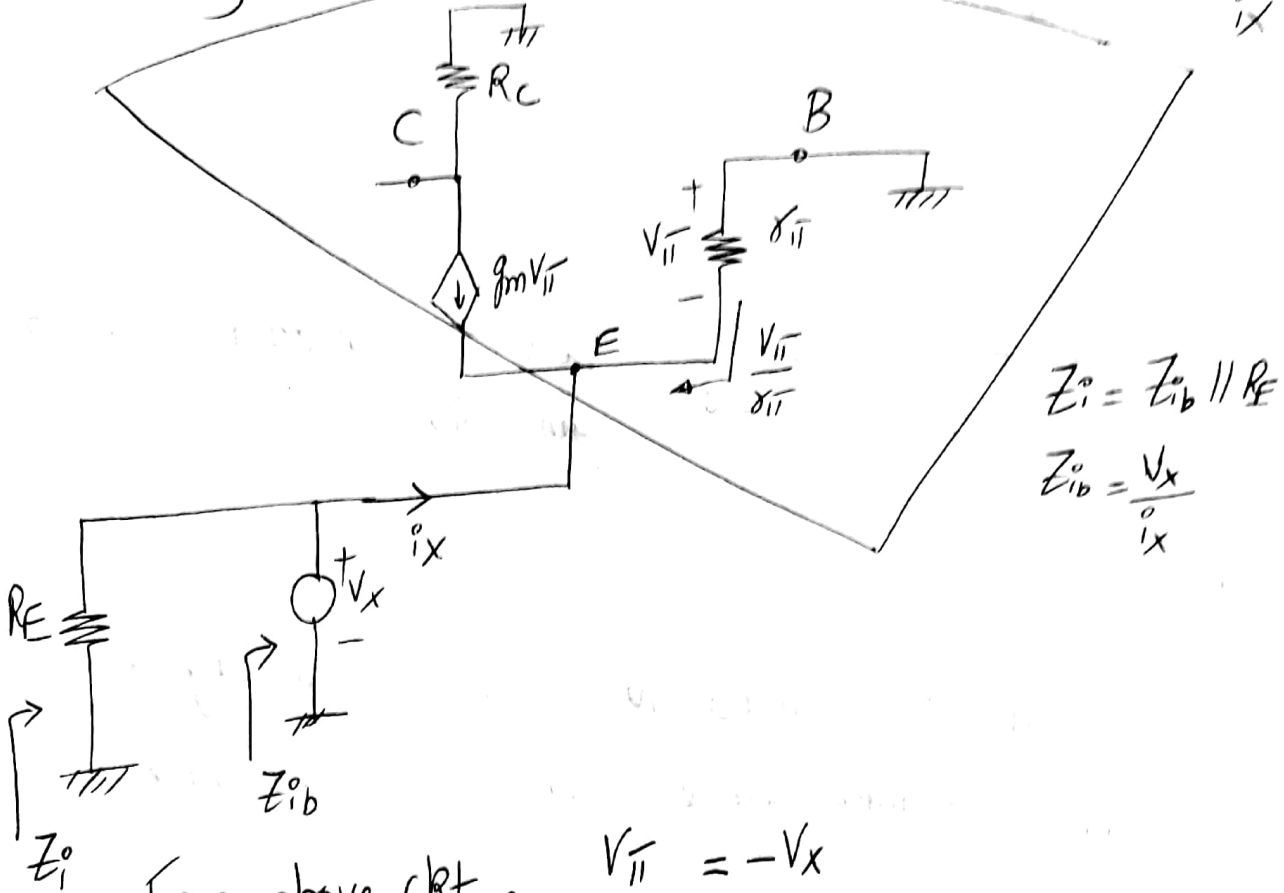

$$Z_i^o = \frac{V_x}{i_x}$$

$$Z_i^o = Z_{ib} \parallel R_E$$

$$Z_{ib} = \frac{V_x}{i_x}$$

From above ckt,  $\frac{V_{11}}{i_x} = -V_x$

KCL at 'E' node, gives

$$i_x + g_m V_{11} + \frac{V_{11}}{r_{11}} = 0$$

$$i_x = -V_{11} \left( g_m + \frac{1}{r_{11}} \right)$$

$$i_x = V_x \left( \frac{1 + g_m r_{11}}{r_{11}} \right)$$

$$i_x = V_x \left( \frac{1 + \beta}{r_{11}} \right)$$

$$g_m r_{11} = \beta$$

$$1 + \beta = \beta$$

$$i_x = V_x \left( \frac{\beta}{r_{\pi}} \right)$$

$$g_m = \frac{\beta}{r_{\pi}}$$

$$i_x = V_x g_m$$


$$\frac{V_x}{i_x} = \frac{1}{g_m}$$

Now,  $Z_i = \frac{1}{g_m} \parallel R_E$

Low  $Z_i$  impedance in CB amplifier


Application :

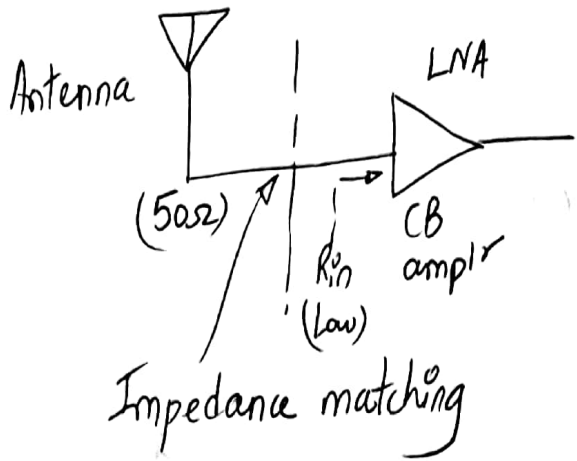↳ CB amplifier is used to be driven by a low impedance source such as an antenna.




which is also of low impedance of around 50Ω

O/P impedance:  $Z_o$

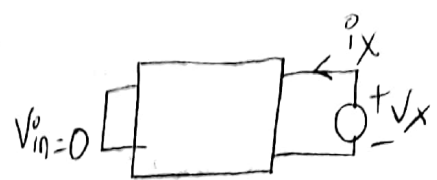

Redrawing ckt (b) by making  $V_{in} = 0$


$$Z_o = \frac{V_x}{i_x}$$

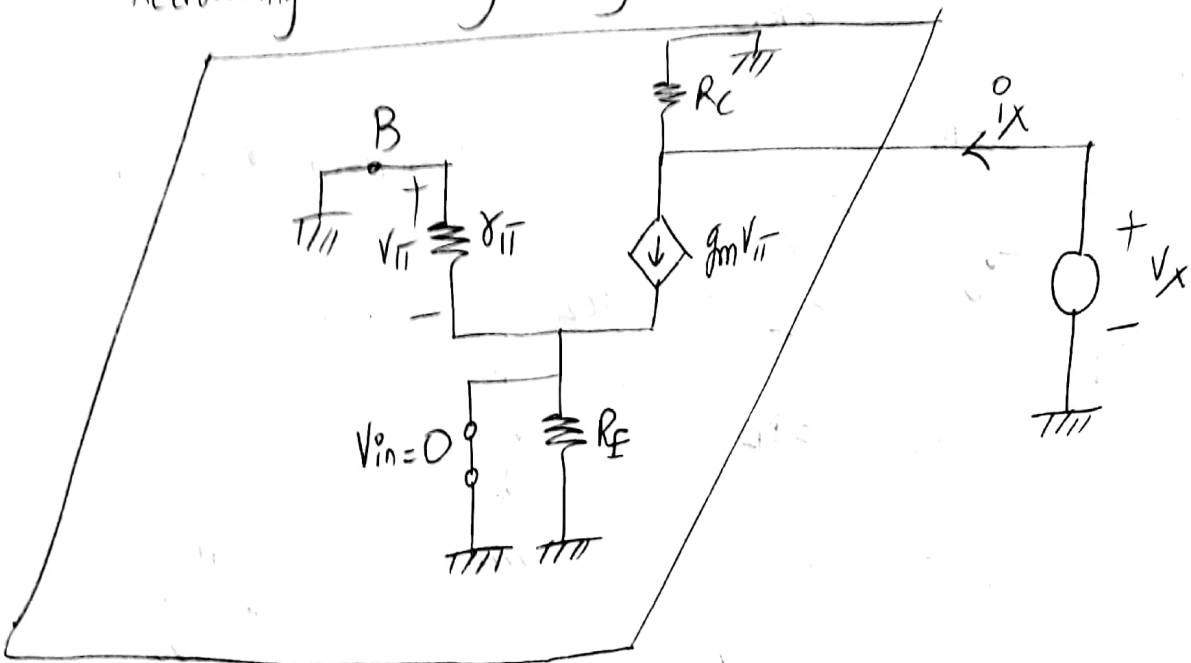

Since,  $V_{in} = 0$  &  $V_{\pi} = -V_{in} = 0$

i.e.  $g_m V_{\pi} = 0$  i.e. current source ( $g_m V_{\pi}$ ) is open-circuited


ckt reduces to

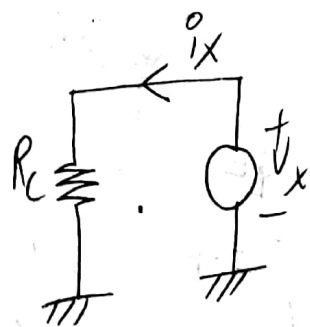

$$Z_o = \frac{V_x}{i_x} = R_c$$


--- O/P impedance

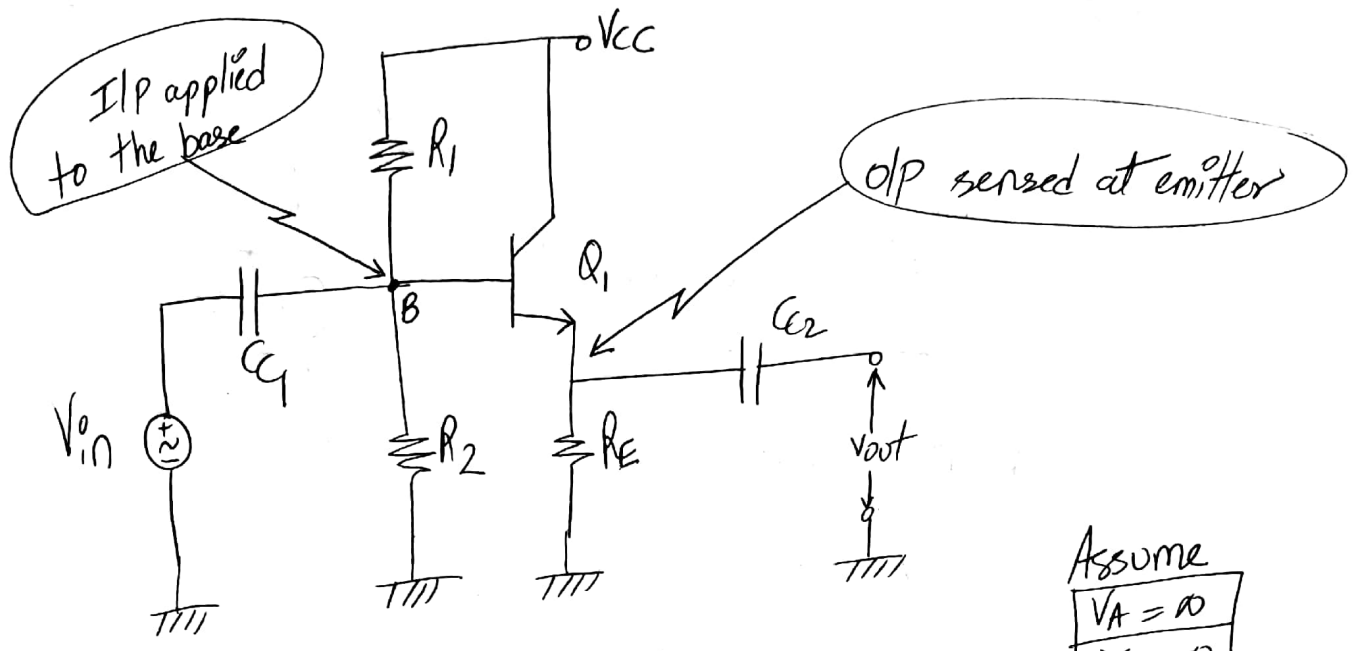\* Common-collector amplifier (npn BJT)  
(Emitter follower)



Assume  
 $V_A = \infty$   
 $\beta \gg 1 = \infty$

Small-signal voltage gain:  $A_v$

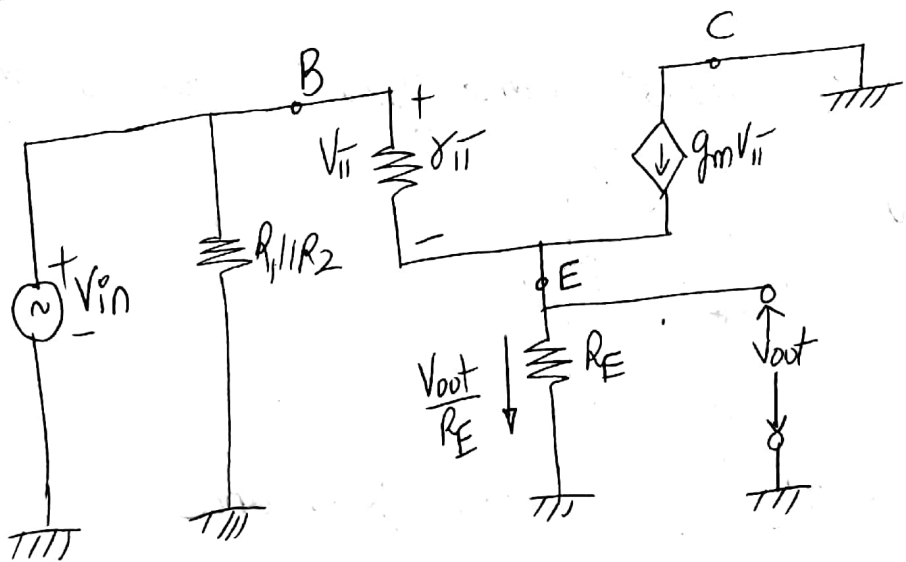

circuit (c): Small-signal equivalent ckt of CC amplifier

From circuit (c), apply KVL to B-E loop,

$$V_{in} = V_{ii} + V_{out} \quad \text{ie} \quad \boxed{V_{ii} = V_{in} - V_{out}} \quad \text{--- (1)}$$



KCL at 'E' node, gives

$$\frac{V_{ii}}{\delta_{ii}} + g_m V_{ii} = \frac{V_{out}}{R_E}$$

$$\frac{V_{in} - V_{out}}{\delta_{ii}} + g_m (V_{in} - V_{out}) = \frac{V_{out}}{R_E} \quad (\text{From (1)})$$

$$\frac{V_{in}}{\delta_{ii}} + g_m V_{in} = \frac{V_{out}}{R_E} + g_m V_{out} + \frac{V_{out}}{\delta_{ii}}$$

$$V_{in} \left( \frac{1}{\delta_{ii}} + g_m \right) = V_{out} \left[ \frac{\delta_{ii} + g_m \delta_{ii} R_E + R_E}{\delta_{ii} R_E} \right]$$

$$V_{in} \left( \frac{1 + g_m \delta_{ii}}{\delta_{ii}} \right) = V_{out} \left[ \frac{\delta_{ii} + g_m \delta_{ii} R_E + R_E}{\delta_{ii} R_E} \right]$$

But,  $g_m \delta_{ii} = \beta$

$$V_{in} (1 + \beta) = V_{out} \left[ \frac{\delta_{ii} + (1 + \beta) R_E}{R_E} \right]$$

$$\frac{V_{out}}{V_{in}} = \frac{R_E (1 + \beta)}{\delta_{ii} + (1 + \beta) R_E}$$

∴ & x Nr & Dr by (1+β)

$$\frac{V_{out}}{V_{in}} = \frac{R_E}{\frac{\delta_{ii}}{(1 + \beta)} + R_E}$$

$$\frac{\delta_{ii}}{1 + \beta} \approx \frac{\delta_{ii}}{\beta} = \frac{1}{g_m}$$

$$i.e. \frac{V_{out}}{V_{in}} = \frac{R_E}{\frac{1}{g_m} + R_E} = A_v$$

34

let's verbalize the gain formula,

$$A_v = \frac{\text{Resistance tied betn Emitter \& ac ground}}{\frac{1}{g_m} + \text{resistance tied betn Emitter \& ac gnd}}$$

$$A_v = \frac{g_m R_E}{1 + g_m R_E}$$

is always very close to 1, but always less than unity



i.e.  $A_v \leq 1$  for a CC amplifier or emitter follower

→ There is no phase difference betn the i/p & o/p signals in an emitter follower.

→ In this amplifier, i/p signal changes in the base follows the changes in the emitter. Hence, the name of circuit is "emitter follower".

ILP impedance :  $Z_i^o$

Redrawing ckt(c),

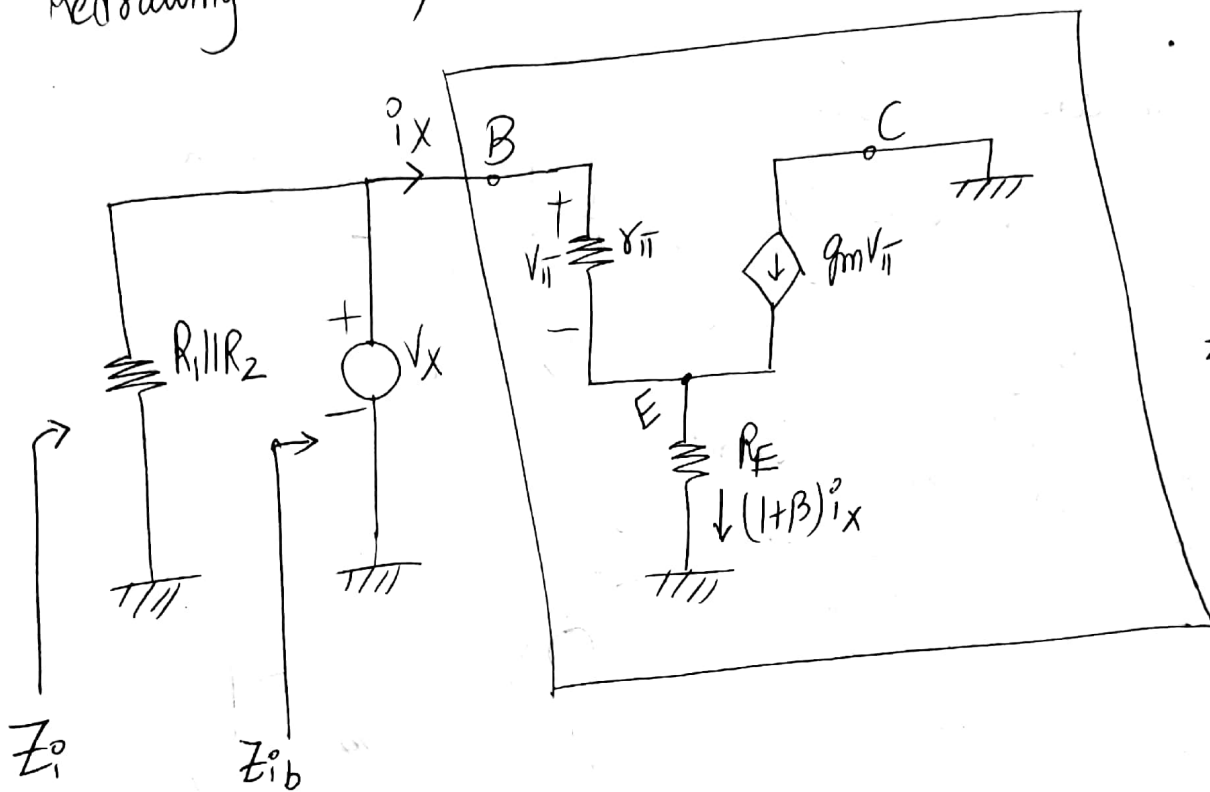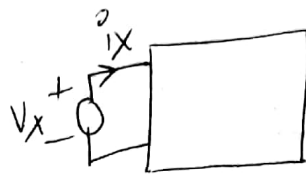

$$Z_{i_b}^o = \frac{V_x}{i_x}$$

From ckt,  $V_{BE} = i_x r_{BE}$

i.e.  $g_m V_{BE} = g_m i_x r_{BE}$

Current through 'B' is  $i_x$

Current through 'E' is  $(1+\beta) i_x$

KVL at B-E loop, gives

$$V_x = V_{BE} + \text{voltage drop across } R_E$$

$$V_x = i_x r_{BE} + (1+\beta) i_x R_E$$

$$Z_{i_b}^o = \frac{V_x}{i_x} = r_{BE} + (1+\beta) R_E$$



$$Z_o = R_1 \parallel R_2 \parallel [\gamma_{ii} + (1+\beta)R_E]$$

high  $i/p$  impedance  
in CC amplifier

36

\* Output impedance :  $Z_o$

Redrawing ckt(c) with  $V_{in}=0$

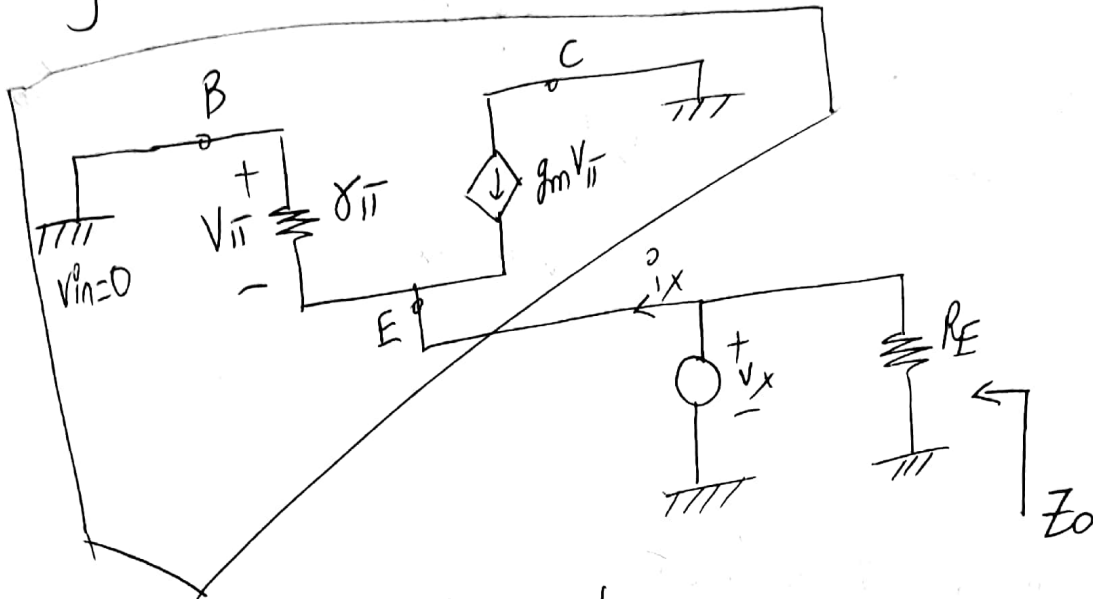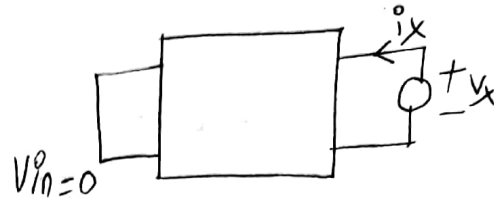

From above ckt,  $V_{ii} = -V_x$

KCL at 'E' node gives,

$$\frac{V_{ii}}{r_{ii}} + g_m V_{ii} + i_x = 0$$

$$-\frac{V_x}{r_{ii}} - g_m V_x = -i_x$$

$$V_x \left( \frac{1}{r_{ii}} + g_m \right) = i_x$$

$$i_x^o = V_x \left( \frac{g_m r_{ii} + 1}{r_{ii}} \right)$$

$$g_m r_{ii} = \beta$$

$$i_x^o = V_x \left( \frac{1 + \beta}{r_{ii}} \right)$$

$$1 + \beta \approx \beta$$

$$i_x^o = V_x \left( \frac{\beta}{r_{ii}} \right)$$

$$\frac{\beta}{r_{ii}} = g_m$$


$$i_x^o = V_x g_m$$

$$\frac{V_x}{i_x^o} = \frac{1}{g_m}$$

$$\therefore Z_o = R_E \parallel \frac{1}{g_m} \quad \text{low output impedance}$$

Application of CC amplifiers :-

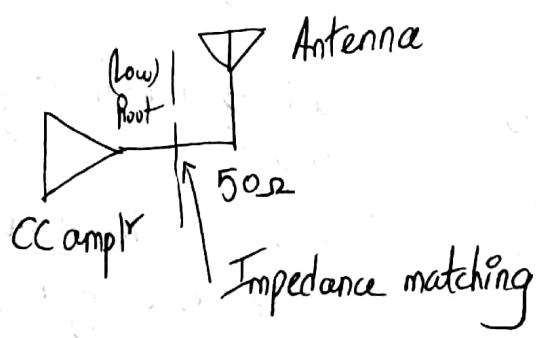- It is used as a buffer betw amplr and o/p stage
- It is used to drive a low impedance antenna or speakers



# Comparison of CE, CB and CC amplifiers


	Common-emitter	Common-base	Common-collector
1. Circuit			
2. I/P applied to	Base terminal	Emitter terminal	Base terminal
3. o/p sensed at	Collector terminal	Collector terminal	Emitter terminal
4. Voltage gain	$A_v = -g_m R_C$ <b>High</b>	$A_v = g_m R_C$ <b>High</b>	$A_v = \frac{g_m R_E}{1 + g_m R_E} \approx 1$ <b>Low</b>
5. I/P impedance	$Z_i = R_1    R_2    r_{\pi}$ <b>Medium</b>	$Z_i = \frac{1}{g_m}    R_E$ <b>Low</b>	$Z_i = R_1    R_2    [r_{\pi} + (1 + \beta) R_E]$ <b>V. High</b>
6. o/p impedance	$Z_o = R_C$ <b>Medium</b>	$Z_o = R_C$ <b>Medium</b>	$Z_o = \frac{1}{g_m}    R_E$ <b>Low</b>
7. Phase of o/p signal	Out. of Phase with i/p signal	In phase with i/p signal	In phase with i/p signal
8. Application	Common used as inverting voltage amplifiers	1) used as non-inverting amplifier 2) used as a ckt which can be driven by a low impedance source	1) used as a voltage buffer 2) used to drive a low impedance load (eg antenna or speaker)

## Numerical 02

39

Determine the following for circuit shown below

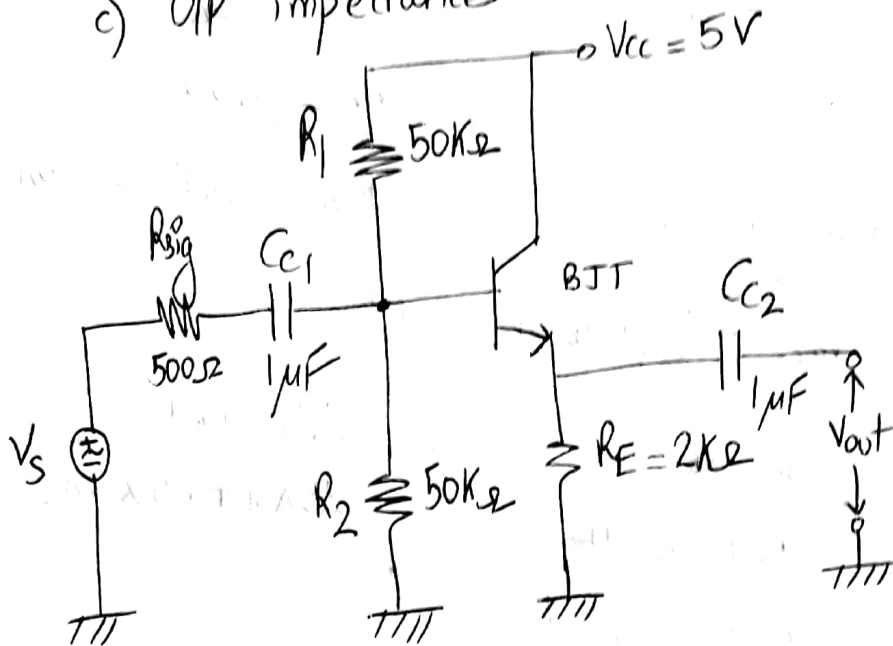
- Small-sig voltage gain
- ILP impedance
- OIP impedance




$$\beta = 100$$
$$V_{BE(on)} = 0.7V$$
$$V_A = 80V$$

Sol<sup>n</sup>:- 1] Above circuit is common collector amplifier using npn BJT

2] DC analysis:-

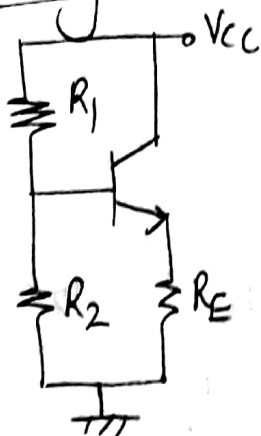

Applying thevenin's equivalent at base,

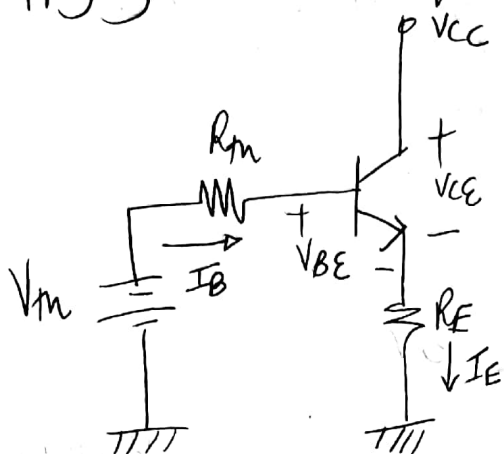

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$= \frac{50K}{100K} \times 5$$

$$V_{th} = 2.5V$$

$$R_{th} = R_1 \parallel R_2 = 25K\Omega$$

KVL to B-E loop gives,

$$V_{th} - I_B R_{th} - V_{BE} - (1 + \beta) I_B R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = \frac{2.5 - 0.7}{25K\Omega + 101 \times 2K\Omega}$$

$$I_{BQ} = 7.93 \mu A$$

$$\therefore I_{CQ} = \beta I_{BQ} = 100 \times 7.93 \times 10^{-6}$$

$$I_{CQ} = 0.793 \text{ mA}$$

$$I_E = I_B + I_C = 0.8 \text{ mA}$$

KVL to C-E loop gives,

$$V_{CC} - V_{CE} - I_E R_E = 0$$

$$V_{CEQ} = V_{CC} - I_E R_E = 5 - 0.8 \times 10^{-3} \times 2K\Omega$$

$$V_{CEQ} = 3.398 \text{ V}$$




3] Small-signal model parameters:-

a)  $r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{V_T}{I_{BQ}} = \frac{26mV}{7.93\mu A} = \underline{3.279 K\Omega}$

b)  $g_m = \frac{I_{CQ}}{V_T} = \frac{0.793 mA}{26 mV} = \underline{30.5 \frac{mA}{V}}$

c)  $r_o = \frac{V_A}{I_{CQ}} = \frac{80}{0.793 mA} = \underline{100.88 K\Omega}$

4] Small-signal equivalent circuit:-

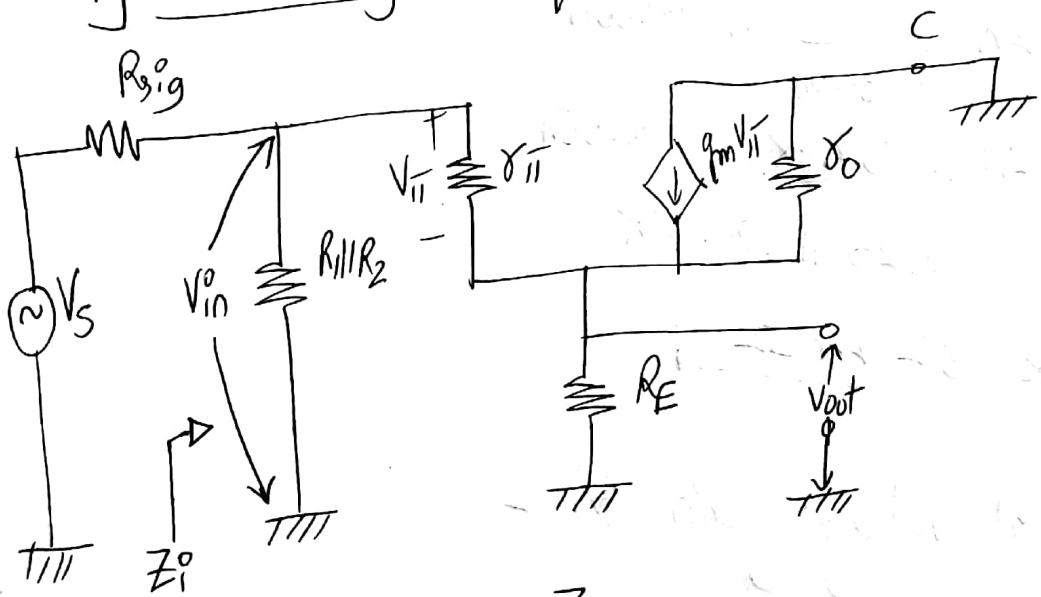

a) I/P impedance:  $Z_i$

$$Z_i = R_1 || R_2 || [\ r_{\pi} + (1+\beta)(R_E || r_o)\ ]$$

$$r_o || R_E = 100.88K || 2K\Omega = 1.96K\Omega$$

$$r_{\pi} + (1+\beta)(r_o || R_E) = 201.24K\Omega$$

$$\begin{aligned}
 Z_o &= R_1 \parallel R_2 \parallel 201.24K \\
 &= 50K \parallel 50K \parallel 201.24K \\
 &= 25K \parallel 201.24K\Omega
 \end{aligned}$$

$$\boxed{Z_o = 22.24K\Omega}$$

b) Output resistance:  $Z_o$

$$Z_o \approx R_E \parallel \frac{1}{g_m} \parallel r_o$$

$$= 2K \parallel \frac{1}{30.5m} \parallel 100.88K$$

$$= 2K \parallel 32.78 \parallel 100.88K$$

$$= 32.25 \parallel 100.88K$$

$$\boxed{Z_o \approx 32.24\Omega}$$

c) Small-signal voltage gain ( $A_v$ ):-

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_{in}} \frac{V_{in}}{V_s} = A_v \times \frac{V_{in}}{V_s}$$

$$A_v = \frac{R_E \parallel r_o}{\frac{1}{g_m} + (R_E \parallel r_o)}$$

$$A_v = \frac{R_{E||r_o}}{1 + R_{E||r_o} g_m}$$

$$R_{E||r_o} = 2K \parallel 100.88K = 1.96K\Omega$$

$$\frac{1}{g_m} = \frac{1}{\frac{30.5mA}{V}} = 32.78$$

$$\therefore A_v = \frac{1.96K\Omega}{32.78 + 1.96K\Omega} \approx \underline{0.9835}$$

$$A_{v_s} = A_v \times \frac{V_{in}}{V_s}$$

$$\frac{V_{in}}{V_s} = \frac{Z_i}{Z_i + R_{s_{sig}}} = \frac{22.24K\Omega}{22.24K + 500} = 0.978$$

$$\therefore A_{v_s} = \frac{V_o}{V_s}$$

$$= 0.9835 \times 0.978$$


$$\boxed{A_{v_s} = +0.962}$$

----- Small-signal voltage gain of CC amplifier

# Numerical 03:

Determine the following for circuit below:-


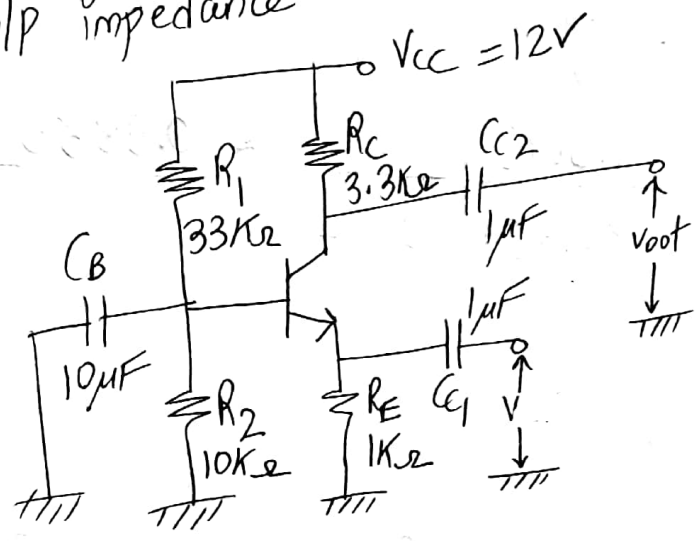
- a) Small-signal voltage gain
- b) I/P impedance
- c) O/P impedance



$\beta = 99$   
 $V_{BE(on)} = 0.7V$   
 $V_A = \infty$

Sol<sup>n</sup>:- 1] Above circuit is common base amplifier using npn BJT

2] DC Analysis:-

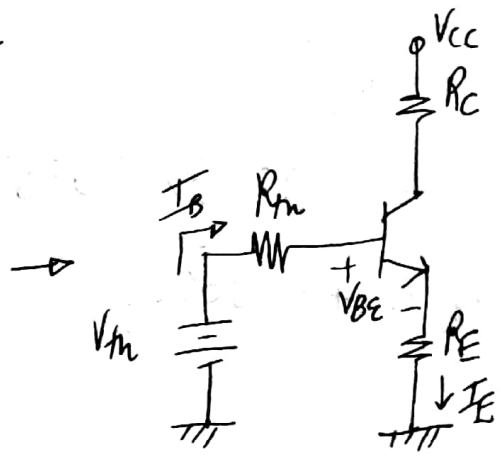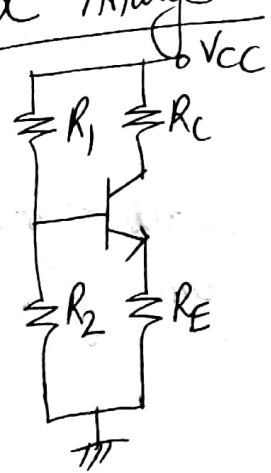

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{cc}$$

$$= 2.79V$$

$$R_{th} = R_1 \parallel R_2$$

$$= 7.67K\Omega$$

KVL to B-E loop gives,

$$V_{th} - I_B R_{th} - V_{BE} - I_B (1+\beta) R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE(ov)}}{R_{th} + (1+\beta) R_E} = \frac{2.79 - 0.7}{7.67K\Omega + 100 \times 1K\Omega}$$

$$I_{BQ} = 19.41 \mu A$$

$$I_{CQ} = \beta I_{BQ} = 99 \times 19.41 \mu A$$

$$I_{CQ} = 1.92 \text{ mA}$$

$$I_E = I_C + I_B = 1.94 \text{ mA}$$

3) Small-signal parameters:-


a)  $r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{26 \text{ mV}}{19.41 \mu A} = 1.34 \text{ K}\Omega$

b)  $g_m = \frac{I_{CQ}}{V_T} = \frac{1.92 \text{ mA}}{26 \text{ mV}} = 73.85 \frac{\text{mA}}{\text{V}}$

c)  $r_o = \frac{V_A}{I_{CQ}} = \infty$

4] Small-signal equivalent circuit :-

46

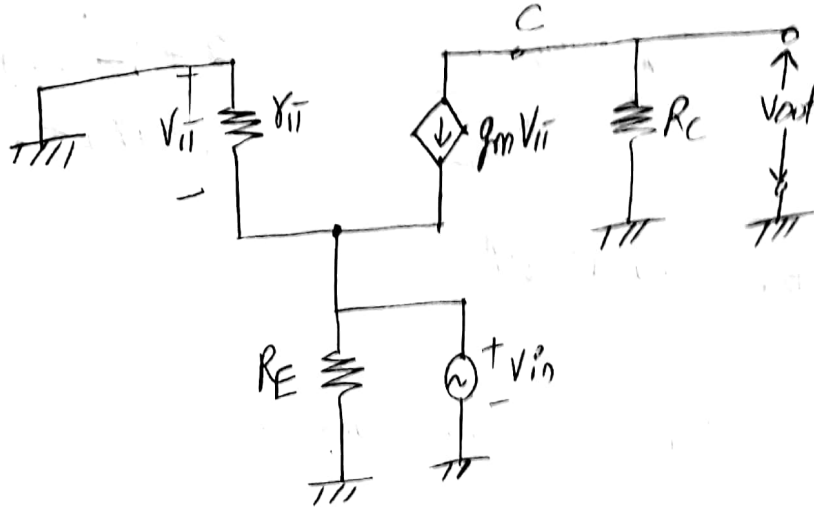

a) Small-signal voltage gain:  $A_v$

$$A_v = \frac{V_o}{V_{in}} = g_m R_C$$

$$A_v = 73.85 \times 10^{-3} \times 3.3 \text{ K}\Omega$$

$$\boxed{A_v = 243.69}$$

b) Input impedance:  $Z_i$

$$Z_i = \frac{1}{g_m} \parallel R_E = \frac{1}{73.85 \times 10^{-3}} \parallel 1 \text{ K}\Omega = 13.54 \parallel 1 \text{ K}\Omega$$

$$\boxed{Z_i = 13.36 \Omega}$$

c) Output impedance:  $Z_o$

$$\boxed{Z_o = R_C} \Rightarrow \text{pe } \boxed{Z_o = 3.3 \text{ K}\Omega}$$