

Dwarkadas. J. Sanghvi College of Engineering
Department of Electronics Engineering

Experiment no: 05

Aim: Simulation of single ended differential sense amplifier.

Apparatus: PC loaded with LT spice software.

Theory: A **differential amplifier** is a type of electronic amplifier that amplifies the difference between two voltages but does not amplify the particular voltages. The output of an ideal differential amplifier is given by:

$$V_{out} = A_d(V_{in}^+ - V_{in}^-)$$

Where V_{in}^+ and V_{in}^- are the input voltages and A_d is the differential gain.

Differential amplifiers are often used to null out noise or bias-voltages that appear at both inputs. The signals common to both the inputs are suppressed at the o/p of amplifier by a ratio called as CMRR. Spikes on the power supply are suppressed by PSRR ratio. This differential approach is directly applicable to SRAM memories, as these are the only memory cells that offer a true differential output.

Figure (a) shows the most basic differential sense amplifier. It is a differential voltage amplifier with a current mirror load. The inputs are fed to the differential i/p terminals M1 & M2 and M3 & M4 acts as an active current mirror load.

There is a current sink ISS which is a constant current sink. The current through this would be always constant and hence the Sum of i_{D1} and i_{D2} would be always constant i.e. $ISS = i_{D1} + i_{D2}$. To keep ISS constant in this circuit, if there is a decrease in one of the branch current the other branch current increases.

When a differential input is applied (bit and bit' lines), let's assume the higher voltage is applied to the transistor M1 gate and the compliment is on the M2 gate. In this case the current through M1, that is i_{D1} increases and the current i_{D2} decreases. Since $i_{D1} = i_{D3}$ the current mirror draws the same current as i_{D1} , which results in a mirrored current $i_{D4} = i_{D3} = i_{D1}$.

Also notice that ISS needs to be constant and hence whenever i_{D1} decreases i_{D2} will increase. Thus the voltage difference is transferred in to a current difference and this current is amplified at the output and again this is converted as a voltage at the output. The ISS keeps the current always constant and because of this it brings one of the transistors to higher saturation by drawing more current through that branch when the other branch supplies reduced current.

As shown in fig. (b) When the inputs are same on bit and bit' lines, $i_{D1} = i_{D2}$ & differential i/p is zero. For positive diff. i/p $i_{D1} > i_{D2}$ & for negative diff. i/p $i_{D2} > i_{D1}$.

Circuit Diagram:

 


Fig a : single ended differential sense amplifier

 


Fig b : Current waveforms

Procedure:

Design Simulation

1. Draw the circuit using LT spice software.
2. Apply $V_{DD} = 12V$, $I_{SS} = 5mA$ dc and $V_{g1} = 1V$ peak-to-peak / 1KHz and $V_{g2} = 0V$.
3. Run the simulation and observe the output waveforms.

Conclusion:

Attach the printouts of circuit diagram and waveform.