 


# Data Path Design

# Contents

- Adder
  - Bit adder circuits
  - Ripple Carry Adder
  - CLA Adder
- Multipliers and Shifter
  - Partial-product generation
  - Partial-product accumulation
  - Final addition
  - Barrel shifter

# A Generic Digital Processor



# Building Blocks for Digital Architectures

## ❑ Arithmetic unit

- Bit sliced data path – adder, multiplier, shifter, comparator, etc.

## ❑ Memory

- RAM, ROM, buffers, shift registers


## ❑ Control

- Finite state machine (PLA, random logic)
- Counters

## ❑ Interconnect

- Switches, arbiters, bus

# Bit-Sliced Design

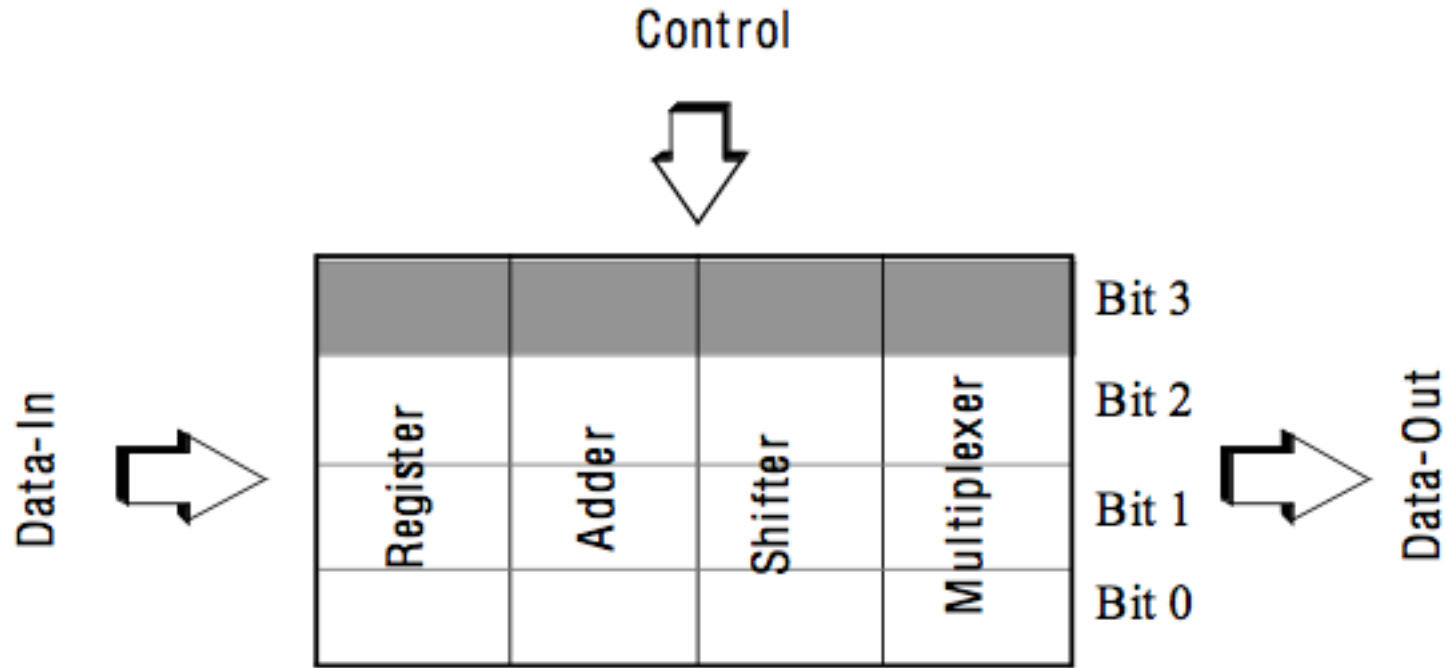

Tile identical processing elements

# Bit Adder Circuits

- Consider two binary digits A and B, binary sum is denoted by  $A+B$  such that


$$0+0=0$$

$$0+1=1$$

$$1+0=1$$

$$1+1=10$$


Half adder

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$Sum = A \oplus B$$

$$Carry = A \cdot B$$

 

# Full-Adder

 


$$\text{sum\_out} = A \oplus B \oplus C$$


$$= ABC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{C}B$$

$$\text{carry\_out} = AB + AC + BC$$

## AOI Full-Adder Logic

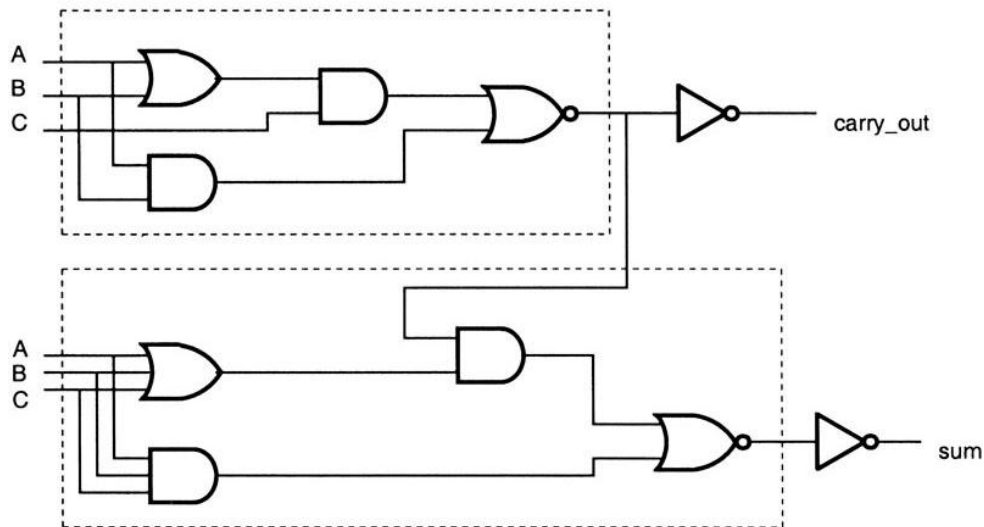
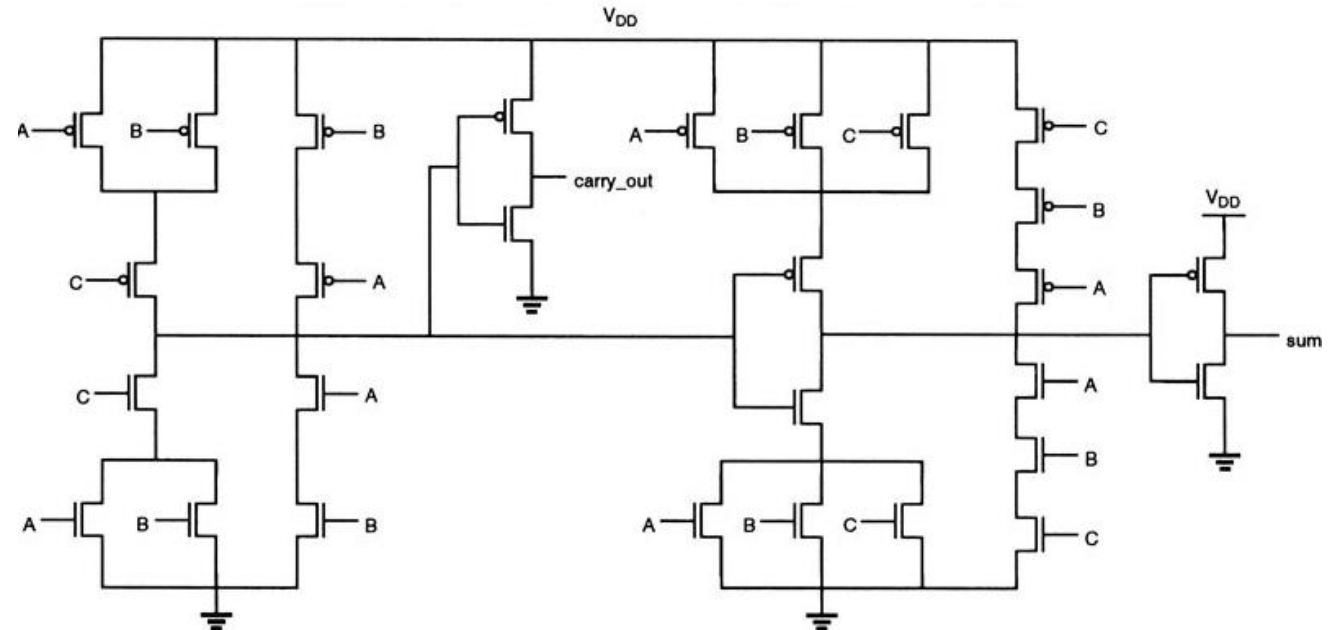
## Transistor-level schematic of the one-bit full-adder circuit



# Full-Adder Circuits

- Adding  $n$ -bit binary words

$$\begin{array}{r} a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline c_4 \ s_3 s_2 s_1 s_0 \end{array} \quad (12.3)$$

- In the standard carry algorithm, each of the  $i$ -th columns ( $i = 0, 1, 2, 3$ ) operates according to the full-adder equation

$$\begin{array}{r} c_i \\ a_i \\ + b_i \\ \hline c_{i+1} \ s_i \end{array} \quad (12.4)$$


- Expressions for the network are

$$s_i = a_i \oplus b_i \oplus c_i \quad (12.5)$$


$$c_{i+1} = a_i \cdot b_i + c_i \cdot (a_i \oplus b_i)$$

or
 
$$c_{i+1} = a_i b_i + c_i \cdot (a_i + b_i) \quad (12.6)$$




(a) NAND2 logic

 


(b) NOR-based network



# Full-adder logic networks

 

(a) Gate-level logic

 

(b) HA-based design

Full-adder logic networks

# Full-adder truth-table

$A$	$B$	$C_i$	$S$	$C_o$	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate


$$\text{Generate } (G) = AB$$

$$\text{Propagate } (P) = A \oplus B$$

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$


# Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$
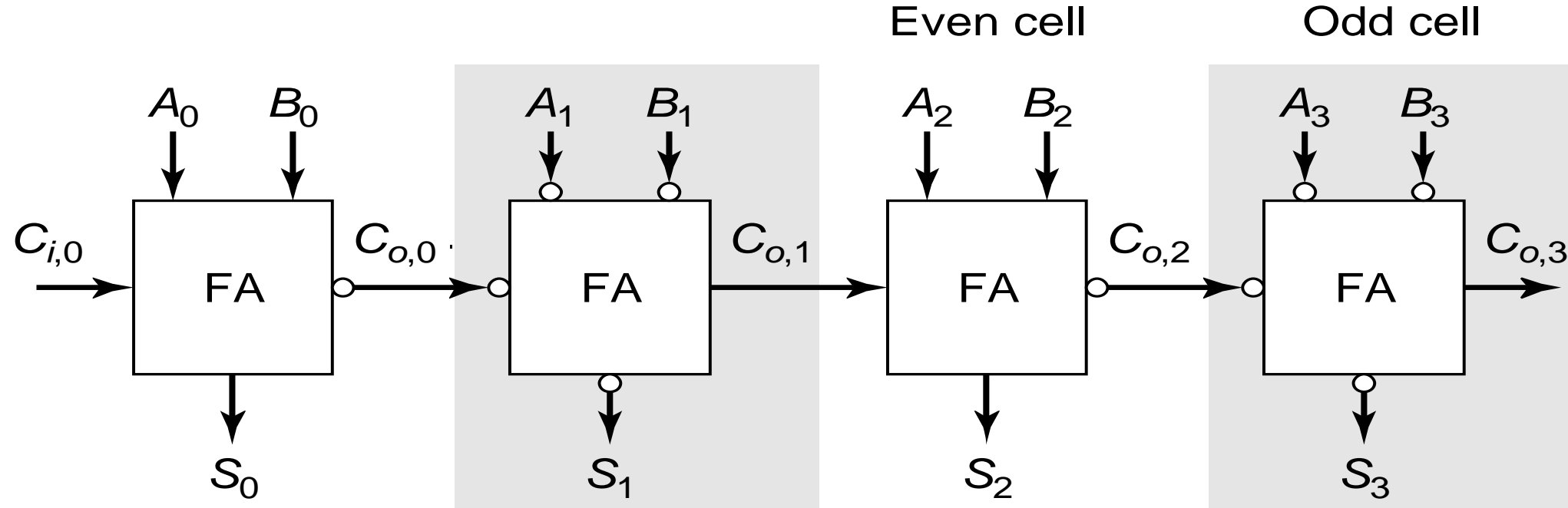
# Minimize Critical Path by Reducing Inverting Stages



**Exploit Inversion Property**

# Mirror Circuits

- ❑ Mirror circuits are based on series-parallel logic gates, but are usually faster and have a more uniform layout
  - » Output 0's imply that an nFET chain is conducting to ground
  - » Output 1's means that a pFET group provides support from the power supply



$a$	$b$	$a \oplus b$	On devices
0	0	0	← nFET
0	1	1	← pFET
1	0	1	← pFET
1	1	0	← nFET


 



Figure 9.1 XOR function table
 
# Mirror Circuits


- ❑ Based on series-parallel logic gates
- ❑ Usually faster, more uniform layout
- ❑ Same transistor topology for nFETs and pFETs



# Evolution of carry-out circuit

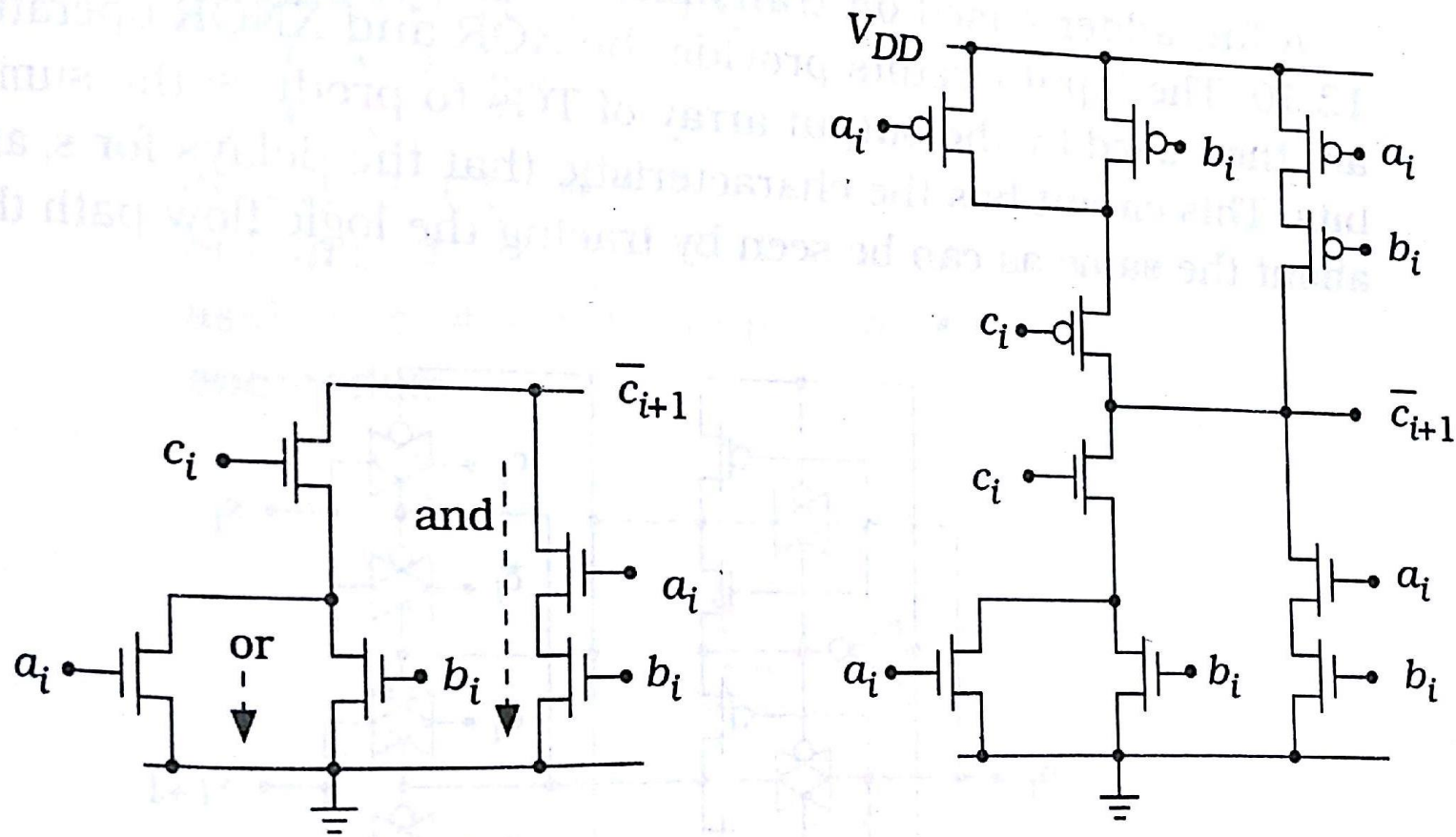


# A Better Structure: The Mirror Adder

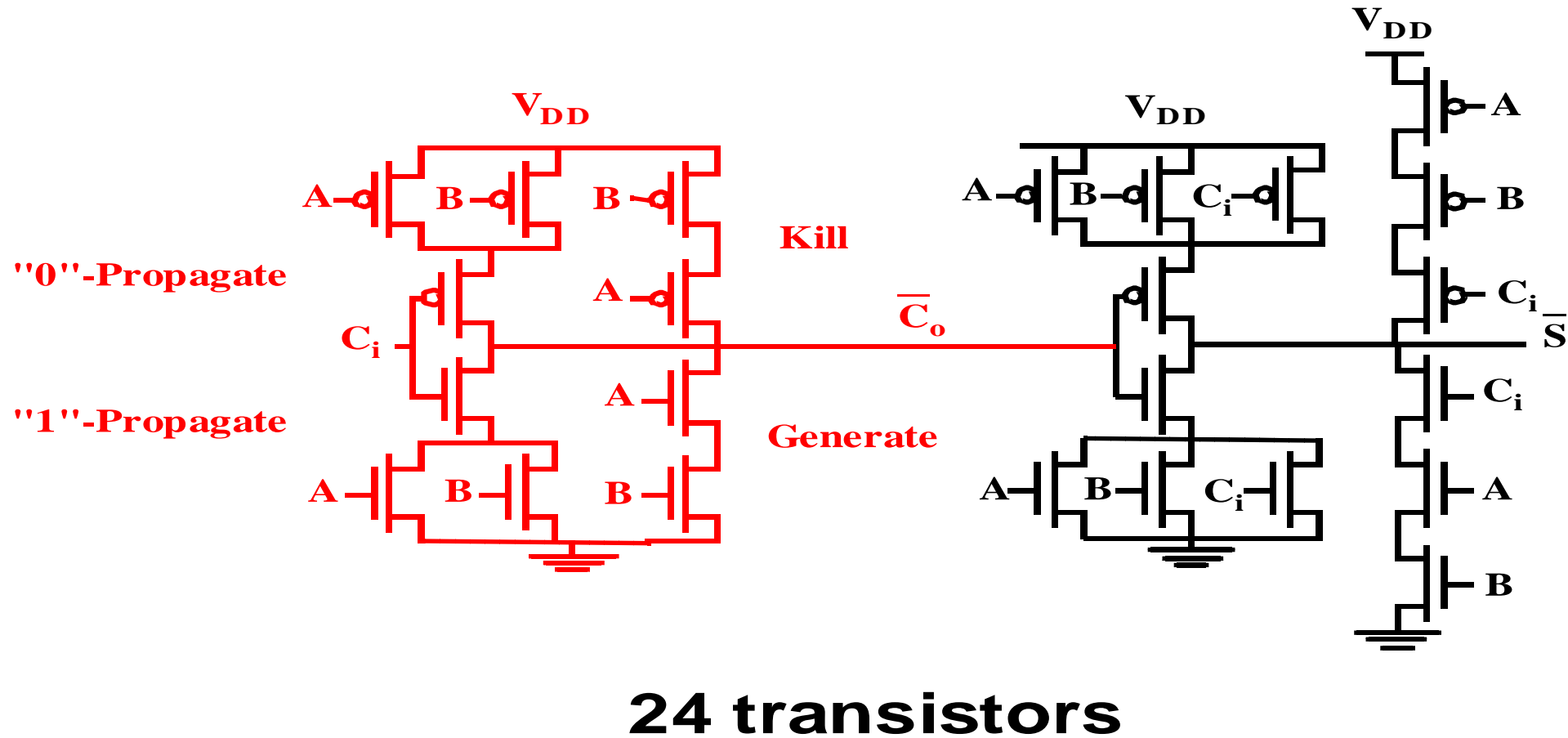



# Transmission-gate full-adder circuit

 

# Complementary Pass-Transistor Logic

- Complementary Pass-Transistor (CPL): an dual-rail tech. that is based on nFET logic equations

$$f = a \cdot b + \bar{a} \cdot \bar{b} \quad (9.41)$$

$$\Rightarrow a \cdot \bar{b} + \bar{a} \cdot b = \bar{a} + \bar{b} = \overline{a \cdot b} \quad (9.42)$$

- CPL has several 2-input gates that can be created by using the same transistor topology with different input sequences
  - » Less layout area
  - » However, threshold will be loss and the fact that an input variable may have to drive more than one FET terminal

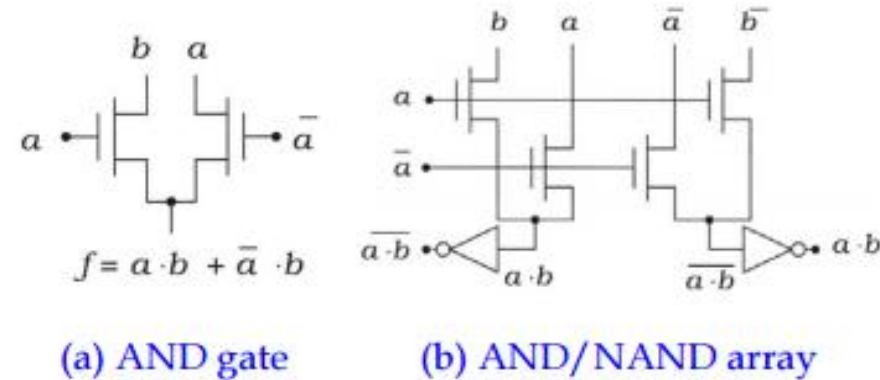


Figure 9.32 CPL AND/NAND circuit

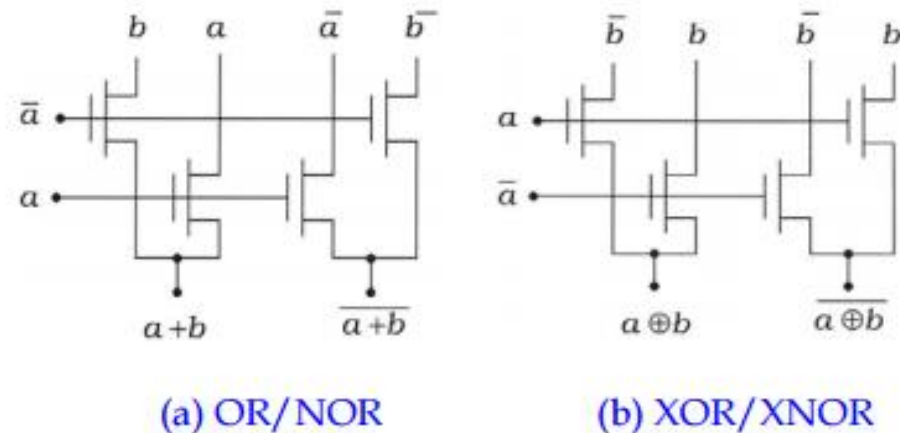


Figure 9.33 2-input CPL arrays

# Complementary Pass-Transistor Logic

## □ Dual-rail complementary pass-transistor logic (CPL)

$$a_i \oplus b_i \text{ and } \overline{a_i \oplus b_i}$$


$$s_n = \overline{(a_i \oplus b_i)} \cdot c_i + (a_i \oplus b_i) \cdot \overline{c_i}$$

$$\overline{a_i} \cdot b_i + \overline{b_i} \cdot \overline{c_i}$$


$$\overline{b_i} \cdot c_i + a_i \cdot b_i$$

$$\overline{a_i} \cdot \overline{b_i} + b_i \cdot \overline{c_i}$$

 
$$b_i \cdot c_i + a_i \cdot \overline{b_i}$$



(a) 2-input array

 


(b) Sum circuit

 


(c) Carry circuit

# Full Adder using Half Adders

 
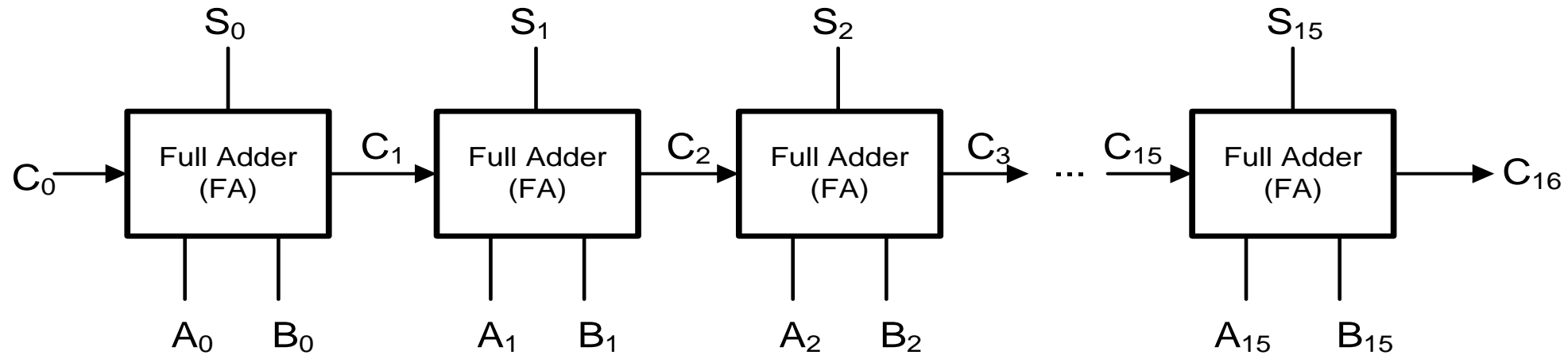
# Ripple Carry Adders

- A carry ripple adder chain : 16-bit binary adder



- Cascade-connection
- Fast carry-out response is essential
- the delay will increase significantly when the number of bit is increased

# Ripple-Carry Adders

 


Figure 12.11 An n-bit adder

 


Figure 12.13 Worst-case delay through the 4-bit ripple adder

 


Figure 12.12 A 4-bit ripple-carry adder

 


Figure 12.14 4-bit adder-subtractor circuit

# Carry Look-Ahead Adder

 


Figure 12.15 Basis of the carry look-ahead algorithm

 


Figure 12.16 Logic network for 4-bit CLA carry bits



 


Figure 12.17 Sum calculation using the CLA network

# Carry Look-Ahead Adders

 

(a) Series-parallel circuit

 

(b) Mirror equivalent

Figure 12.20 Static CLA mirror circuit

 


Figure 12.21 Static mirror circuit for  $C_2$

 


Figure 12.22 MODL carry circuit



# Carry Look-Ahead Adders

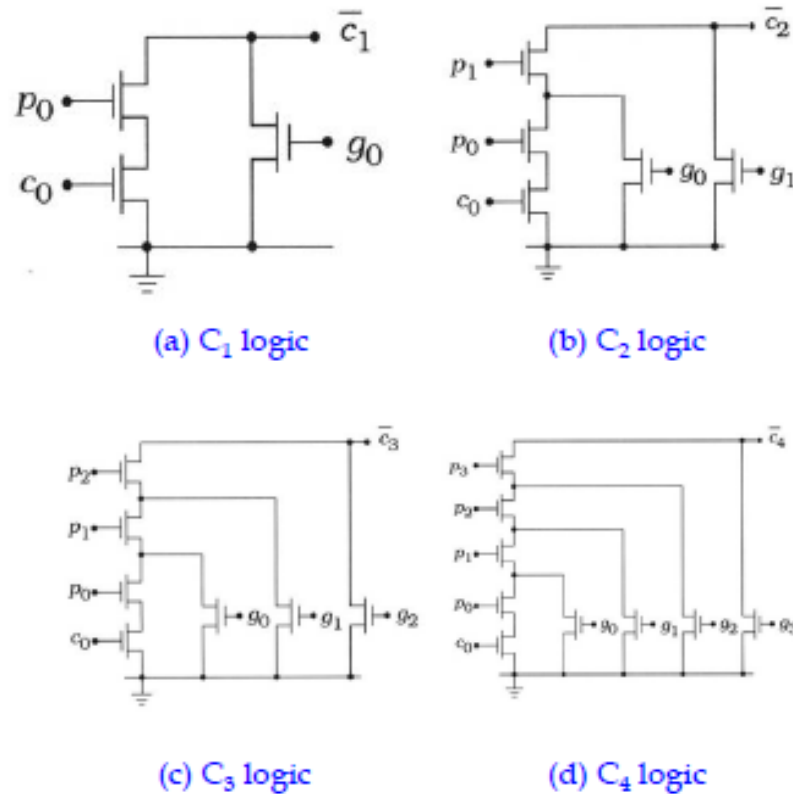


Figure 12.18 nFET logic arrays for the CLA terms

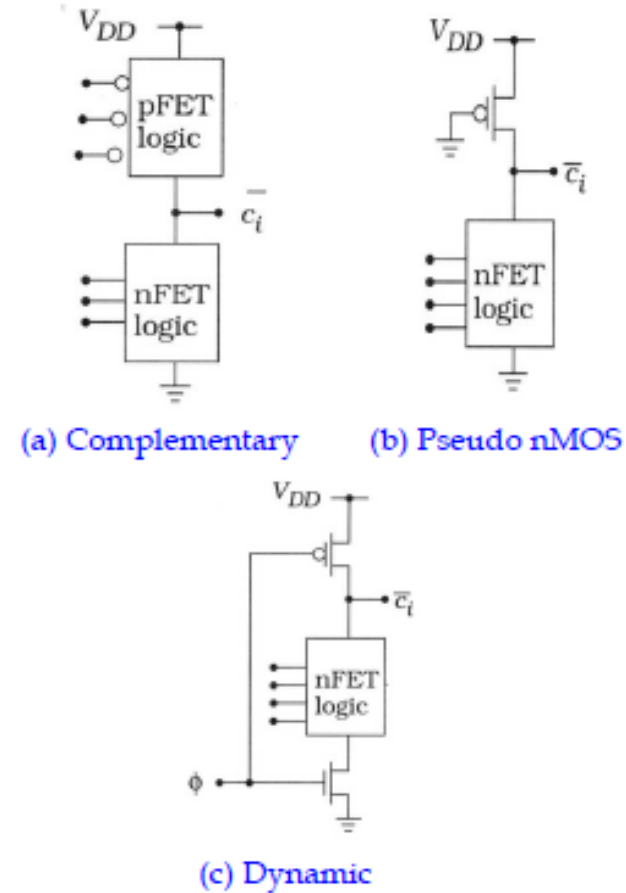


Figure 12.19 Possible uses of the nFET logic arrays in Figure 12.18

# Manchester Carry Chains

$a_i$	$b_i$	$p_i$	$g_i$	$k_i$
0	0	0	0	1
0	1	1	0	0
1	0	1	0	0
1	1	0	1	0

Figure 12.23 Propagate, generate, and carry-kill values



 


Figure 12.24 Switching network for the carry-out equation

 

(a) Static circuit

 

(b) Dynamic circuit

Figure 12.25 Manchester circuit styles

 


Figure 12.26 Dynamic Manchester carry chain

# Multipliers

 


Figure 12.39 Bit-level multiplier

 


Figure 12.40 Multiplication of two 4-bit words

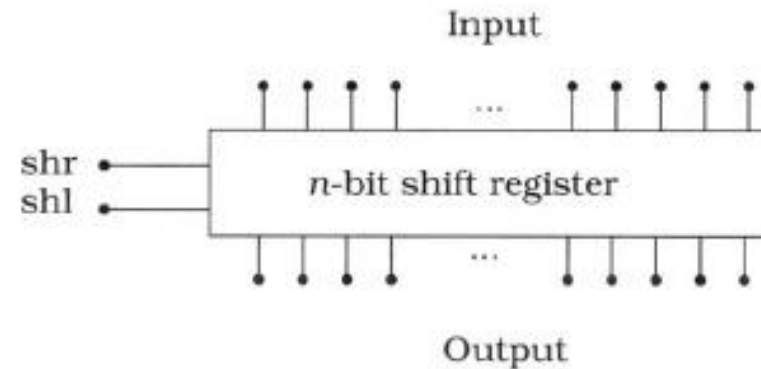


Figure 12.41 Shift register for multiplication or division by a factor of 2

# Binary Multiplication

				1	0	1	0	1	0		Multiplicand
x						1	0	1	1		Multiplier
<hr/>											
				1	0	1	0	1	0		Partial products
			1	0	1	0	1	0			
		0	0	0	0	0	0				
	0	0	0	0	0	0	0				
+	1	0	1	0	1	0					
<hr/>											
	1	1	1	0	0	1	1	1	0		Result

# Multipliers

				$a_3$	$a_2$	$a_1$	$a_0$		
				$\times$	$b_3$	$b_2$	$b_1$	$b_0$	multiplier
				<hr/>					
				$(a_3 \ a_2 \ a_1 \ a_0) \times b_0$				$(a \times b_0) 2^0$	
			$(a_3 \ a_2 \ a_1 \ a_0) \times b_1$					$(a \times b_1) 2^1$	
		$(a_3 \ a_2 \ a_1 \ a_0) \times b_2$						$(a \times b_2) 2^2$	
	$+$	$(a_3 \ a_2 \ a_1 \ a_0) \times b_3$						$(a \times b_3) 2^3$	
<hr/>									
$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$	product	

Figure 12.42 Alternate view of multiplication process


 


Figure 12.43 Using a product register for multiplication

# Partial product generation logic

 

# Shift-right multiplication sequence

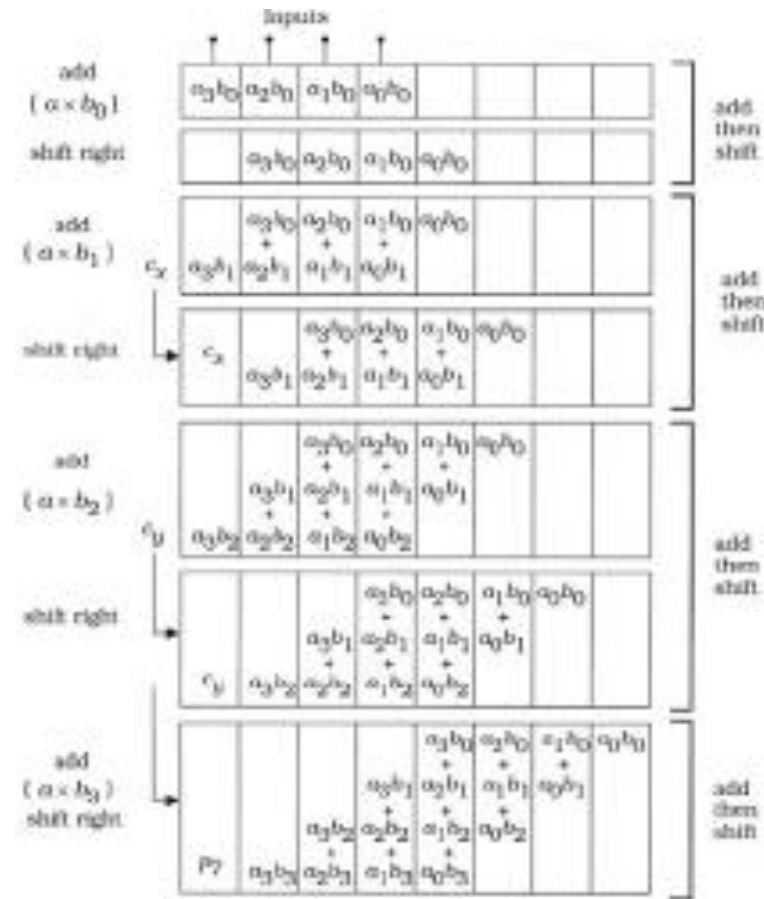


Figure 12.44 Shift-right multiplication sequence

# Register based multiplier network

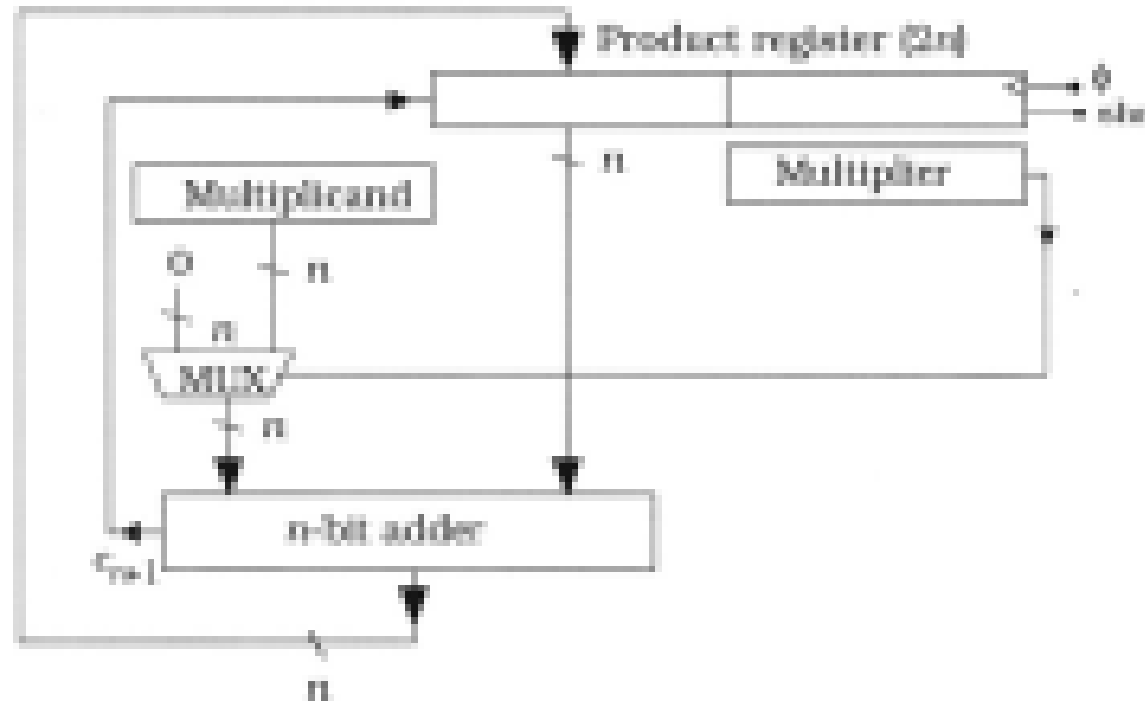


Figure 12.45 Register-based multiplier network



# Partial Product Accumulation- Array Multipliers



Figure 12.46 An array multiplier

 


Figure 12.47 Modularized view of the multiplication sequence



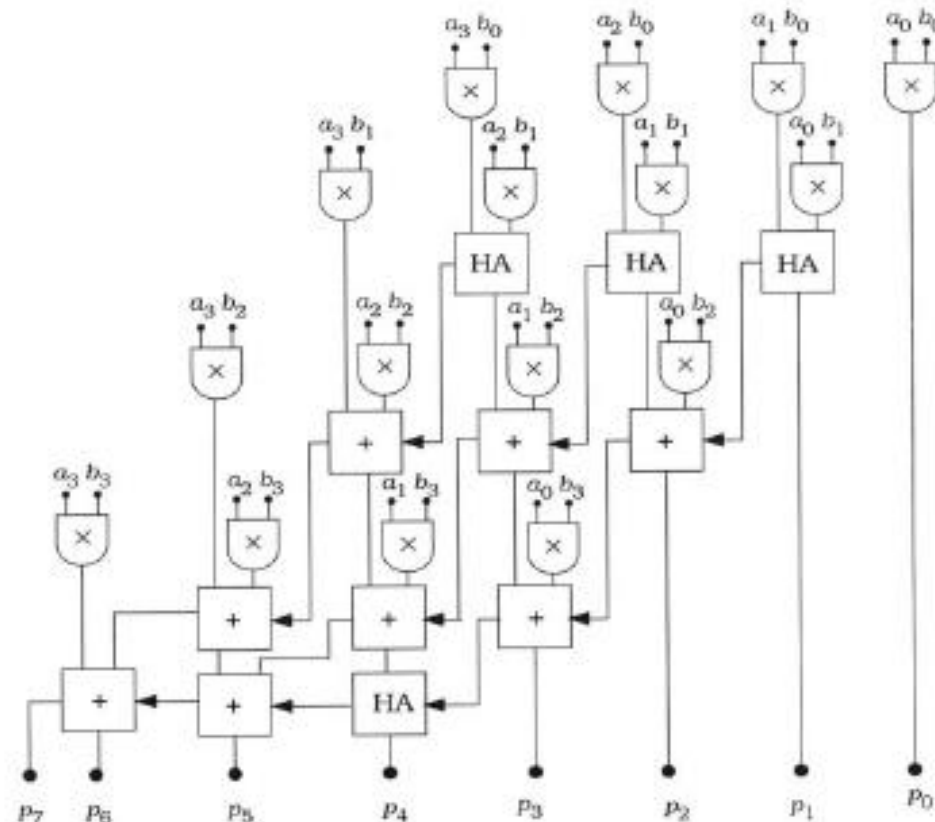


Figure 12.48 Details for a 4 X 4 array multiplier


# General Rotator

 


# 4-bit rotate-right network

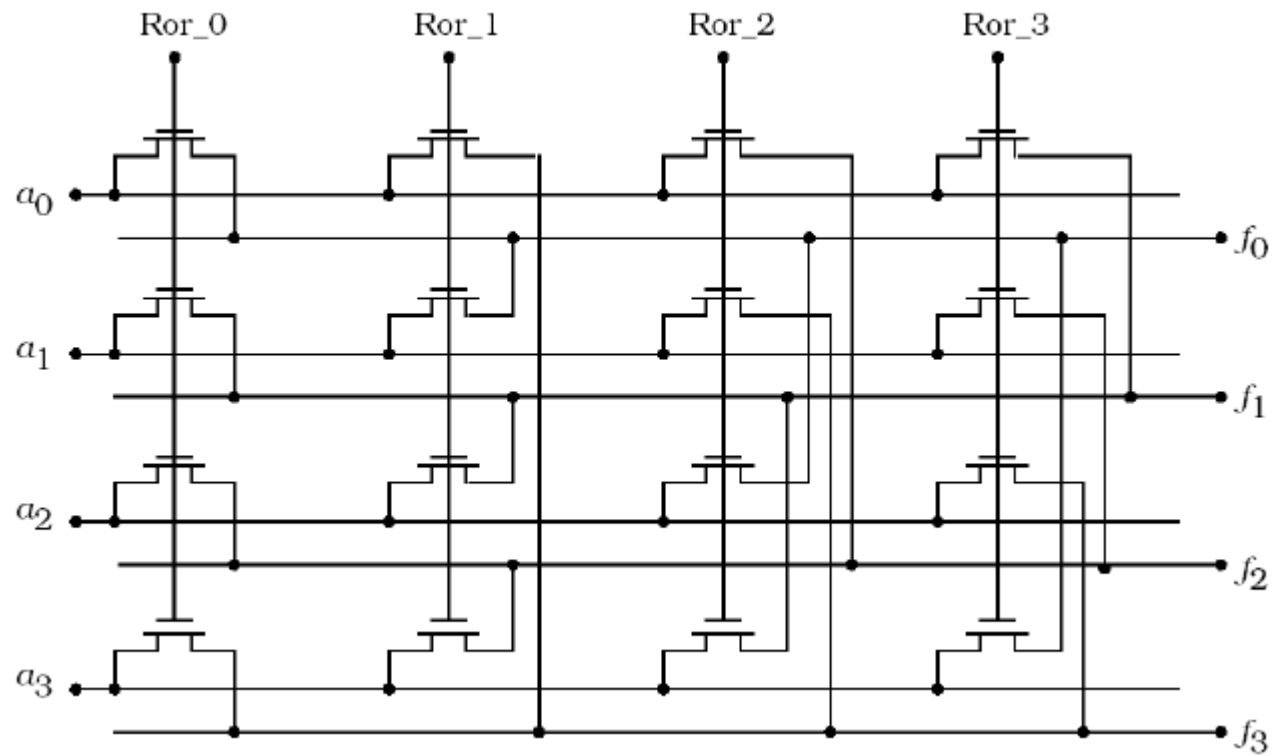

# Left-rotate switching array

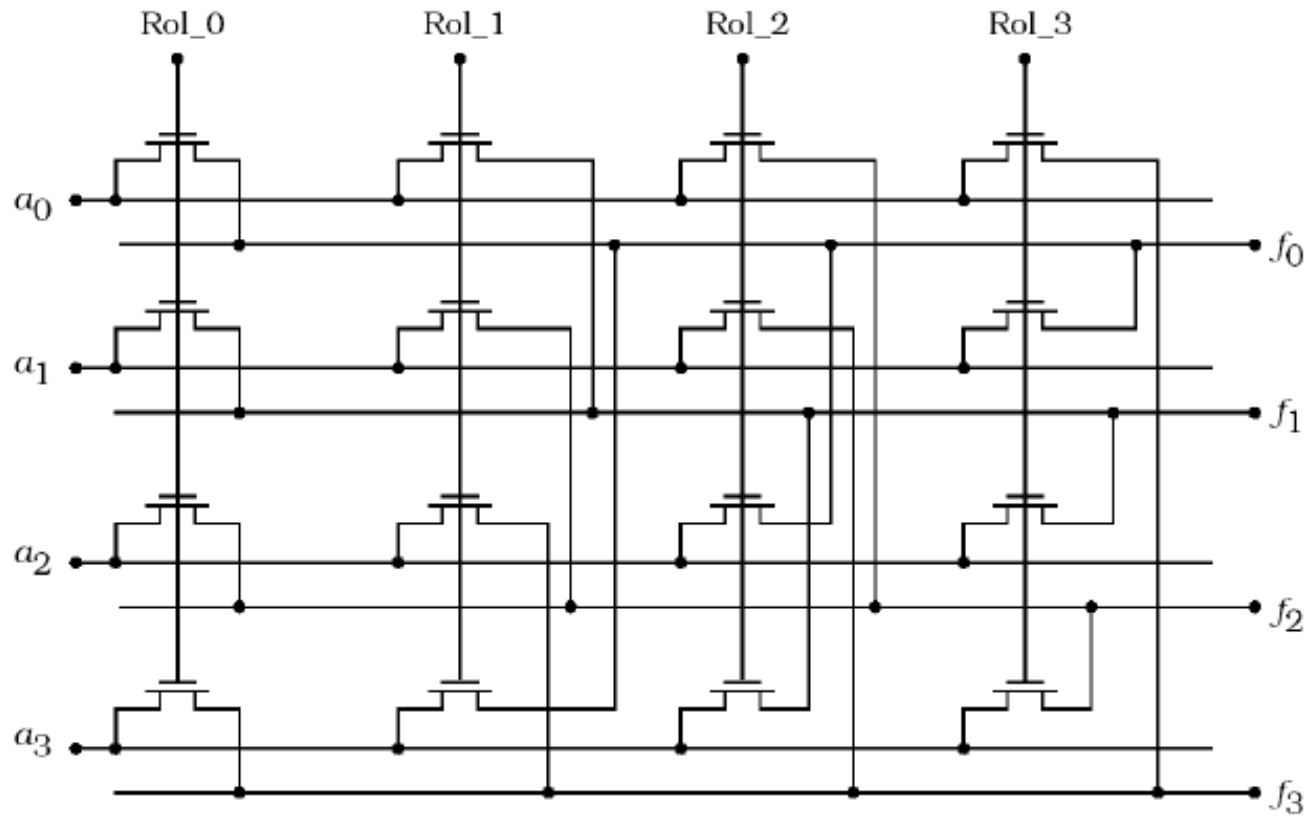


# 8 x 4 Barrel Shifter

 

shift	$b_0 b_1 b_2 b_3$
0	$a_0 a_1 a_2 a_3$
1	$a_1 a_2 a_3 a_4$
2	$a_2 a_3 a_4 a_5$
3	$a_3 a_4 a_5 a_6$
4	$a_4 a_5 a_6 a_7$

# FET Array Barrel Shifter

 

Thank You