 


Clamper circuit's

01
25/11/19

Numerical 01:-

Identify the circuit below and draw output waveform with proper voltage levels. Write the output expression



Solution:-

→ Since given diode is S_i , we will prefer constant voltage model (ie $V_{D_{on}} = 0.7V$)


→ Given $V_{in} = 10V_{p-p}$ ie $V_m = 5V$

Assumption:-

RC time constant is large enough (than time period of i/p sig) to ensure that voltage across capacitor does not discharge significantly during the period the diode is OFF.

Operation:

 a) During positive half cycle, Diode D_1 is ON when $V_{in} > V_{D,ON}$ i.e. the circuit becomes:



i.e. $V_{out} = V_{D,ON} = 0.7V$ --- during +ve half cycle of AC i/p

→ At the same time, C_1 charges and voltage across capacitor V_C reaches up to V_m .

KVL gives us: $V_{in} - V_C - V_{D,ON} = 0$


$$V_C = V_{in} - V_{D,ON} = V_m - V_{D,ON} = 5 - 0.7$$

$V_C = 4.3$ --- voltage across capacitor

during positive half cycle

b) During negative half cycle, Diode D_1 is OFF
 for entire negative cycle, i.e. the circuit becomes

03

 

Note: During -ve half cycle, capacitor holds the charges $V_c = 4.3V$ and act as a battery

KVL gives us :


$$-V_{in} - V_c - V_{out} = 0$$

$$V_{out} = -V_{in} - V_c = -V_m - V_c$$

$$V_{out} = -5 - 4.3 = -9.3V$$

i.e. $V_{out} = -9.3V$ ---- during -ve half cycle


I/P and o/p waveforms:-

 

$V_{D,ON} = 0.7V$

→ Since, the o/p waveform is shifted down of x-axis, the given circuit is a Negative clamper

 → If $V_{D,ON} = 0$ i.e. given diode was an ideal diode, then the above waveforms would have looked like.





$V_{D,ON} = 0V$

Design Q1:-

05
25/11/19

 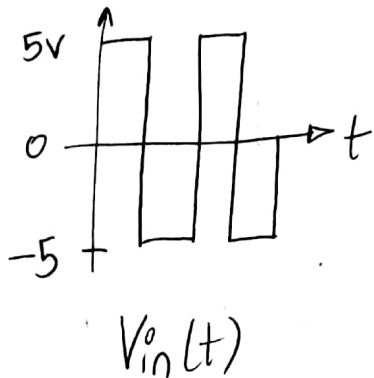
Design a diode clamper to generate a steady state output V_{out} from the i/p V_{in} shown in the figure below :-



Solⁿ:-

- 1) Inspecting the above waveforms, we have to shift the waveform above x-axis by some amount. Hence, it's a Positive clamper.
- 2) From $V_{out}(t)$, it is clear that we can use constant voltage model with $V_{D(on)} = 0.7V$
- 3) Also, from o/p waveforms, we deduce that during -ve half cycle of I/P, $V_{out} = -0.7V$ and during +ve half cycle of I/P, o/p is $V_{out} = 9.3V$

 
4) The diode clamper circuit which does this is shown below:



Let's see how the above designed diode clamper gives the desired O/P.

Operation:-

 a) During negative half cycle, D_1 is ON when $v_{in} < -V_{D,ON}$, i.e. the circuit becomes



i.e. $V_{out} = -V_{D,ON} = -0.7V$ ----- during negative half cycle of \mp/P

This is consistent with our design

b) At the same ^{time}, C_1 charges and voltage across C_1 charges up to $-V_m$.

KVL gives us:

$$V_{in} + V_C + V_{D, on} = 0$$

$$V_C = -V_{in} - V_{D, on}$$

$$= -(-V_m) - V_{D, on}$$


$$= -(-5) - 0.7$$

$$\boxed{V_C = 4.3V}$$

In negative half cycle
 $V_{in} = -V_m$

 c) During the positive half cycle, Diode is OFF for entire positive cycle i.e. the circuit becomes,

Note:- During +ve half cycle, capacitor C_1 holds the charge $V_C = 4.3V$ & act as a battery



KVL gives,

$$V_{in} + V_C - V_{out} = 0$$

$$V_{out} = V_{in} + V_C$$

$$= V_m + V_C$$

$$= 5 + 4.3$$


$$\boxed{V_{out} = 9.3V}$$

This value of o/p is in consistent with our design.

Numerical 02:-

Draw o/p waveforms with proper voltage levels for the circuit shown below:-

$$V_1 = 2.7V$$

 


Solⁿ:- i) Since given diode D_1 is Si diode, we will use constant voltage model i.e. $V_{on} = 0.7V$

Given:- $V_{in} = 10V$ peak i.e. $\pm V_m = \pm 10V$

Operation:-

 a) During negative half cycle, D_1 is ON when $V_{in} < (-V_{on} + V_1)$, \rightarrow ckt reduces to



$$V_{out} = -V_{on} + V_1$$

$$= -0.7 + 2.7V$$

$$V_{out} = 2V$$

ie $V_{out} = 2V$ ---- during negative half cycle

09

b) At the same time, voltage across capacitor V_C charges upto $-V_m$

KVL gives us: $V_{in} + V_C + V_{D,OV} - V_1 = 0$


$$\begin{aligned} V_C &= -V_{in} - V_{D,OV} + V_1 \\ &= -(-V_m) - 0.7 + 2.7 \\ &= 10 - 0.7 + 2.7 \end{aligned}$$

-ve h.c
 $V_{in} = -V_m$

$V_C = 12V$ ---- voltage across

Capacitor C_1 during +ve half cycle

 c) During positive half cycle, Diode D_1 is OFF for entire positive half cycle ie the circuit becomes



Note: During positive half cycle, capacitor C_1 holds the charge $V_C = 12V$ and act as a battery

KVL gives us :-

$$V_{in} + V_c - V_{out} = 0$$

$$V_{out} = V_{in} + V_c$$


$$= V_m + V_c$$

$$= 10 + 12$$

$$\boxed{V_{out} = 22V}$$

--- during +ve half cycle

Input and Output waveforms:-



 


Note : The o/p waveform only shifts up and down the x-axis, without distorting the o/p at all.

→ Since, the o/p waveform is shifted above x-axis, the circuit is a Biased Positive clamper.

Design 02:

   Design a circuit which does the following




Solⁿ: 1) Inspecting the above waveforms, we have to shift the waveform below x-axis by some amount & also some +ve portion of o/p also remains above x-axis.

Hence, it must a Biased Negative clamper

2) From $V_{out}(t)$, it is clear that we can either choose $V_{D,ON} = 0.7$ or $V_{D,ON} = 0V$
 We will go with constant voltage model with $V_{D,ON} = 0.7V$.

3) Also, from o/p waveforms, we deduce that during +ve half cycle of I/P, $V_{out} = +6V$ and during -ve half cycle of I/P, o/p is $V_{out} = -14V$

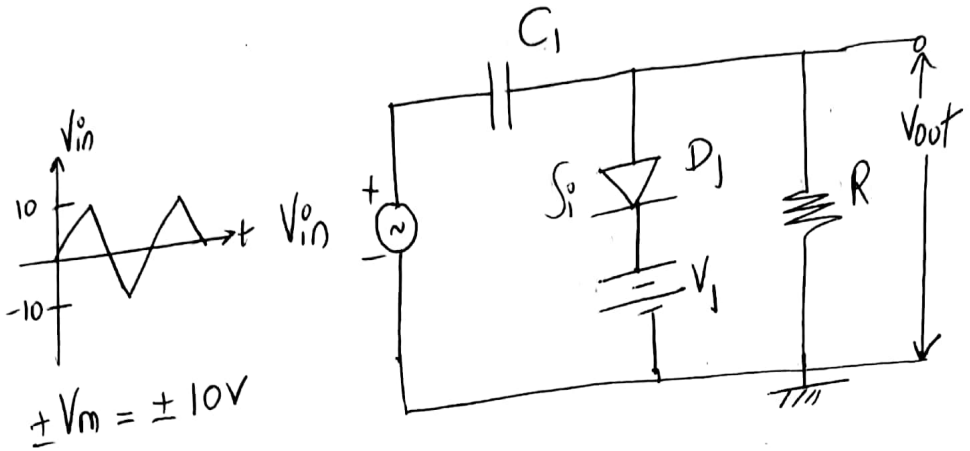4) The diode clamper circuit which can produce such an o/p is:




Consider D_1 as a Si diode

let's see how the above designed diode clamper gives the desired o/p

Operation:-

a) We want $V_{out} = +6V$ during +ve half cycle
 i.e. during +ve half cycle, Diode D_1 should be ON when $V_{in} > V_{D,ON} + V_1$

i.e. circuit reduces to

 

$V_{out} = V_{D,ON} + V_1$

We know $V_{D,ON} = 0.7V$
 So, V_1 has to be 5.3

ie $V_{out} = 0.7 + 5.3 = 6V$ ----- during +ve half cycle of I/P as desired

This is now consistent with our design

b) At the same time, voltage across C_1 charges up to V_m .

KVL gives us :

$$V_{in} - V_C - V_{D,ON} - V_1 = 0$$

$$V_C = V_{in} - V_{D,ON} - V_1$$

$$V_C = V_m - V_{D,ON} - V_1$$

$$V_C = 10 - 0.7 - 5.3$$

$V_C = 4V$

It indicates the voltage across C_1 during positive half cycle.

c) During the negative half cycle, capacitor C_1 holds the charges $V_C = 4V$ and acts as a battery

Also, during -ve half cycle, Diode D_1 is OFF ie the circuit becomes

KVL gives us:- $V_{in} - V_C - V_{out} = 0$

$$\begin{aligned} V_{out} &= V_{in} - V_C \\ &= -V_m - V_C \\ &= -10 - 4 \end{aligned}$$

During -ve half cycle,
 $V_{in} = -V_m$

$$V_{out} = -14V$$

----- during -ve half cycle as desired

Hence, the circuit which produce o/p is given below

