

# Design Rules for CMOS



- Design Rules
- Stick Diagrams
- Layout Diagram
- Examples

# Design Rules: Introduction

---

- ❑ Design rules are a set of geometrical specifications that **dictate the design** of the layout
- ❑ **Layout is top view of a chip.**
- ❑ Design process are aided by stick diagram and layout
- ❑ Stick diagram gives the placement of different components and their connection details
- ❑ But the dimensions of devices are not mentioned
- ❑ Circuit design with Darshana Sankhe, DJSGOE all dimensions is Layout

# Design Rules: Introduction

---

- ❑ Fabrication process needs different masks, these masks are prepared from layout
- ❑ Layout is an Interface between circuit designer and fabrication engineer
- ❑ Layout is made using a set of design rules.
- ❑ Design rules allow translation of circuit (usually in stick diagram or symbolic form) into actual geometry in silicon wafer
- ❑ These rules usually specify the minimum allowable line widths for physical objects on-chip
- ❑ Example: metal, polysilicon, interconnects, diffusion areas, minimum feature dimensions, and minimum allowable separations between two such features.

# NEED FOR DESIGN RULES








---

- Better area efficiency
- Better yield
- Better reliability
- Increase the probability of fabricating a successful product on Si wafer

If design rules are not followed:

- Functional or non-functional circuit.
- Design consuming larger Si area.
- The device can fail during or after simulation.

# Colour Codes :

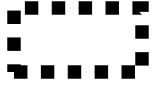Layer	Color	Representation
N+ Active	Green	
P+ Active	Yellow/Brown	
PolySi	Red	
Metal 1	Blue	
Metal 2	Magenta	
Contact	Black	<b>X</b>
Buried contact	Brown	<b>X</b>
Via	Black	<b>X</b>
Implant	Dotted yellow	
N-Well	Dotted Green/Black	

# Stick Diagrams :

---


- ❑ A stick diagram is a symbolic representation of a layout.
- ❑ In stick diagram, each conductive layer is represented by a line of distinct color.
- ❑ Width of line is not important, as stick diagrams just give only wiring and routing information.
- ❑ Does show all components/vias, relative placement.
- ❑ Does not show exact placement, transistor sizes, wire lengths, wire widths, tub boundaries.

# Stick Diagrams: Basic Rules

---

- Poly crosses diffusion forms transistor
- Red (poly) over Green(Active), gives a FET.


L:W

 

nFET/  
nMOS

- Aspect Ratio

L:W

 

pFET/pMOS

# Stick Diagrams (CMOS): Basic Steps

---

- Normally, the first step is to draw two parallel metal (**blue**)  $V_{DD}$  and GND rails.
- There should be enough space between them for other circuit elements.
- Draw Demarcation line (**Brown**) at center of  $V_{DD}$  and GND rails.
- This line represents the well (n/p-well).
- Next, Active (**Green/yellow**) paths must be drawn for required PU & PD transistors above & below DL.
- Draw vertical poly crossing both diffusions (**Green & yellow**)
- Remember, Poly (**Red**) crosses Active (**Green/yellow**), where transistor is required.



# Stick Diagram (CMOS): Basic Steps

---

- ❑ No Diffusion can cross demarcation line.
- ❑ Only poly and metal can cross demarcation line
- ❑ N-diffusion and p-diffusion are joined using a metal wire.
- ❑ Place all PMOS above and NMOS below demarcation line.
- ❑ Connect them using wires (metal).
- ❑ Blue may cross over red or green, without connection.
- ❑ Connection between layers is specified with **X**.
- ❑ Metal lines on different layer can cross one another, connections are done using via.


# Inverter Using MOSFET

---

- ❑ Enhancement-Mode MOSFETs act as switches.
- ❑ They are switched OFF, when the input to gate is low.
- ❑ So, they can be used to pull the output down.
- ❑ Now, for pull-up, we can use a resistor.
- ❑ But resistors consume larger area.
- ❑ Another alternative is using MOSFET as pull-up.
- ❑ PU's can be NMOS or PMOS.


# Inverter Using MOSFET

---



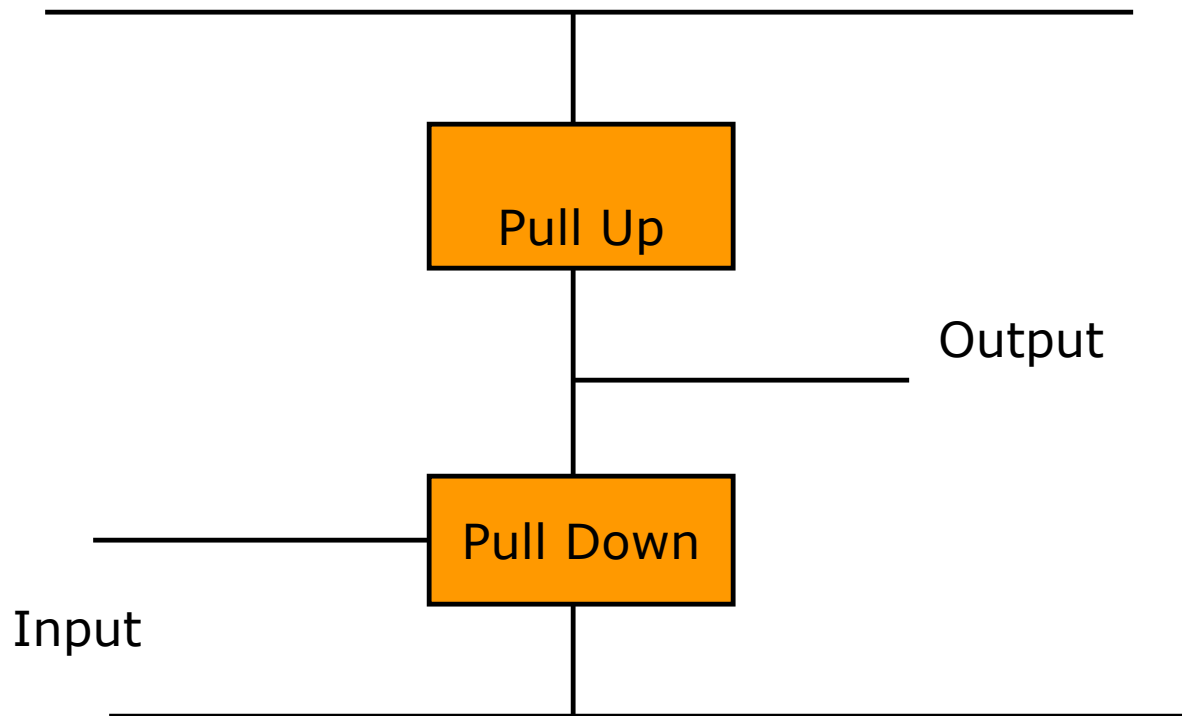


# CMOS Inverter (Circuit Diagram)

---

 


# CMOS Invertor (Stick Diagram)

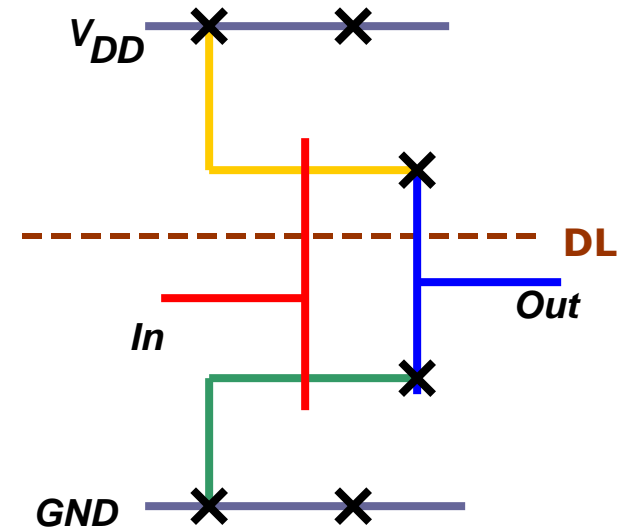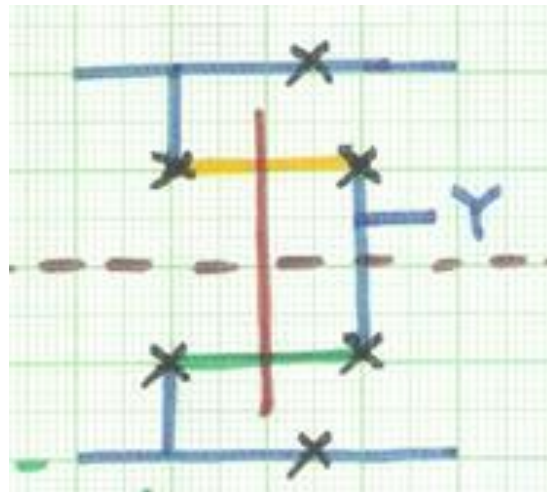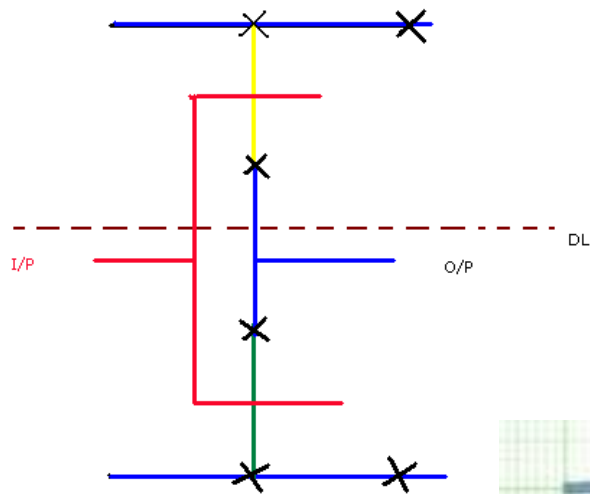

# CMOS INVERTER :

---


 


# Well Biasing :

---

- ❑ The various N and P diffusions must be reverse biased to ensure that those wells are insulated from each other.
- ❑ This requires that the N- wells are connected to the most positive voltage, VDD.
- ❑ The P- substrate must be connected to the most negative voltage, ground.
- ❑ This assumes that all other nets are at a voltage between 0V and VDD.

# MOSFET

 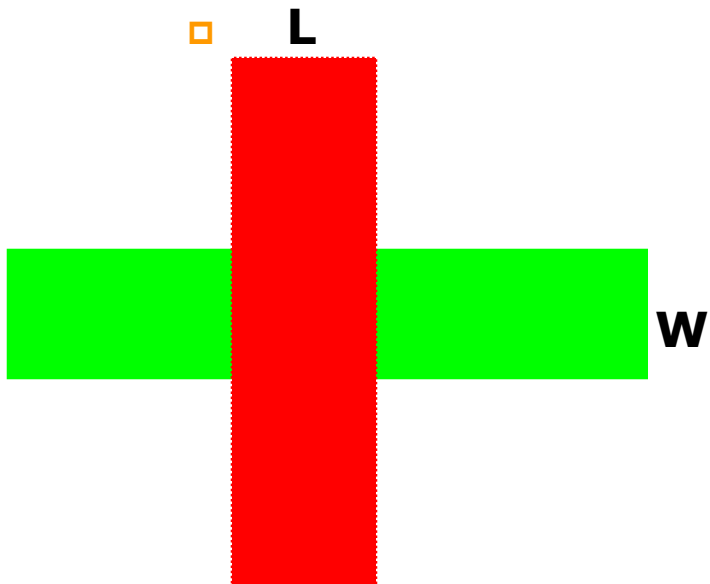

A silicon wafer



# Types of Layout Design Rules

---

- Industry Standard: Micron Rule
- $\lambda$  Based Design Rules

# Types of Design Rules (Contd...)

---

- **Industry Standard: Micron Rule**
  - All device dimensions are expressed in terms of absolute dimension( $\mu\text{m}/\text{nm}$ )
  - These rules will not support proportional scaling

# Types of Design Rules (Contd...)

---

## □ $\lambda$ Based Design Rules :

- Developed by Mead and Conway.
- All device dimensions are expressed in terms of a scalable parameter  $\lambda$ .
- $\lambda = L/2$ ;  $L =$  The minimum feature size of transistor
- $L = 2 \lambda$
- These rules support proportional scaling.
- They should be applied carefully in sub-micron CMOS process.

# Design Rules

---

- Minimum **length or width** of a feature on a layer is  **$2\lambda$** 
  - To allow for shape contraction
- Minimum **separation** of features on a layer is  **$2\lambda$** 
  - To ensure adequate continuity of the intervening materials.

# Design Rules :

---

- Two Features on different mask layers can be misaligned by a maximum of  $2\lambda$  on the wafer.
- If the overlap of these two different mask layers can be catastrophic to the design, they must be separated by at least  $2\lambda$
- If the overlap is just undesirable, they must be separated by at least  $\lambda$

# Design Rules: CMOS

---

- Line size and spacing:
  - **metal1:**
    - Minimum width= $3\lambda$ , Minimum Spacing= $3\lambda$
  - **metal2:**
    - Minimum width= $3\lambda$ , Minimum Spacing= $4\lambda$
  - **poly:**
    - Minimum width=  $2\lambda$ , Minimum Spacing= $2\lambda$
  - **ndiff/pdiff:**
    - Minimum width=  $3\lambda$ , Minimum Spacing= $3\lambda$ ,
  - **wells:**
    - minimum width= $6\lambda$ ,  
minimum n-well/p-well space =  $6\lambda$  (They are at same potential)  
=  $9\lambda$  (They are at different potential)


# Design Rules: CMOS

---

- Transistors:
  - Min width =  $3\lambda$
  - Min length =  $2\lambda$
  - Min poly overhang =  $2\lambda$
  
- Contacts (Vias)
  - Cut size: exactly  $2\lambda \times 2\lambda$
  - Cut separation: minimum  $2\lambda$
  - Overlap: min  $1\lambda$  in all directions
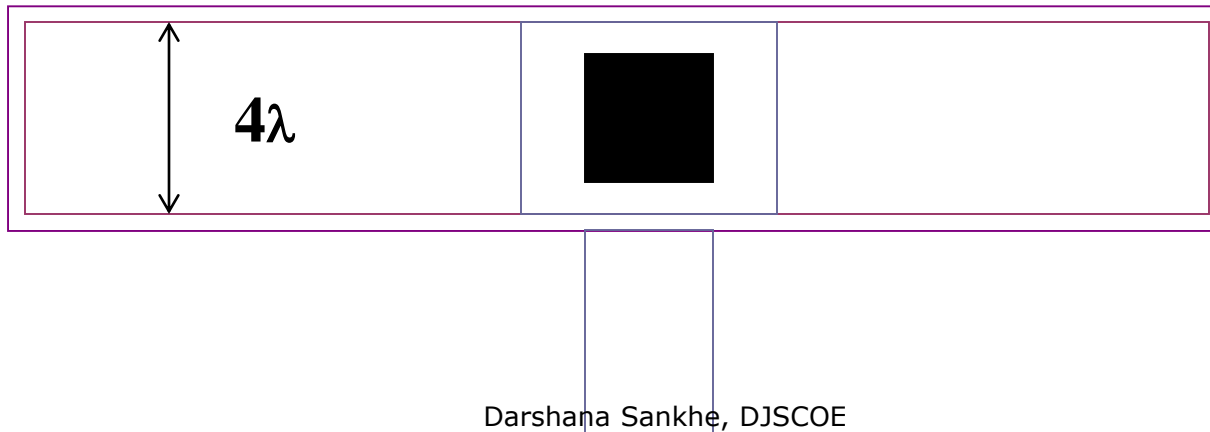
# Contact Cut :

- Metal connects to polySi/diffusion by contact cut.
- Contact area:  $2\lambda * 2\lambda$
- Metal and polySi or diffusion must overlap this contact area by  $\lambda$  so that the two desired conductors encompass the contact area despite any misalignment between conducting layers and the contact hole





 
# Contact Cut

---

- **Contact cut – contact cut:  $2\lambda$  apart**
- **Why? To prevent holes from merging.**



# Interlayer Contacts :


---

- Interconnection between poly and diffusion is done by contacts.
- Metal contact
- Butting contact
- Buried contact
 
# Metal contact :


---


- Contact cut of  $2\lambda * 2\lambda$  in oxide layer above poly and diffusion
- Metal used for interconnection
- Individual contact size becomes  $4\lambda * 4\lambda$





# CMOS Inverter:

---



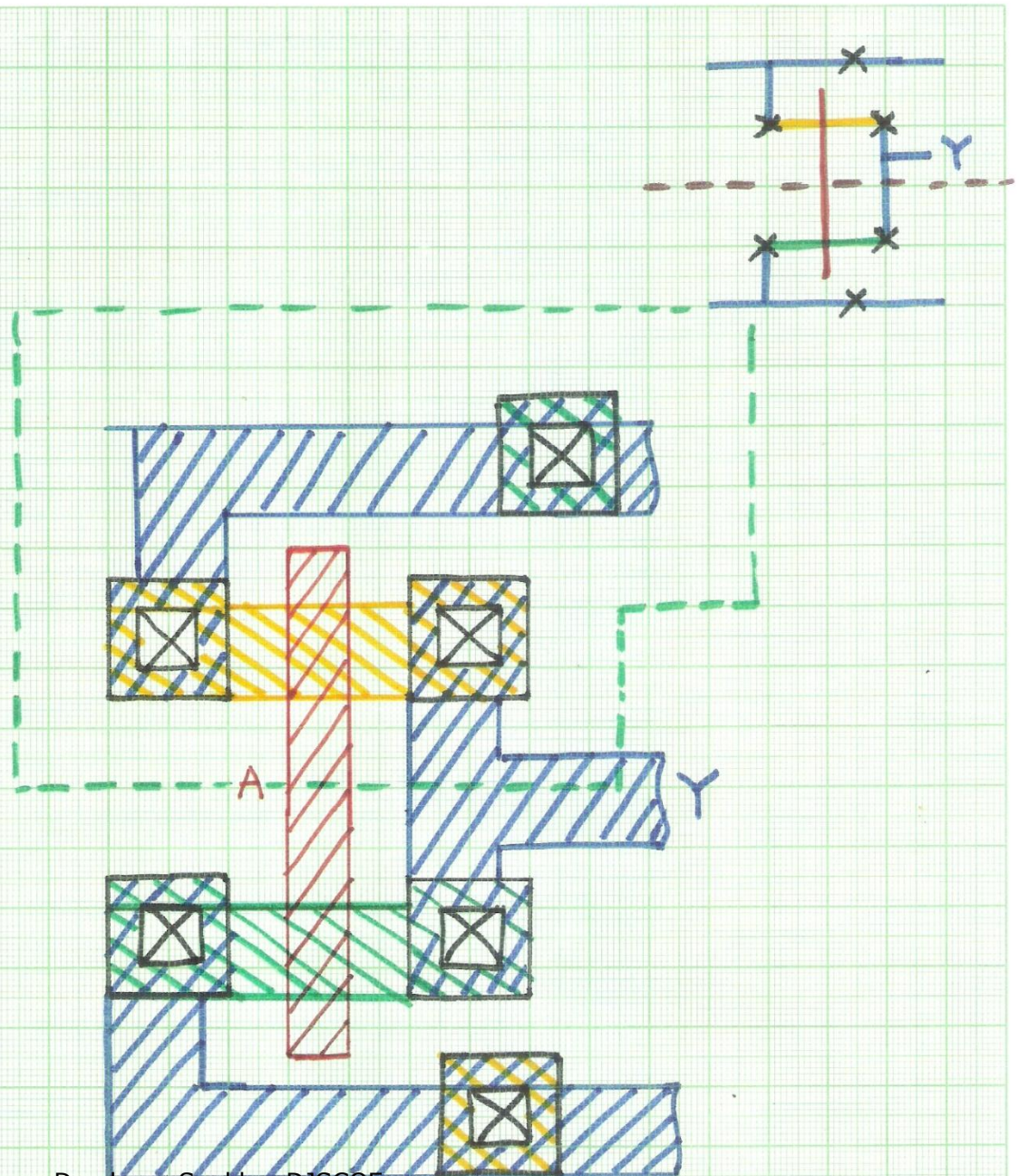


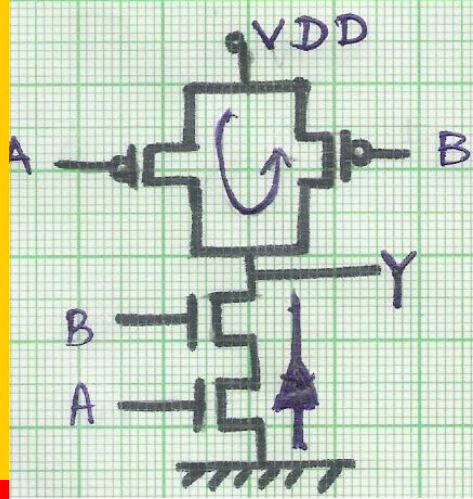

# CMOS NAND

 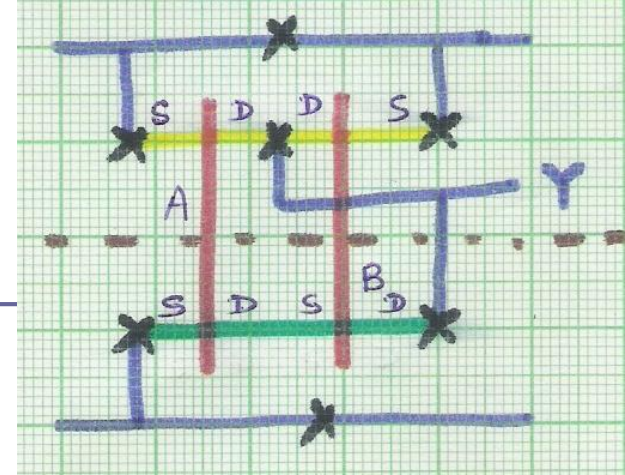

# CMOS NOR:

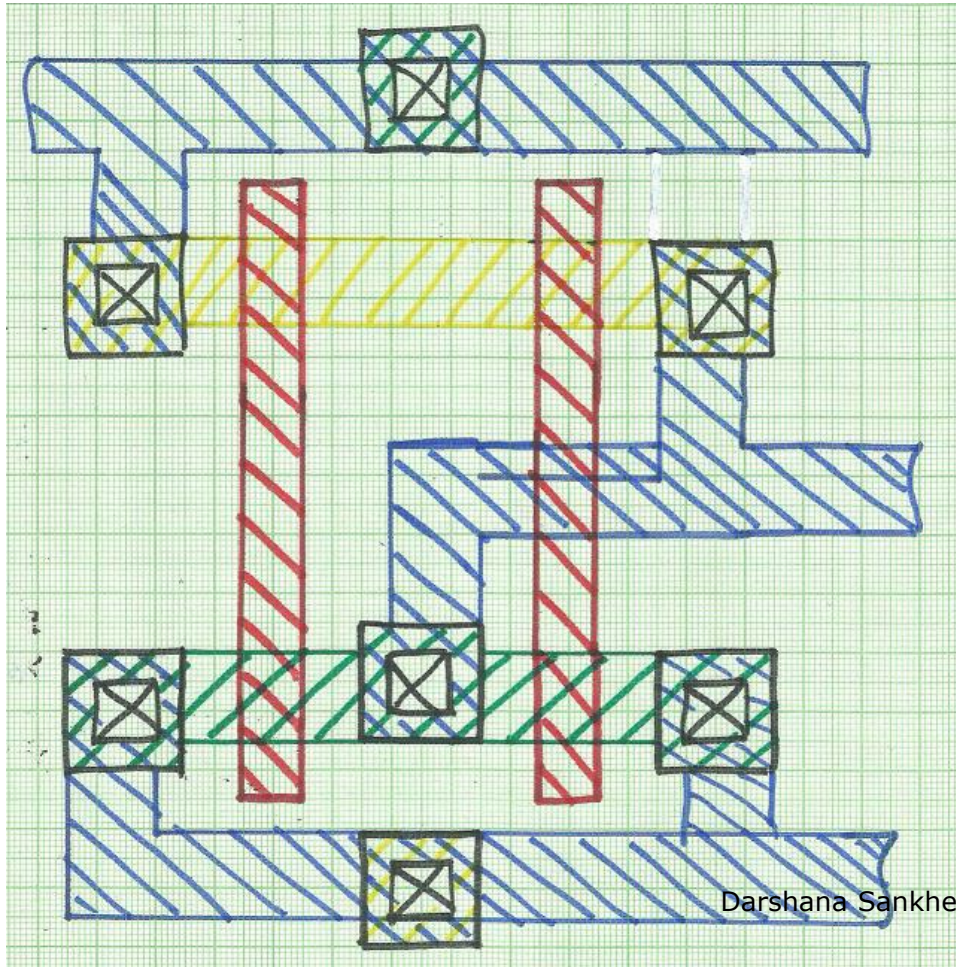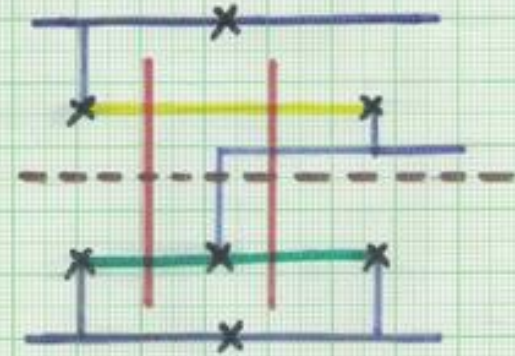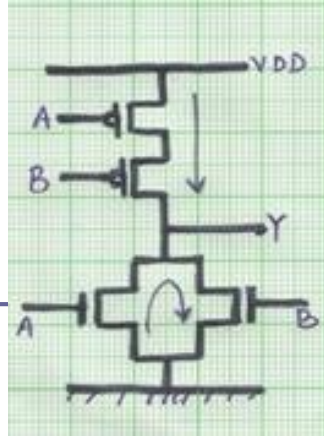

# Design of NMOS/CMOS Circuits:

---


- **PDN** – The Function to be implemented, must be expressed in a inverted form.

- $F = \overline{(A + BC)} D$

- $F = (AB + C) (D + E)$

- $\overline{F} = A + B + CD$

$$F' = A + B + CD$$

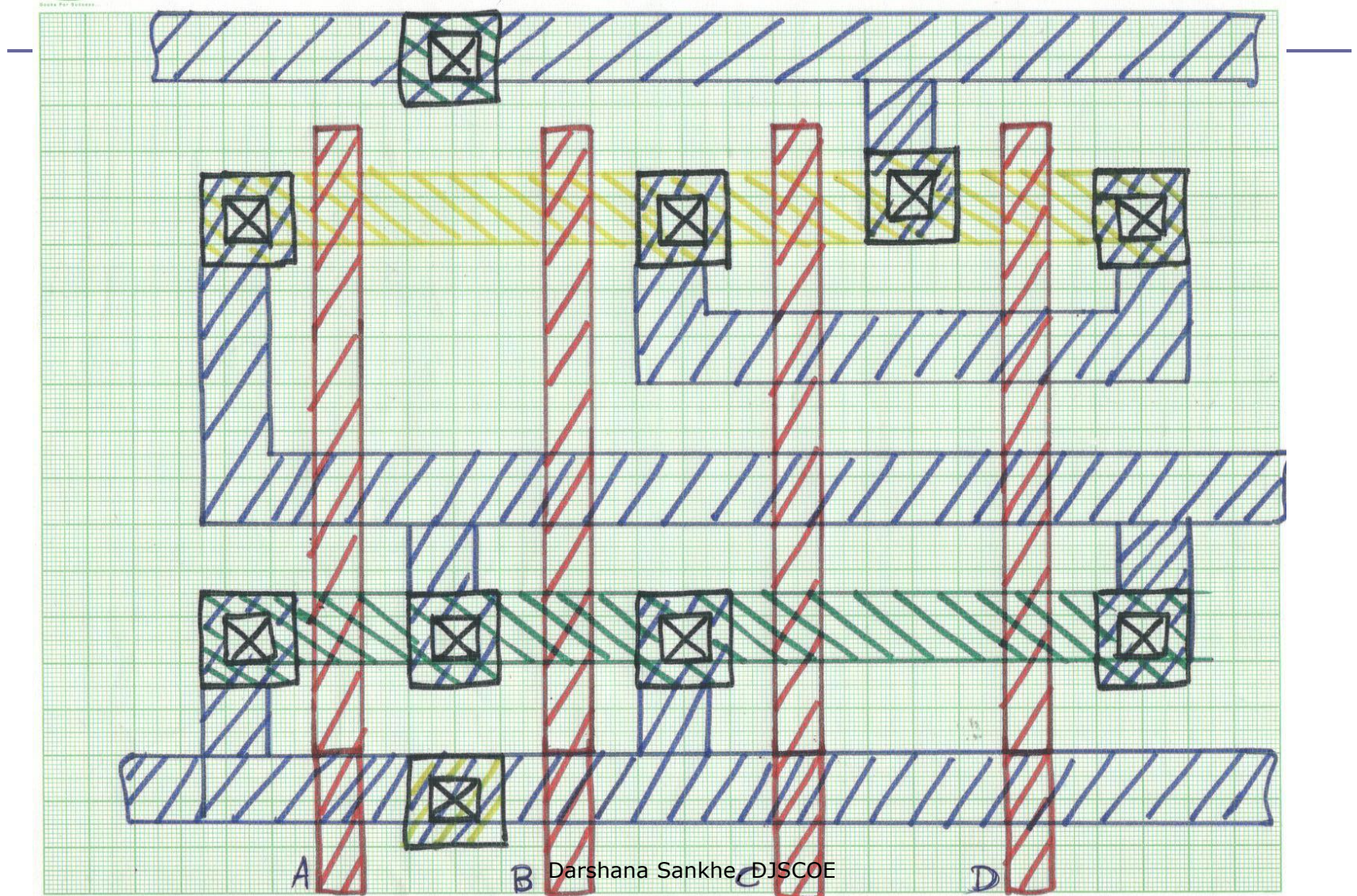



---

**Thank you**

Darshana Sankhe, DJSCOE