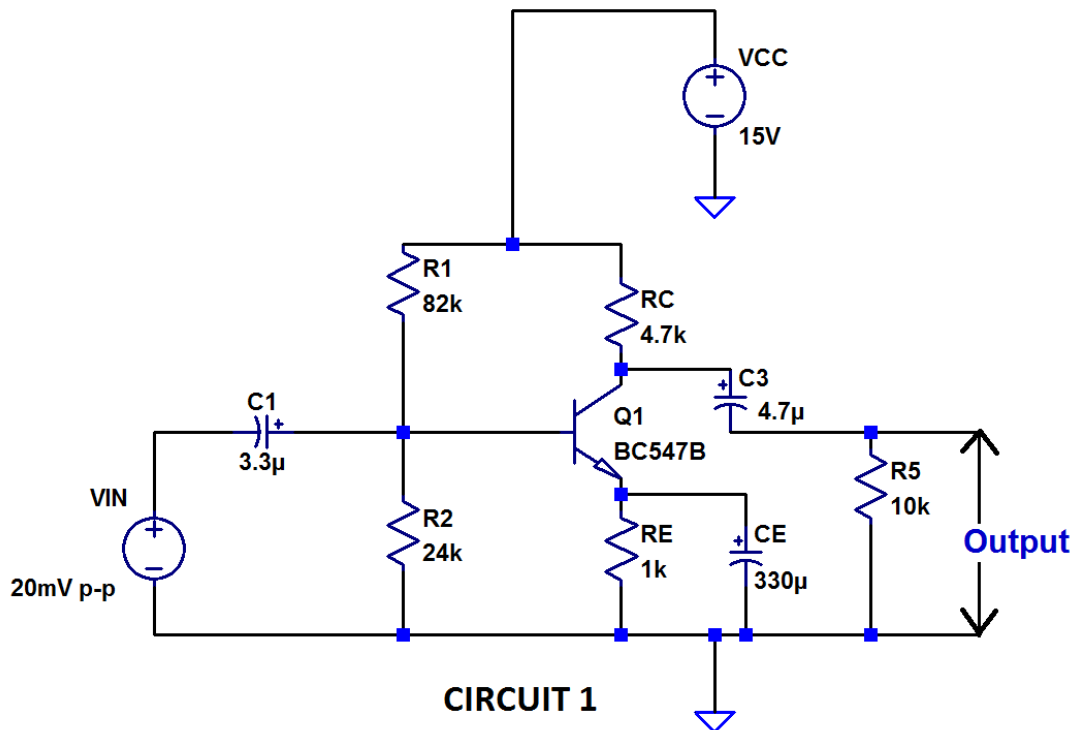



D. J. SANGHVI COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
EXC402: DISCRETE ELECTRONIC CIRCUITS SEM IV
ASSIGNMENT 1

22nd February, 2017


[Total Marks: 80]

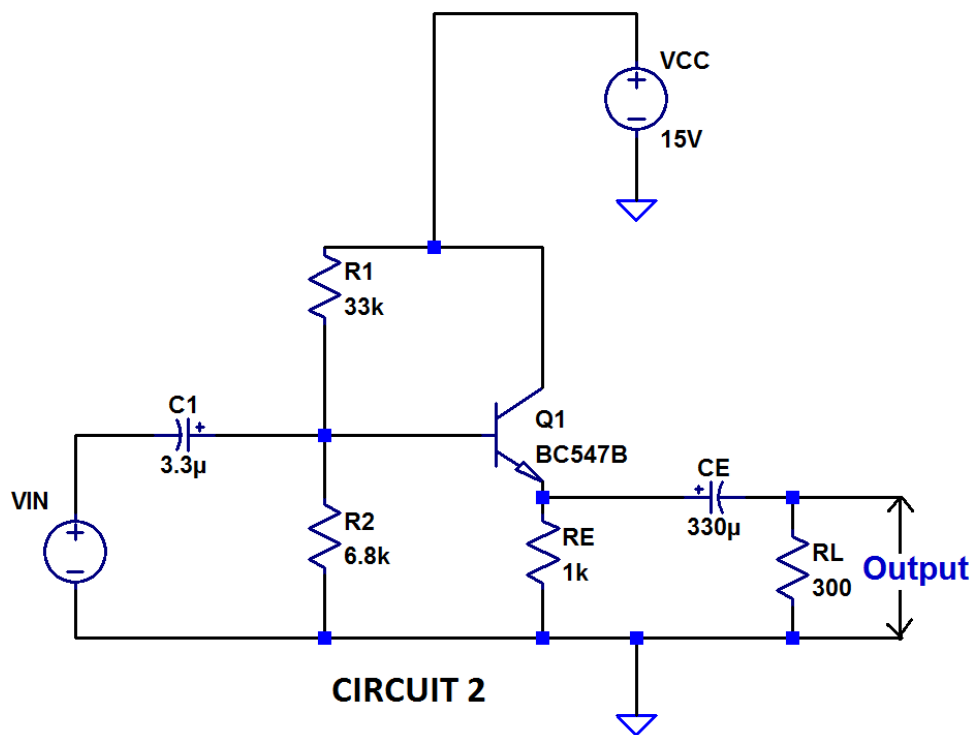1. Attempt all the questions.
 2. Read the questions carefully before attempting.
-
1. Derive the expression for small-signal hybrid π model parameters r_{π} , g_m and r_o for npn bipolar transistor. [05]
 2. Explain the need of dc biasing in BJT amplifiers. [05]
 3. What are the different biasing scheme used for npn BJT, explain voltage-divider bias technique. [05]
 4. Draw approximate hybrid π model of CE transistor amplifier and derive the expression for A_v , Z_i and Z_o [10]
 5. Design voltage divider biased circuit to give $I_{CQ} = 6mA$, $V_{CQ} = 6V$ and $\beta = 100$ [10]
 6. Identify the amplifier configuration (Circuit 1). Find input impedance, output impedance, voltage gain and output voltage for the given circuit. Given ($\beta = 300$, $V_{BE} = 0.65V$) [10]






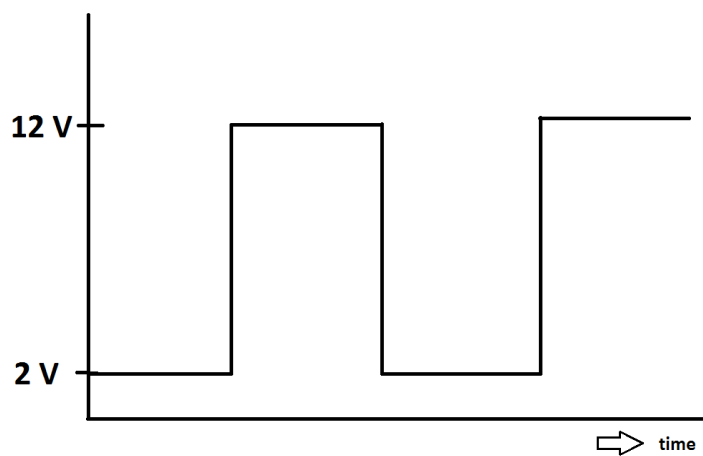7. Identify the amplifier configuration (Circuit 2). Find input impedance, output impedance and voltage gain for the given circuit. Given ($\beta = 300, V_{BE} = 0.65V$) [10]
8. Compare CE, CC and CB amplifiers. [5]
9. Implement appropriate circuit to generate following waveform. [5]



10. Identify the circuit and draw output waveform with proper voltage levels.

[5]

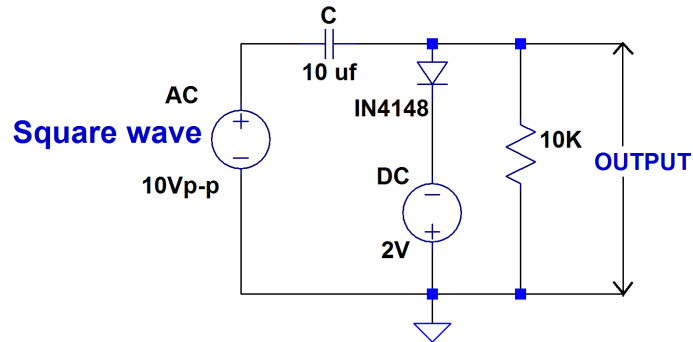

11. For the circuits given below, name the given clipper, draw Output waveforms, with proper justification using [10]

- a) Ideal diode model
- b) Constant voltage model

