

## \* MOSFET I-V Characteristics and device parameters estimation

Principle: A voltage at its gate terminal controls current between its source and drain.

- Note: i) Body terminal of an NMOS is connected to gnd  
ii) Body terminal of a PMOS is connected to highest voltage in the circuit i.e.  $V_{DD}$ .

This is done to minimize any drift in threshold voltage  $V_T$ .

• Long-channel approximation: - (NMOS)

$$I_D = \frac{K_n}{2} [2(V_{GS} - V_T)V_{DS} - V_{DS}^2] \quad \text{-- } V_{GS} - V_T > V_{DS} \quad \text{(Linear region)}$$

$$I_D = \frac{K_n}{2} [V_{GS} - V_T]^2 \quad \text{-- } V_{GS} - V_T < V_{DS} \quad \text{(Saturation region)}$$

$V_{TN}$  of NMOS is positive

$V_{TP}$  of PMOS is negative.

$$K_n = \mu_n C_{ox} \left( \frac{W}{L} \right)$$

### Problem Statement:

In this experiment, we will do the following for an NMOS transistor: -


- \* Measure threshold voltage  $V_{TN}$
- \* Measure o/p DC characteristics:  $I_D$  Vs  $V_{DS}$
- \* Measure  $I_D$  Vs  $V_{GS}$  characteristics in saturation region

\* Measure small signal transconductance ( $g_m$ )

Components required:

CD4007 MOSFET IC, 5.6V Zener,  
Resistor  $\rightarrow 680\Omega, 100\Omega, 5K\text{ pot}, 1K\Omega$   
Capacitor  $\rightarrow 10\mu F$ , Multimeter, Function generator, CRO.

CD4007: (PIN OUT)

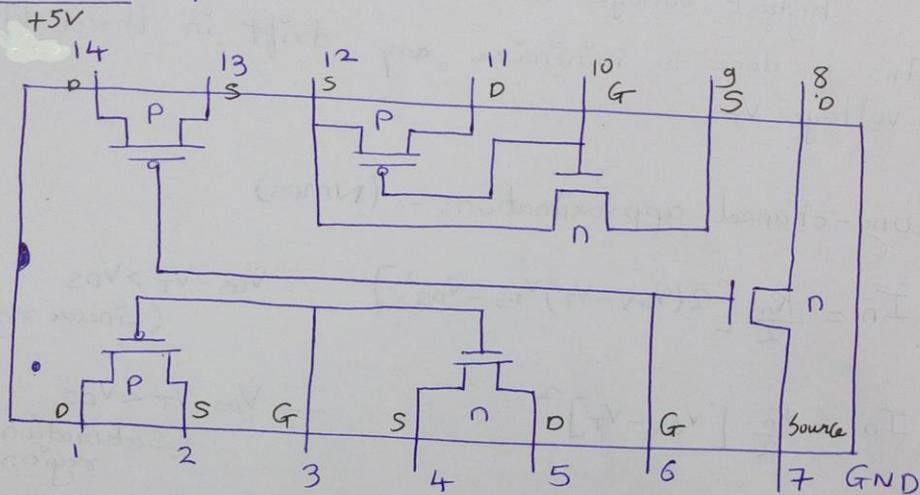


7  $\rightarrow$  gnd  
14  $\rightarrow$  ~~V<sub>DD</sub>~~ +5V (body terminal of all NMOS T<sup>s</sup> are tied together)

Analysis (PART I):  $V_T$  of NMOS

$\Rightarrow$  Threshold voltage ( $V_T$ ) can be found by biasing NMOS in Linear region and varying  $V_{gs}$  in small steps and noting Linear change in  $I_D$   
(Refer circuit @)

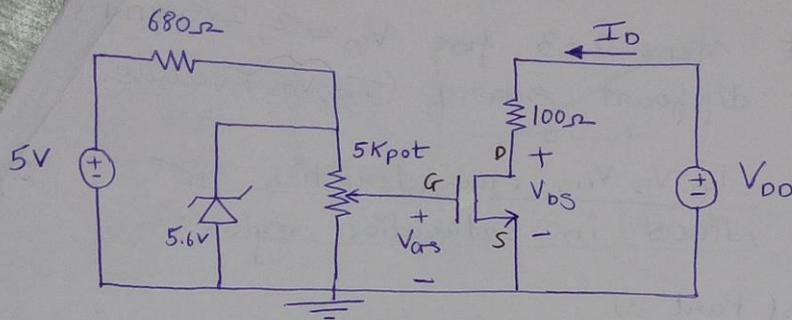Zener-diode is used to prevent gate voltage from going above 5.6V  $\Rightarrow$  which may cause device oxide to break down.



Circuit @

Procedure (Part A):

- 1) Wire up the above circuit @. Adjust  $V_{DD}$  such that  $V_{DS} \approx \underline{200\text{mV}}$ . (Keep monitoring  $V_{DS}$  throughout this part - it should be kept constant at 200mV)
- 2) Vary  $V_{GS}$  by means of 5K pot and note  $I_D$ . Take  $(I_D, V_{GS})$  readings till  $V_{GS} = 5\text{V}$

Note: Do not dismantle the ckt @, you will be using it for part B as well.

PART 2:  $I_D - V_{GS}$  characteristics | at  $V_{DS}$  constant

Procedure: (Part B)


- 1) Wire up the circuit @.
- 2) Adjust  $V_{GS} = 1.5\text{V}$  and monitor it to ensure that it stays constant.
- 3) Vary  $V_{GS}$  in small steps from 0 to 5V and note  $I_D$ .

4) Repeat steps 2-3 for  $V_{GS} = 2, 2.5$  and  $3V$  to get different sets of  $(I_D, V_{DS})$  values.

PART 3:  $I_D$  vs  $V_{GS}$  characteristics for NMOS in saturation region

Procedure: (Part 3)

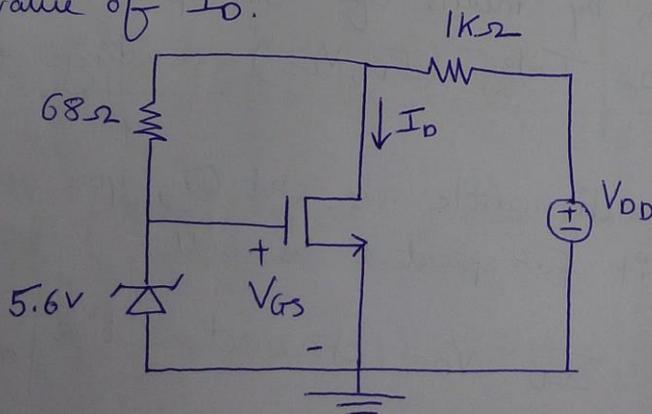- 1) Wire up circuit (b). The circuit is designed to make  $V_{GS} < V_{DS}$ . This ensures that  $V_{DS} > V_{GS} - V_{TN}$  i.e. transistor always remain in saturation.
- 2) Now vary  $V_{GS}$  by varying  $V_{DD}$  in small steps from 0 to 5V. Note down the value of  $I_D$ .




Circuit (b)

\* Obtaining results and Interpreting them:-

PART A :

From  $I_D - V_{GS}$  data in part A:-

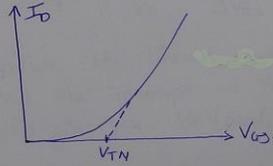- 1) Plot graph of  $I_D$  vs  $V_{GS}$  on linear scale.
- 2) Extrapolate linear portion of plot as shown below to find the intercept on  $V_{GS}$  axis. This will give  $V_{TN}$ .




- 3) Also compute  $g_m = \frac{\partial I_D}{\partial V_{GS}}$ . At what value of  $V_{GS}$  is  $g_m$  maximum?
- 4) Calculate Linear region resistance  $r_o$  and plot it as a function of  $V_{GS} - V_{TN}$ .

## PART B:

From  $I_D$ - $V_{DS}$  data in Part B:

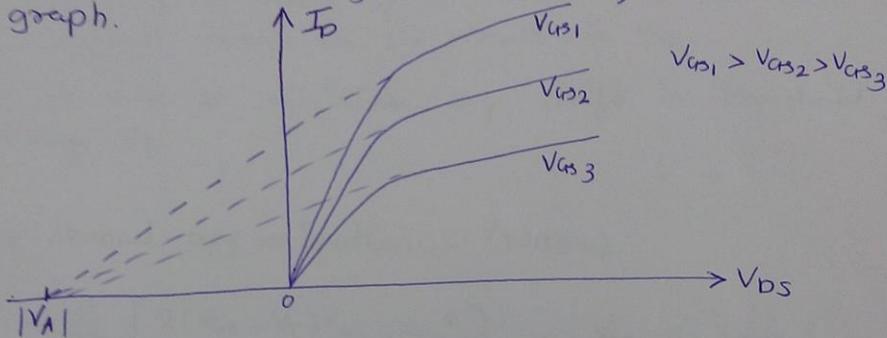- 1) Plot a graph of  $I_D$  vs  $V_{DS}$  on a linear scale. Plot all of these  $V_{GS}$   $\Rightarrow$  different constant values  $\Rightarrow$  for  $I_D$  vs  $V_{DS}$  on same graph.



- 2) From the slope of linear portion of graph, find o/p drain-source resistance  $r_o$  at  $V_{DS} = 5V$  for different value of  $V_{GS}$  as,

$$\text{slope} = \frac{1}{r_o} = \frac{\Delta I_D}{\Delta V_{DS}} \Big|_{V_{GS}}$$

- 3) ~~Extrapolate the linear portion of graph to find the intercept on  $V_{DS}$  axis. This will give you  $V_A$  (Early voltage).~~

Part C: From  $I_D$ - $V_{DS}$  characteristics in saturation

- 1) Plot a graph of  $I_D$  vs  $V_{DS}$  on a linear scale.