 


FET CHARACTERISTICS

AIM :- To study the FET characteristics .


APPARATUS :- FET – BFW 10/11, resistors, 2 – power supply , multimeter.

CIRCUIT DIAGRAM :-




THEORY :-

Construction & Char. of JFET:-

 

The basic construction of n –channel FET is as shown in figure. The major part of JEET is the channel between embedded P type of material.

The top of the n- channel is connected to an ohmic contact called as ‘Drain’ (D) & Lower end of Channel is called as ‘Source’ (S). The two p types of materials are connected together & to the ‘Gate ‘terminal (G).

 Characteristic:-**1. $V_{GS} = 0V$, V_{DS} - Some +ve Value:-**

As shown in the figure the gate is directly connected to source to achieve $V_{GS} = 0V$, this is similar to no bias condition. The instant the voltage $V_{DD}(=V_{DS})$ is applied, the e^- will be drawn to the drain terminal, causing I_D & I_S to flow (i.e. $I_D = I_S$). Under this condition the flow of charge is limited solely by Resistance of the n channel between drain & source.

It is important to note that the depletion region is wider at the top of both p type of material. Since the upper terminal is more R.B. than the lower terminal (source - S).

As voltage V_{DS} is increased from 0 to few volts, the current will increase as determined by ohm's law. If still V_{DS} is increased & approaches a level referred to as V_p , the depletion region will widen, causing a noticeable reduction in channel width. The reduced path of conduction causes the resistance to increase. The more the horizontal curve, the higher the resistance.

If V_{DS} is increased to a level where it appears that the two depletion regions would touch each other, the condition referred to as 'pinch-off' will result. The level of V_{DS} that establishes this condition is called as 'pinch-off voltage' (V_p). At V_p , I_D should be zero, but practically a small channel still exists & very high density current still flows through the channel.

As V_{DS} is increased beyond V_p the saturation current will flow through the channel (I_{DSS}).


I_{DSS} – Drain to source current with short-circuit connection from source to Gate.

2. $V_{GS} < 0V$:-

If a -ve bias is applied between gate and source, the effect of the applied -ve bias V_{GS} is to establish a depletion region similar to those obtained with $V_{GS} = 0V$ but at a lower level of V_{DS} .

As V_{GS} will become more & more -ve biased, the depletion layer pinch-off occurs at a less & less value of V_{DS} . Eventually, when $V_{GS} = -V_p$, will be sufficiently -ve to establish a

 saturation level, i.e. essentially 0 mA & for all practical purpose the device has been 'turned OFF.'



The region to the right of the pinch-off locus is typically employed in linear amplifiers (Amplifier with min. distortion at applied signal) is commonly referred as the constant current, saturation or linear amplification region.

Voltage controlled region. :-

The region left of pinch-off locus is called as ohmic or voltage controlled region.

In this region the JFET can actually be employed as a variable resistor whose resistance is controlled by V_{GS} . As V_{GS} becomes more & more -ve, the slope of the curve becomes more & more horizontal, corresponding with an increasing resistance level.

$$r_d = \frac{r_o}{\left(1 - \frac{V_{GS}}{V_P}\right)^2}$$

Where,

r_o – the resistance with $V_{GS} = 0V$


r_d – the resistance at particular value of V_{GS} .

Transfer characteristic:-

The relation between I_D & V_{GS} , is given by Shockley's equation.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

 The squared term of equation will result in a non-linear relationship between I_D & V_{GS} .



PROCEDURE:-

1. Assemble the circuit as per given diagram properly.
2. Adjust both supply to 0V i.e $V_{GS} = 0V$ & $V_{DS} = 0V$
3. Note down drain current I_D in mA.
4. By keeping V_{GS} constant to 0V, increase drain to source voltage V_{DS} in step of 1V upto 10 volts and measure the current I_D .
5. Now change V_{GS} from 0V to 0.5, 1V, 1.5V, 2V, 2.5, 3 V etc. and repeat the above step no.4. (V_{GS} voltage should be constant)
6. Now keep the voltage V_{DS} constant at 10 v. Change the V_{GS} in the step of 0.5 upto 4V. Measure current I_D . Tabulate all readings.
7. Plot the characteristics i.e V_{DS} vs I_D and V_{GS} vs I_D .
8. Calculate I_{DSS} , V_P , g_{mo} , r_{ds} from the graphs and verify it from the data sheet.

OBSERVATION TABLE :- Table 1

$V_{GS} = 0V$		$V_{GS} = 0.5V$		$V_{GS} = 1V$		$V_{GS} = 1.5V$upto 3V	
V_{DS} (V)	I_D (mA)	V_{DS} (V)	I_D (mA)	V_{DS} (V)	I_D (mA)	V_{DS} (V)	I_D (mA)
0							
1							
2							
Upto 10							

Table 2 $V_{DS} = 10V$

$V_{GS}(V)$	I_D (mA)
-0.5 V	
-1V	
1.5V upto 5V	

CONCLUSION :-