

## Module 02: Bipolar Junction Transistor

01 R  
24/08/2014

### Topic: 1) Equivalent Circuit Models for BJT

2) Non-Ideal Effects  
• In order to analyze or design a transistor circuit, one needs a mathematical model or equivalent circuit of the transistor.

#### Models for BJT

- A] Eber's mott model
- B] Gummel-Poon model
- C] Hybrid- $\pi$  model

→ These 3 equivalent circuit models can replace transistors in a circuit.

\* Eber's mott model can be used for a transistor biased in any of its operating modes. & are particularly used in switching applications.

\* Gummel-Poon model also take into account non-ideal effects in a BJT, which are ignored (Early effects & high level injection) in Eber's mott model.

\* Hybrid- $\pi$  model is applied when the transistors are operated in a small signal linear amplifier & takes into account frequency effects within the transistor.

INDERJIT SINGH

## \* Eber's - Moll model:

02

A BJT consists of two interacting junction diodes and Eber's - moll model uses this interaction as its basic fundamental foundation and is applicable in any of BJT operating modes

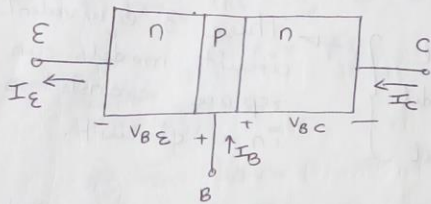


fig a. Current directions and voltage polarity definitions for Eber's - moll model.

From fig a,  $I_E = I_B + I_C$  — (1)

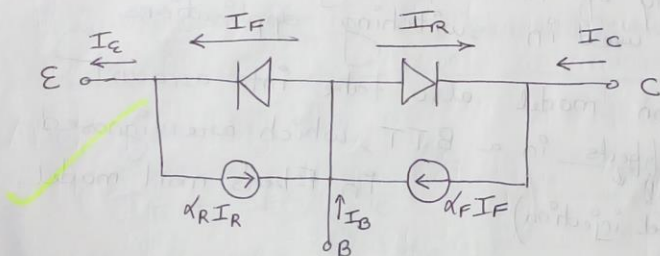


fig b: Eber's moll model for npn BJT

xtor!

Idea here is to evaluate terminal currents i.e  $I_E, I_B, I_C$ , if voltage applied between the two junction's are known i.e  $V_{BE}$  and  $V_{BC}$  and vice-versa. That the idea behind this model.

From fig (b), we can write

03

A) For  $V_{BE} \neq 0, V_{BC} \neq 0$ , cases.

$$I_C = \alpha_F I_F - I_R \quad \text{--- (2)}$$

$$I_E = I_F - \alpha_R I_R \quad \text{--- (3)}$$

Extra!

B) For  $V_{BE} = 0, \Rightarrow I_F = 0$

$$\leftarrow \beta_R = \frac{\alpha_R}{1 - \alpha_R}$$

Reverse current gain

C) For  $V_{BC} = 0 \Rightarrow I_R = 0$

then  $I_C = \alpha_F I_F, I_E = I_F$   $\left\{ \begin{array}{l} I_E = I_C + I_B \\ I_B = I_E - I_C \end{array} \right.$

$$I_B = (1 - \alpha_F) I_F$$

$$\therefore \frac{I_C}{I_B} = \frac{\alpha_F}{1 - \alpha_F} = \beta_F \rightarrow \text{forward current gain}$$

Also, from fig (b),

$$I_F = I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) \quad \text{--- (4)}$$

$$I_R = I_{CS} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) \quad \text{--- (5)}$$

INDERJIT SINGH

where,  $I_{ES}$  is reverse-bias BE junction current

$I_{CS}$  is reverse saturation current for B-C junction.

Substitutes eq<sup>n</sup> (4) and (5) values in to eq<sup>n</sup> (2), we get <sup>04</sup>

$$I_C = \alpha_F I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - I_{CS} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) \quad \text{--- (6)}$$

Substitute eq<sup>n</sup> (4) & (5) values into eq<sup>n</sup> (3), we get

$$I_E = I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_R I_{CS} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) \quad \text{--- (7)}$$

Equation (6) and (7) represent the Ebers-Moll Equations, which are used to develop Ebers-moll equivalent circuit.

• The equivalent circuit consists of two current sources and two ideal pn junctions as shown in fig (b). Each current source is dependent upon the voltages across other junction.

• The Ebers-moll model has 4 parameters:

$$\alpha_F, \alpha_R, I_{ES} \text{ and } I_{CS}.$$

• However, these 4 parameters are not independent (only 3 are independent) quantities but are inter-related through the relation.

$$\alpha_F I_{ES} = \alpha_R I_{CS} \quad \text{--- (8)}$$

Reciprocity relationship

Ebers-moll model is valid for any mode of operation of BJT. For example, in the saturation mode, both B-E and B-C junctions are forward-biased, i.e.  $V_{BE}$  &  $V_{BC}$  used in equations (6) and (7) are positive (i.e.  $V_{BC} > 0$ ,  $V_{BE} > 0$ )

Extra!

- The B-E voltage will be a known parameter, since we will apply a voltage across this junction.
- The F.B. B-C voltage is a result of driving the transistor into saturation and is the unknown to be determined from the Ebers-moll equations.

In a lot of applications involving BJT, C-E voltage at saturation i.e.  $V_{CE(sat)}$  is an important quantity (of interest).

$$V_{CE(sat)} = V_{BE} - V_{BC} \quad \text{--- (9)}$$

We will find an expression for  $V_{CE(sat)}$  by combining Ebers-moll equations.

Solving for  $V_{BE}$  :

Rewriting eq<sup>n</sup> (6) and putting value of  $I_{CS}$  from eq<sup>n</sup> (9)  
ie  $I_{CS} = \frac{\alpha_F I_{ES}}{\alpha_R}$

$$\text{ie } I_C = \alpha_F I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \frac{\alpha_F I_{ES}}{\alpha_R} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) \quad (10)$$

$$\text{ie } \alpha_R I_C = \alpha_R \alpha_F I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_F I_{ES} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) \quad (11)$$

Now from eq<sup>n</sup> (1) and (7), we get  $I_E = I_C + I_B$

$$I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_R I_{CS} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) = I_B + I_C$$

ie using relation from eq<sup>n</sup> (8), we get

$$I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_F I_{ES} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) = I_B + I_C \quad (12)$$

Eq<sup>n</sup> (11) can be written as,

$$\alpha_F I_{ES} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) = \alpha_R \alpha_F I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_R I_C \quad (13)$$

Put eq<sup>n</sup> (13) in eq<sup>n</sup> (12), we get (ie eliminating  $V_{BC}$  term)

$$I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \left[ \alpha_R \alpha_F I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_R I_C \right] = I_B + I_C$$

$$\text{ie } I_{ES} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) (1 - \alpha_R \alpha_F) = I_B + I_C (1 - \alpha_R)$$

$$\text{ie } \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) = \frac{I_B + I_C (1 - \alpha_R)}{I_{ES} (1 - \alpha_R \alpha_F)}$$

$$e^{\frac{V_{BE}}{V_T}} = \frac{I_B + I_C(1-\alpha_R)}{I_{ES}(1-\alpha_R\alpha_F)} + 1$$

07

$$\therefore V_{BE} = V_T \ln \left[ \frac{I_B + I_C(1-\alpha_R) + I_{ES}(1-\alpha_R\alpha_F)}{I_{ES}(1-\alpha_R\alpha_F)} \right]$$

— (A)

Similarly, Solving for  $V_{BC}$ :

From eq<sup>n</sup> (6) and (8), we get  $\alpha_F I_{ES} = \alpha_R I_{CS}$

$$I_C = \alpha_R I_{CS} (e^{\frac{V_{BE}}{V_T}} - 1) - I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1) \quad (14)$$

Using eq<sup>n</sup> (7) & substituting  $I_{ES} = \frac{\alpha_R I_{CS}}{\alpha_F}$  we get

$$I_E = \frac{\alpha_R I_{CS}}{\alpha_F} (e^{\frac{V_{BE}}{V_T}} - 1) - \alpha_R I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1)$$

$$\text{i.e. } \alpha_F I_E = \alpha_R I_{CS} (e^{\frac{V_{BE}}{V_T}} - 1) - \alpha_F \alpha_R I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1)$$

Now,  $I_E = I_C + I_B$ ,

$$\text{i.e. } \alpha_F I_C + \alpha_F I_B = \alpha_R I_{CS} (e^{\frac{V_{BE}}{V_T}} - 1) - \alpha_F \alpha_R I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1) \quad (15)$$

Rewriting eq<sup>n</sup> (14), (Eliminate  $V_{BE}$  terms)

$$\alpha_R I_{CS} (e^{\frac{V_{BE}}{V_T}} - 1) = I_C + I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1) \quad (16)$$

Substituting eq<sup>n</sup> (16) into eq<sup>n</sup> (15), we get 08

$$\alpha_F I_C + \alpha_F I_B = I_C + I_{CS} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) - \alpha_R \alpha_F I_{CS} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right)$$

$$\text{i.e. } I_{CS} \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) [1 - \alpha_R \alpha_F] + I_C (1 - \alpha_F) - \alpha_F I_B = 0$$

$$\text{i.e. } I_{CS} (1 - \alpha_R \alpha_F) \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) = \alpha_F I_B - I_C (1 - \alpha_F)$$

$$\text{i.e. } \left( e^{\frac{V_{BC}}{V_T}} - 1 \right) = \frac{\alpha_F I_B - I_C (1 - \alpha_F)}{I_{CS} (1 - \alpha_R \alpha_F)}$$

$$\therefore e^{\frac{V_{BC}}{V_T}} = \frac{\alpha_F I_B - I_C (1 - \alpha_F)}{I_{CS} (1 - \alpha_R \alpha_F)} + 1$$

INDERJIT SINGH

$$\therefore V_{BC} = V_T \ln \left[ \frac{\alpha_F I_B - I_C (1 - \alpha_F) + I_{CS} (1 - \alpha_F \alpha_R)}{I_{CS} (1 - \alpha_F \alpha_R)} \right]$$

(B)

$$V_{CE(sat)} = V_{BE} - V_{BC} \quad (\text{From eq<sup>n</sup> (A) \& (B), we get})$$

$$\text{i.e. } V_{CE(sat)} = V_T \ln \left[ \frac{I_C (1 - \alpha_R) + I_B}{\alpha_F I_B - (1 - \alpha_F) I_C} \times \frac{I_{CS}}{I_{ES}} \right]$$

$$V_{CE(sat)} = V_T \ln \left[ \frac{I_C (1 - \alpha_R) + I_B}{\alpha_F I_B - (1 - \alpha_F) I_C} \frac{\alpha_F}{\alpha_R} \right] \quad - C$$

INDERJIT SINGH

$$\left( \because \alpha_F I_{ES} = \alpha_R I_{CS} \right. \\ \left. \text{From eq<sup>n</sup> (8).} \right)$$



1. A BJT has following significant parameters 03R  
 at  $T = 300K$ ,

$$\alpha_F = 0.98, \alpha_R = 0.18, I_C = 2mA, I_B = 60\mu A$$

Calculate collector to emitter voltage at saturation.

Solution:

$$V_{CE(sat)} = V_T \ln \left[ \frac{I_C (1 - \alpha_R) + I_B}{\alpha_F I_B - (1 - \alpha_F) I_C} \left( \frac{\alpha_F}{\alpha_R} \right) \right]$$

$$\text{i.e. } V_{CE(sat)} = 0.026 \ln \left[ \frac{2 \times 10^{-3} (1 - 0.18) + 60 \times 10^{-6}}{0.98 \times 60 \times 10^{-6} - (1 - 0.98) 2 \times 10^{-3}} \left( \frac{0.98}{0.18} \right) \right]$$

$$V_{CE(sat)} \approx 0.16V \rightarrow \text{Ans}$$

Note: Because of log function,  $V_{CE(sat)}$  is not a strong function of  $I_C$  or  $I_B$ .

## \* NON-IDEAL EFFECTS IN BJT: 25/08/14 IIR

So far we have considered a BJT with

- a) uniform doped regions
  - b) low injection level
  - c) Constant emitter and base widths
  - d) Constant energy bandgap
  - e) Uniform current densities and
  - f) Junctions which are not in breakdown.
- } Ideal conditions for a BJT.


If any of these ideal conditions are not present, then the transistor properties will deviate from the ideal characteristics derived.

Various non-ideal effects <sup>that</sup> need to be investigated then for BJT are including;

- a) Base width modulation (Early effect)
- b) High level injection
- c) Non-uniform Base doping
- d) Breakdown voltage
- e) Emitter Bandgap narrowing.


## Base width modulation:

12

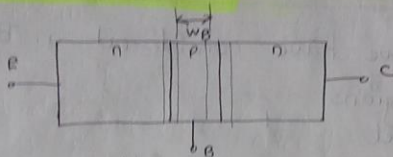

npn transistor

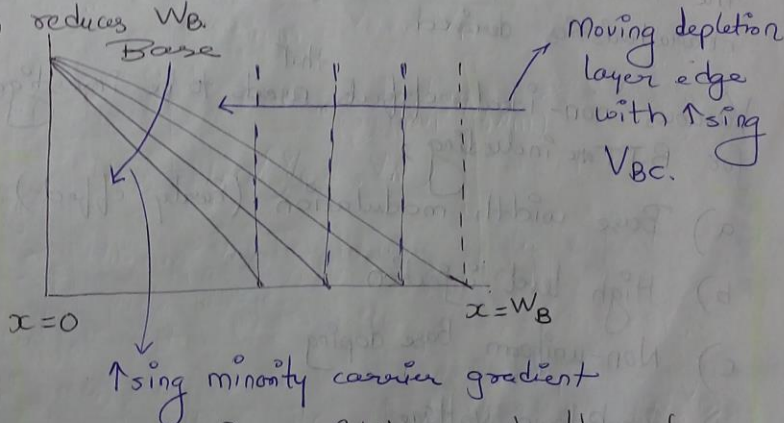- Uptill now we have assumed that base width ' $W_B$ ' was constant.
- However, ' $W_B$ ' is a function of B-C voltage  $V_{BC}$ , width of depletion region extending into the base region varies with  $V_{BC}$ .
- As R.B.  $V_{BC} \uparrow$  so, B-C depletion region width  $\uparrow$  so, which reduces  $W_B$ .



INDERJIT SINGH

Fig 1: Change in Base-width and the change in minority carrier gradient as the BC depletion region width changes.

A change in  $W_B$  will change collector current  $I_C$  as can be observed in fig 1.

That is, a reduction in base-width ( $W_B$ ) will cause the gradient in minority carrier to increase which in turn causes an increase in diffusion current. This effect is known as 'Base-width modulation' or 'Early effect'.

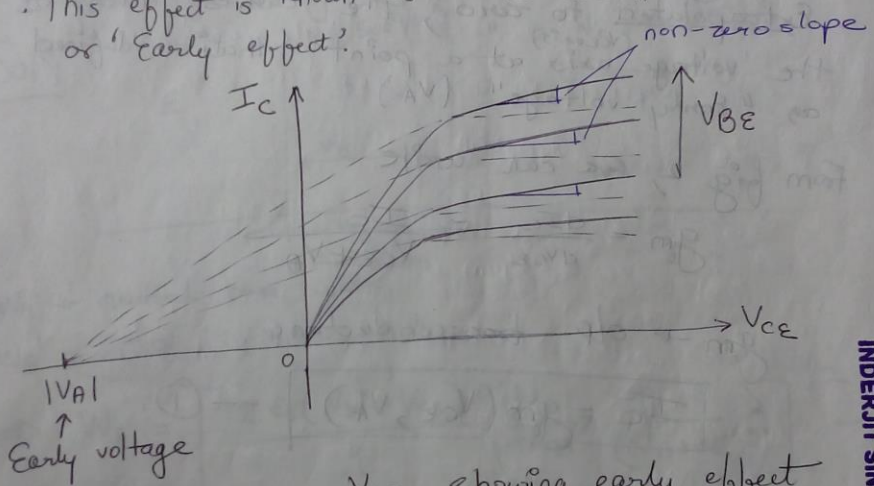


fig 2:  $I_C$  versus  $V_{CE}$  showing early effect and early voltage.

In most cases,  $V_{BE}$  constant is equivalent to constant base current. Ideally,  $I_C$  is independent of  $V_{CE}$  thus, slope of curve would be zero & hence o/p conductance of BJT would be zero.

(ie  $g_o = \frac{\Delta I_C}{\Delta V_{CE}} \approx 0$ )  $\rightarrow$  since  $\Delta I_C \Rightarrow$  constant (without BWM)

INDERJIT SINGH

14  
 However, "BWM" or "Early effect", produces a 'non-zero slope' & give rise to a finite o/p conductance ( $g = \frac{\Delta I_c}{\Delta V_{CE}}$ )

From fig 2, if "Ic characteristics" are extrapolated to zero, the curves intersect the voltage axis at a point that is defined as "Early voltage" ( $V_A$ )

From fig 2, we can write

$$g_o = \frac{dI_c}{dV_{CE}} \approx \frac{I_c}{V_{CE} + V_A}$$

$g_o \rightarrow$  o/p conductance.

$$\therefore \boxed{I_c = g_o (V_{CE} + V_A)} \quad \text{--- (1)}$$

Eqn (1) shows that collector current is now a function of C-E voltage or the CB voltage.

i.e.  $\boxed{V_{CE} = V_{BE} - V_{BC}}$

Summary:

As  $V_{BC} \uparrow$ ,  $W_B \downarrow$   
 $\downarrow W_B$  causes gradient in minority-carrier concentration to  $\uparrow$ , which causes an  $\uparrow$  in diffusion current.  
 $\therefore \beta$  also  $\uparrow$ .  
 $\therefore I_c \uparrow$  with  $\uparrow$ ing  $V_{CE}$   
 $\Rightarrow$  BWM