

D. J. SANGHVI COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELX302: ELECTRONIC DEVICES AND CIRCUITS 1 SEM III
ASSIGNMENT 03

10th October, 2017

[Total Marks: 80]

1. Assume any suitable data if necessary
2. Read the questions carefully before attempting
3. Questions to be attempted by B1 batch : 01,02,05,08,14,15,17,18
4. Questions to be attempted by B2 batch : 01,03,04,09,14,16,17,18
5. Questions to be attempted by B3 batch : 01,06,10,11,14,15,16,18
6. Questions to be attempted by B4 batch : 01,07,12,13,14,16,17,18
7. Date of submission: 14-10-2017
8. Hint: One can verify answers in LT Spice only for E- type MOSFETs

1. Consider the figure 1

✕ Input to amplifier is 20mV peak to peak voltage, with 1KHz frequency

- i) What type of circuit is this [1]
- ii) Find k_n [1]
- iii) Calculate the value of V_{GSQ} [1]
- iv) Calculate the value of I_{DQ} [1]
- v) Sketch the small signal AC equivalent of the figure 1 [1]
- vi) Calculate the value of g_m [1]
- vii) Find r_d [1]
- viii) Find the input impedance Z_i of the circuit [1]
- ix) Find the output impedance Z_o of the circuit [1]
- x) Calculate the voltage gain of the circuit [1]

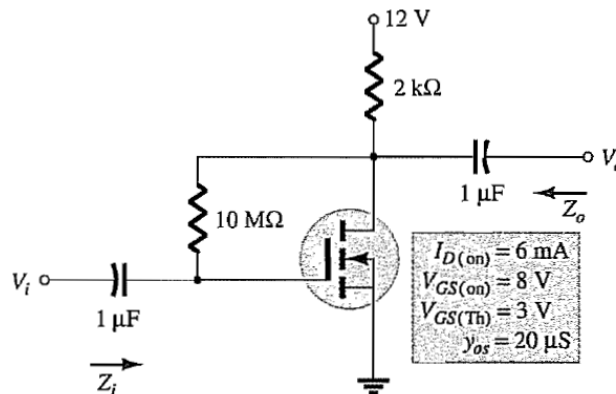


Figure 1: Question 1

2. Draw circuit diagram of common-source amplifier with voltage divider bias with un-bypassed source resistance R_S using n-channel E-MOSFET. Derive the expression for voltage gain, input resistance and output resistance. [10]
3. For the given circuit, find V_{GSQ} , I_{DQ} and voltage gain A_V with C_S and without C_S
 Given: $V_T = 1V, k_n = 1mA/V^2$ [10]

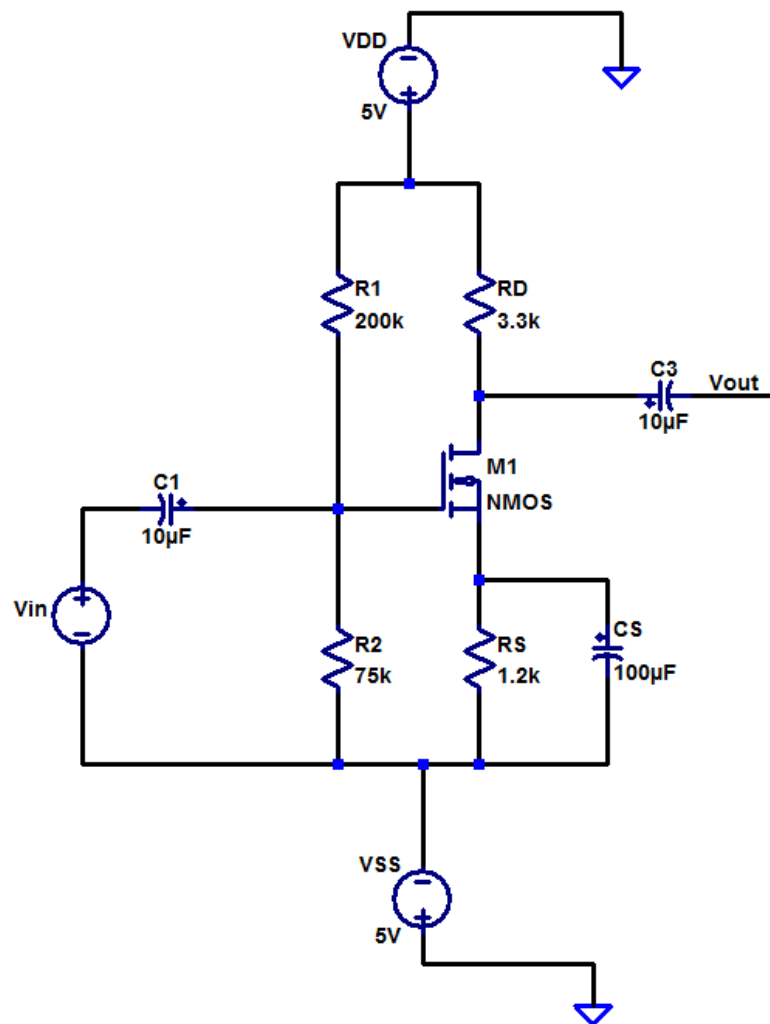


Figure 2: Question 3

4. Draw circuit diagram of common-source amplifier with voltage divider bias with C_S [10]
 using n-channel E-MOSFET. Derive the expression for voltage gain, input resistance
 and output resistance.

5. Determine V_o if $y_{os} = 20\mu S$

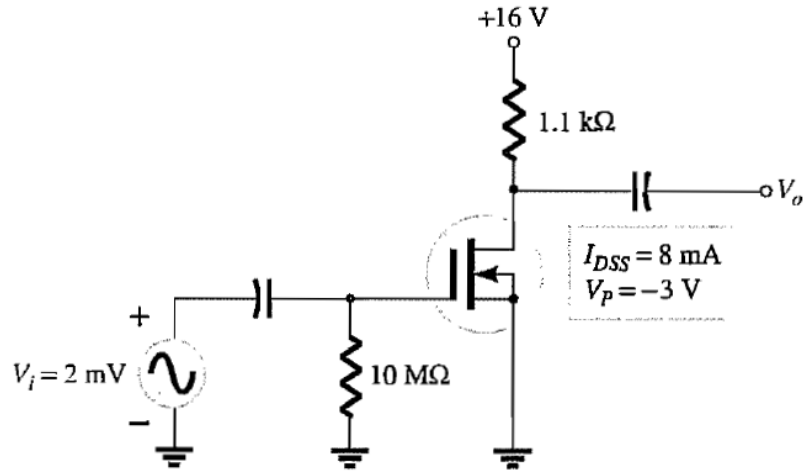


Figure 3: Question 5

6. What are different biasing circuits for E-MOSFET. Explain drain-feedback bias in detail. [10]

7. What are different biasing circuits for D-MOSFET. Explain voltage divider bias in detail. [10]

8. For the circuit shown find A_V , R_i and R_o [10]
 Given: $V_{GS(th)} = 3\text{ V}$, $I_{D(on)} = 5\text{ mA}$, $V_{GS(on)} = 6\text{ V}$, $r_d = 80\text{ K}$

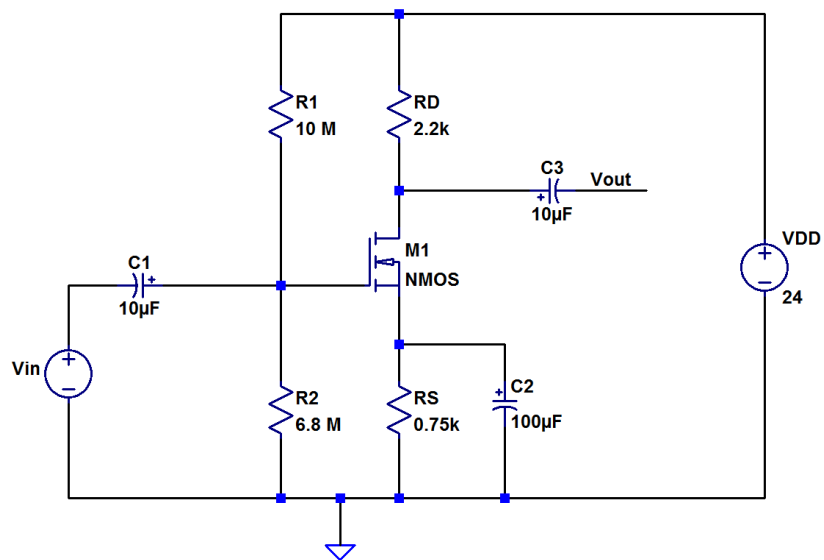


Figure 4: Question 8

9. Compare D-MOSFET and E-MOSFET considering construction and characteristics. [10]

10. Draw circuit diagram of common-source amplifier with voltage divider bias with un-bypassed source resistance R_S using D-MOSFET. Derive the expression for voltage gain, input resistance and output resistance [10]
11. For the circuit shown find A_V , R_i and R_o [10]
 Given: $V_{GS(th)} = 3V$, $K = 0.4 \times 10^{-3}$, $r_d = 80K\Omega$

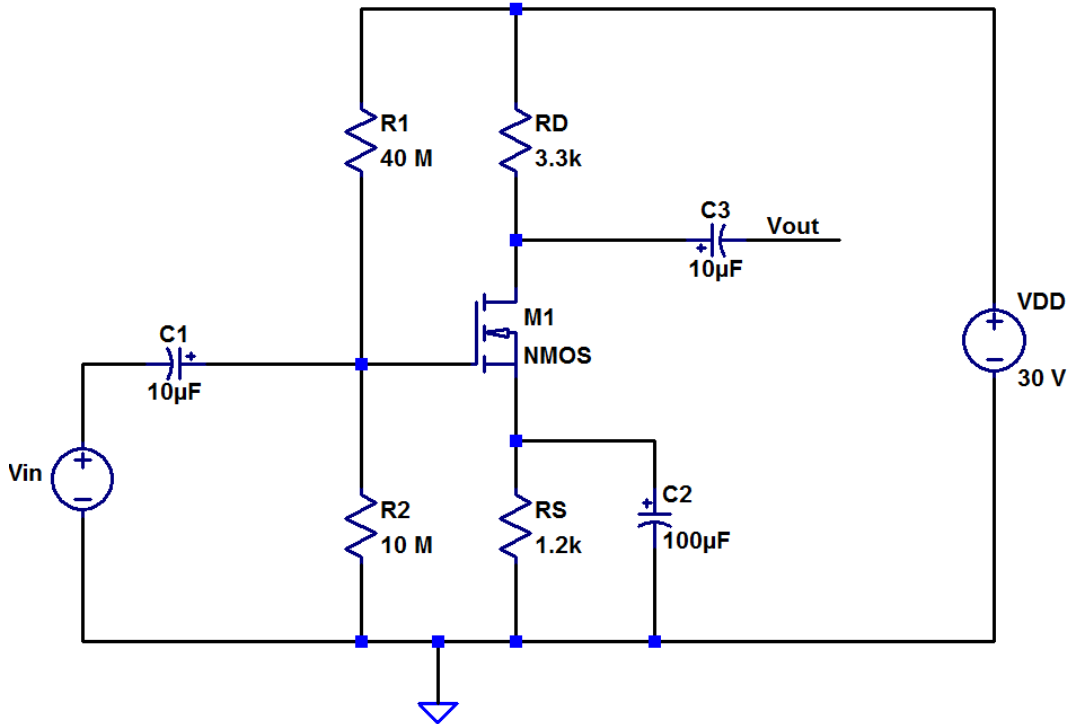


Figure 5: Question 11

12. Draw circuit diagram of common-drain amplifier using MOSFET. Derive the expression for voltage gain, input resistance and output resistance. [10]
13. Draw circuit diagram of common-gate amplifier using MOSFET. Derive the expression for voltage gain, input resistance and output resistance. [10]
14. Design an N-channel Enhancement type MOSFET using voltage-divider biasing for the following specifications: [10]
 $I_{DQ} = 5mA$, $V_{DSQ} = 5V$
 MOSFET parameters given are: $K_n = 20mA/V^2$, $V_{TN} = 1V$

15. Determine Z_i , Z_o and A_v if $r_d = 60K\Omega$

[10]

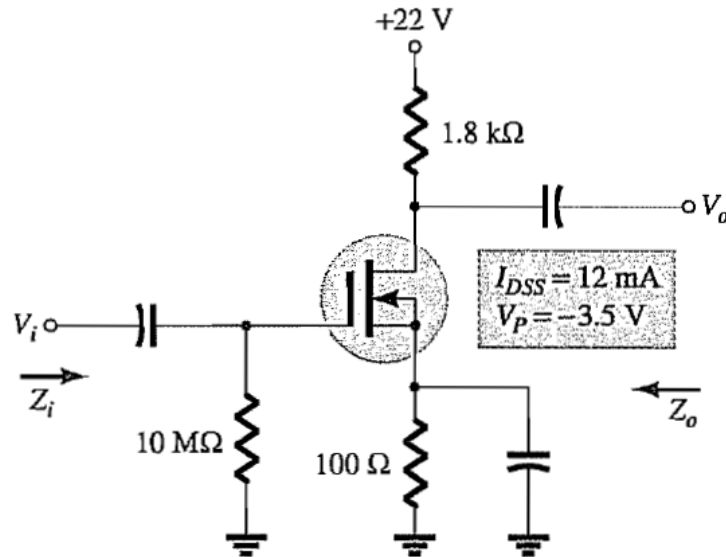


Figure 6: Question 15

16. Determine Z_i , Z_o and A_v

[10]

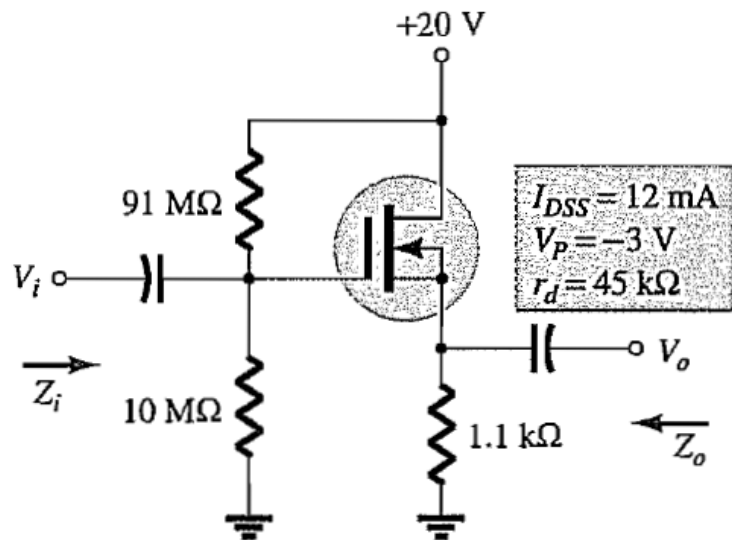


Figure 7: Question 16

17. For the NMOS common-source amplifier, the transistor parameters are: [10]

MOSFET parameters given are: $K_n = 1\text{mA/V}^2$, $V_{TN} = 0.8\text{V}$ and $\lambda = 0$

The circuit parameters are: $V_{DD} = 5\text{V}$, $R_S = 1\text{K}\Omega$, $R_D = 4\text{K}\Omega$, $R_1 = 225\text{K}\Omega$, $R_2 = 175\text{K}\Omega$

- Calculate the quiescent values I_{DQ} and V_{DSQ}
- Determine the small-signal voltage gain for $R_L = \infty$
- Determine the value of R_L that will reduce the small-signal voltage gain to 75 % of the value found in part (b)

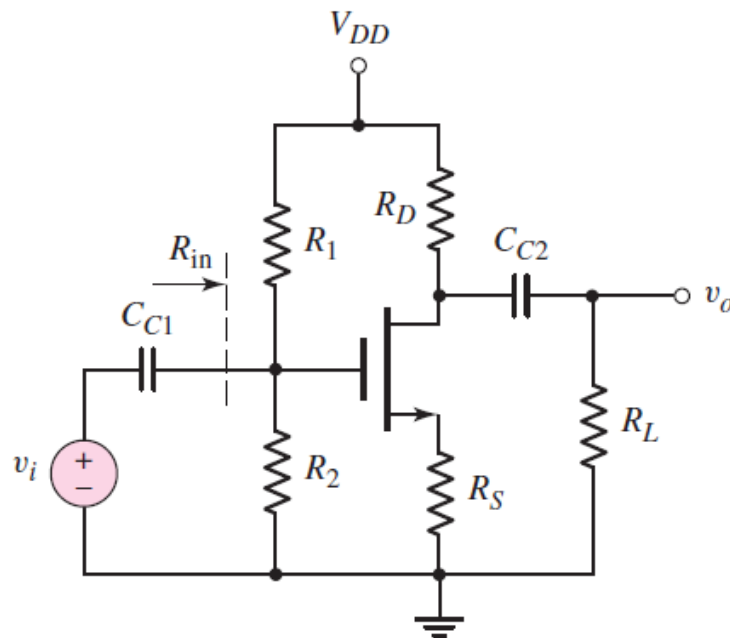


Figure 8: Question 17

18. Compare CS, CG and CD configuration using NMOS-E type w.r.t following parameters: [10]

- Input impedance
- Circuit diagram
- Output impedance
- Voltage gain
- Phase shift between input and output
- Application
