

D. J. SANGHVI COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELX302: ELECTRONIC DEVICES AND CIRCUITS I SEM III

Home Work 01

15th September, 2017

[Maximum Benefit: Knowledge]

1. Attempt the following questions

1. For the voltage-divider configuration of figure 1, determine:

1. I_{DQ} , V_{GSQ} and V_{DSQ}

2. V_D and V_S

MOSFET parameters: $K_n = 4\text{mA/V}^2$, $V_{TN} = 1.2\text{V}$

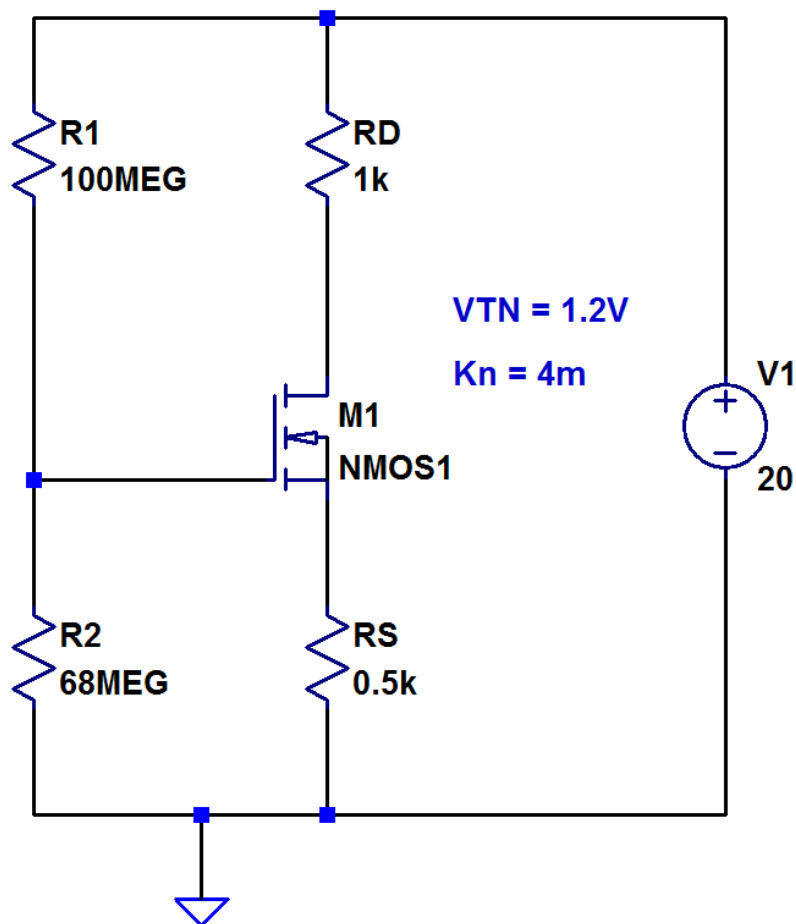


Figure 1: Question 1

2. For the configuration of figure 2, determine:

1. I_{DQ} , V_{GSQ} and V_{DSQ}
2. V_D and V_S

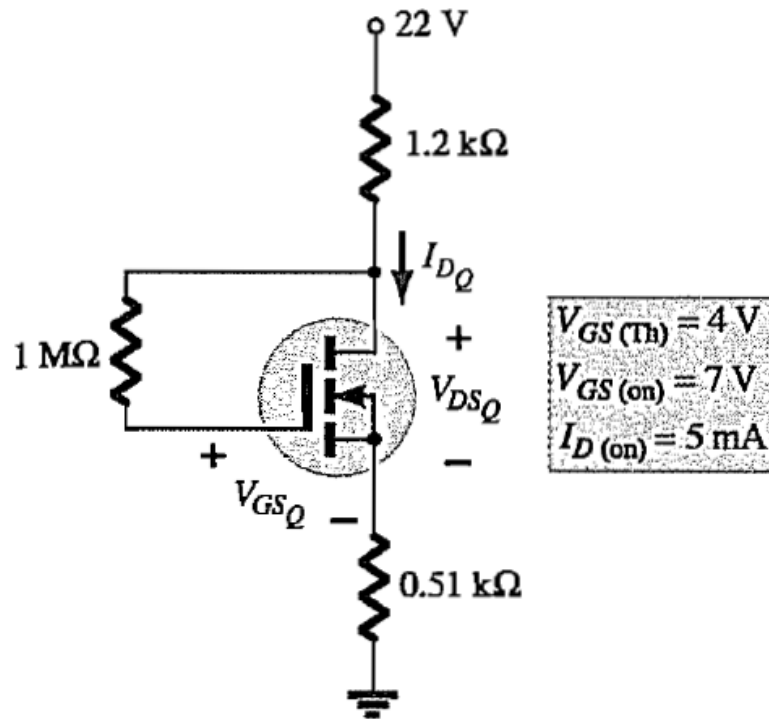


Figure 2: Question 2

3. For the self bias NMOS-D configuration of figure 3, determine:
1. I_{DQ} and V_{GSQ}
 2. V_D and V_{DS}

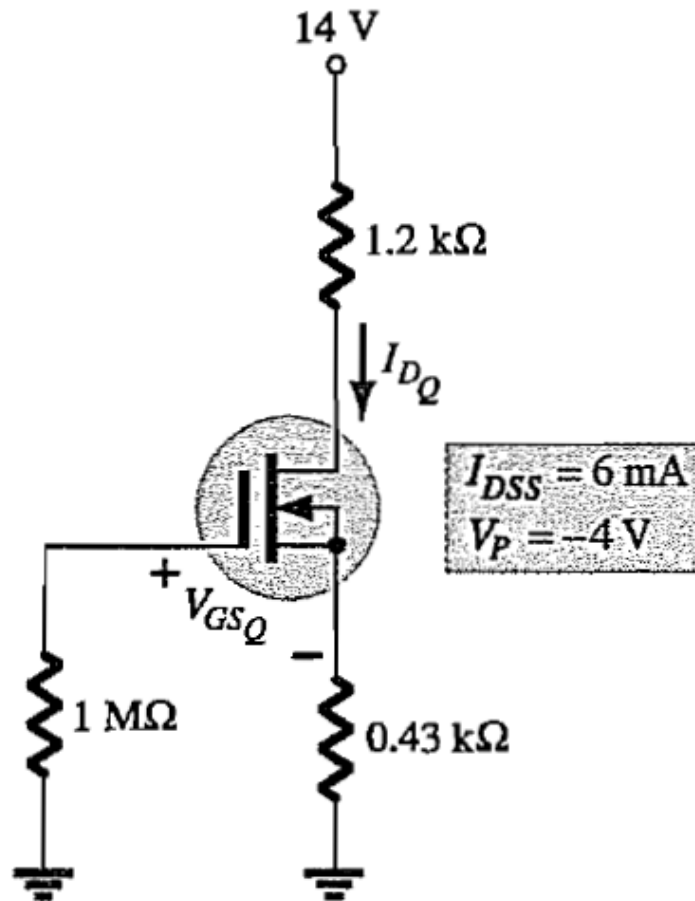


Figure 3: Question 3

4. For the configuration of figure 4, determine:

1. I_{DQ} and V_{GSQ}
2. V_D and V_{DS}

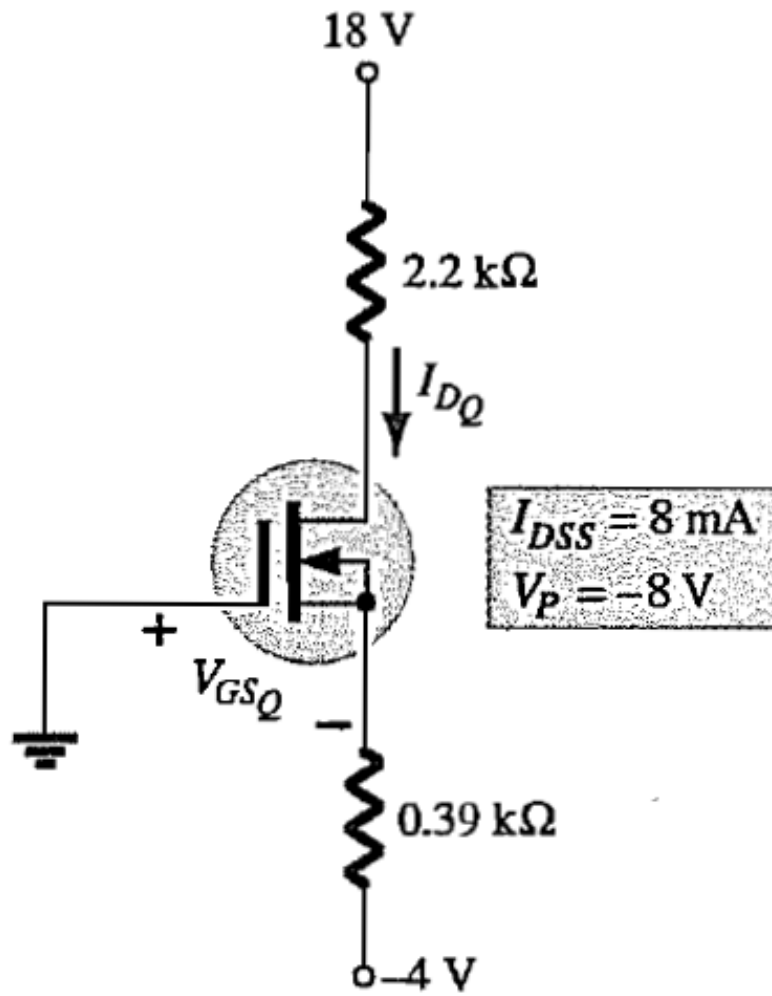


Figure 4: Question 4

5. For the configuration of figure 5, determine:

1. I_{DQ} and V_{GSQ}
2. V_D and V_{DS}

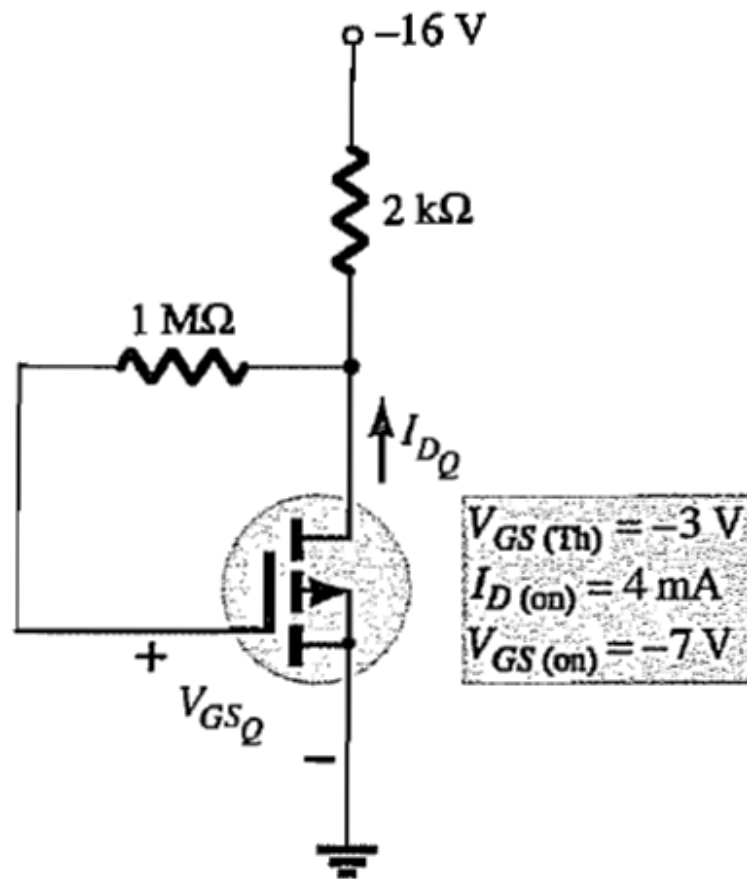


Figure 5: Question 5

6. Design a voltage-divider bias network using depletion-type MOSFET with $I_{DSS} = 10mA$ and $V_P = -4V$ to have a Q point at $I_{DQ} = 2.5mA$ using a supply of 24V. In addition, set $V_G = 4V$ and use $R_D = 2.5R_S$ with $R_1 = 22M\Omega$. Use standard values.
7. Design a drain feedback bias network using an enhancement type MOSFET with $V_{TN} = 4V$ and $k_n = 0.5 \times 10^{-3} \frac{A}{V^2}$ to have a Q point of $I_{DQ} = 6mA$. Use a supply of 16V and standard values.
