

**D. J. SANGHVI COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**EXL302: ELECTRONIC DEVICES AND CIRCUITS 1 SEM III**  
**MID TERM 2**

11<sup>th</sup> October, 2017

[Total Marks: 20]

1. Attempt all the questions for 20 marks
2. Read the questions carefully before attempting
3. Don't rewrite the question while answering, only answers have to be written.

1. Consider the circuit 1

✕ Input to amplifier is 20mV peak to peak voltage, with 1KHz frequency

- i) What type of circuit is this [1]
- ii) Calculate the value of  $V_{GSQ}$  [1]
- iii) Calculate the value of  $I_{DQ}$  [1]
- iv) Sketch the small signal AC equivalent of the circuit 1 [1]
- v) Calculate the value of  $g_m$  [1]
- vi) Find the input impedance  $Z_i$  of the circuit [1]
- vii) Find the output impedance  $Z_o$  of the circuit [1]
- viii) Calculate the voltage gain of the circuit [1]
- ix) If input is 20mV p-p, calculate the output voltage of the circuit [1]
- x) Plot input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms of the circuit [1]

 


Figure 1: Question 1

2. a) Design an N-channel Enhancement type MOSFET using voltage-divider biasing [5]  
for the following specifications:  
 $I_{DQ} = 5mA$ ,  $V_{DSQ} = 5V$   
MOSFET parameters given are:  $K_n = 25mA/V^2$ ,  $V_{TN} = 1V$

OR

- a) Mention the various DC biasing schemes for n-channel E-type MOSFET. [1]  
b) Draw voltage divider bias circuit using n-channel enhancement type MOSFET [1+2]  
and write the expressions of  $V_{DSQ}$ ,  $V_{GSQ}$  and  $I_{DQ}$ .  
c) Draw the DC load line for the voltage divider biasing scheme along with equation [1]  
for DC load line.
3. a) Draw voltage divider bias circuit using NPN BJT and derive the expression of [1+3]  
 $V_{CEQ}$  and  $I_{CQ}$   
b) For an NPN BJT to be in active region, how should be the EB junction and BC [1]  
junction be biased.

\*\*\*\*\*