

### 6.3 Design of full-wave rectifier with LC and pi filter

01  
10/8/17

Design 01:

Design a full-wave center tapped rectifier to meet the following specifications

- Output voltage :  $12\text{ V dc}$
- Load current (max):  $500\text{ mA}$
- Ripple voltage must be less than  $60\text{ mV}$

The above design should employ

- i) L section LC filter
- ii)  $\pi$  filter

Solution:-

A] i] Given data:


$$V_{dc} = 12\text{ V}$$

$$I_{dc} \text{ (or } I_L) = 500\text{ mA}$$

$$V_{ac \text{ ripple}} \text{ (or } V_{r \text{ rms}}) = 60\text{ mV}$$

Assume :- [ Input voltage :  $230\text{ V}_{rms}$  @  $50\text{ Hz}$  ]  
(ac mains)

2] Circuit diagram:-

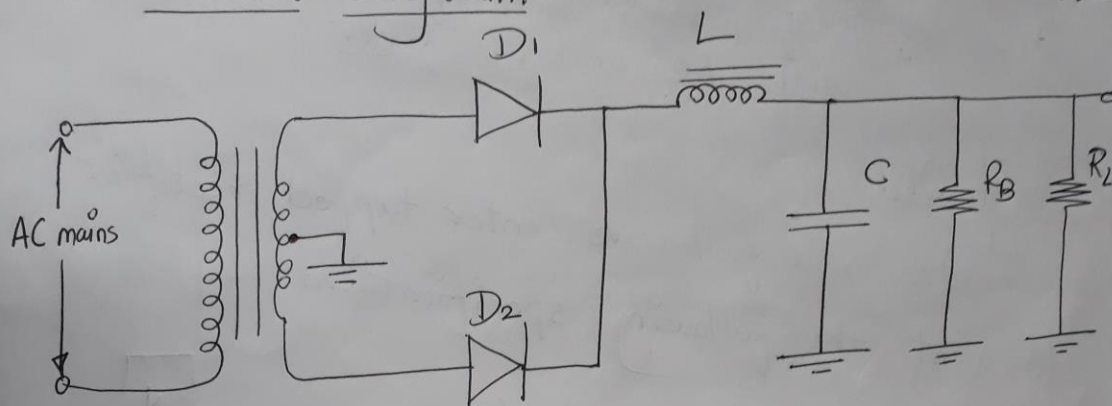

3) Selection of  $R_L$ :

$$R_L = \frac{V_{dc}}{I_{dc}} = \frac{12V}{0.5A} = 24\Omega$$

Power rating for load resistor  $R_L$ :

$$P_{R_L} = \frac{V_{dc}^2}{R_L} = \frac{(12)^2}{24} = 6W$$

Selecting  $R_L = 24\Omega / 6W$

Its wattage rating

#### 4) Selection of L and C :-

03

Ripple factor for an LC filter is given by,

$$\gamma = \frac{1}{6\sqrt{2} \omega^2 LC} \quad - (1)$$

Also,  $\gamma = \frac{V_{ac, rms}}{V_{dc}}$

(Assume  $f = 50\text{Hz}$ )

ie  $\gamma = \frac{60 \times 10^{-3}}{12} = 0.005$

From eq<sup>n</sup> (1),

$$0.005 = \frac{1}{6\sqrt{2} \omega^2 LC}$$

ie  $LC = \frac{1}{0.005 \times 6\sqrt{2} \times (2\pi \times 50)^2}$

$$LC = 2.388 \times 10^{-4} \quad - (2)$$

• We know, critical inductance value,

04

$$L_c \geq \frac{R_L}{3\omega}$$

$$\text{i.e. } L_c \geq \frac{24}{3 \times 2\pi \times 50}$$

$$L_c \geq 0.0254 \text{ H}$$

$$\therefore \text{ Select } L = 10L_c = 0.254 \text{ H}$$

$$L = 254 \text{ mH}$$

$$\text{Select } L = 250 \text{ mH (standard value) / 1 A rating}$$

It's current rating!  
(Selected more than 500mA)



From (2),

05

$$LC = 2.388 \times 10^{-4}$$

$$C = \frac{2.388 \times 10^{-4}}{250 \times 10^{-3}} = 956 \mu F$$

Select $C = 1000 \mu F$ (standard value) / <u>30V</u>
---

It's voltage rating (Selected more than  $V_{secondary}$ )

5) Selection of  $R_B$ : (Bleeder resistor)

$$R_B < 3\omega L$$

$$< 3 \times 2\pi \times 50 \times 250 \times 10^{-3}$$

$$< 235.6 \Omega$$

$$\therefore R_B \approx 220 \Omega$$

Power rating:  $P_{RB} = \frac{V_{dc}^2}{220} \approx 0.65W$

Select $R_B \approx 220 \Omega$ (standard value) / 1W
---

6) Selection of transformer :-

06

$$V_{dc} \approx \frac{2V_m}{\pi}$$

$$V_m = \frac{12 \times \pi}{2} \approx \underline{18.85V}$$

• Allowing for 20% drop across the resistance of secondary winding, we have


$$V_{m(sec)} = 1.2 \times 18.85 \approx \underline{22.62V}$$

$$\therefore V_{rms(sec)} = \frac{22.62}{\sqrt{2}} \approx \underline{15.99V}$$

Since, it's a center-tapped transformer, the two secondary rms voltages will be 16-0-16V

• I/p to transformer is from ac mains i.e. 230V @ 50Hz

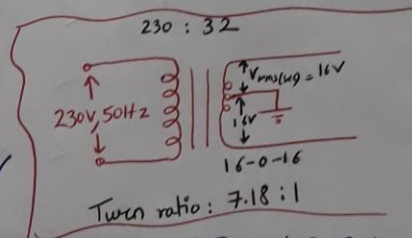$\therefore$  Turn ratio of transformer is  $\boxed{7.18:1}$   
 (230:32) total secondary rms voltage



Selecting a transformer with 16-0-16V/1A rating; turn ratio 7.18:1

### 7) Selection of diodes:-


07

a) Forward current rating must be equal to or greater than maximum Load current i.e.  $500\text{mA}$

b) PIV rating of diodes must be greater than minimum calculated value of  $2V_m$  i.e.  $2 \times 22.6 = 45.2\text{V}$

Select diodes with ratings  $90\text{V}/500\text{mA}$ .

### 8) Designed ckt is:-

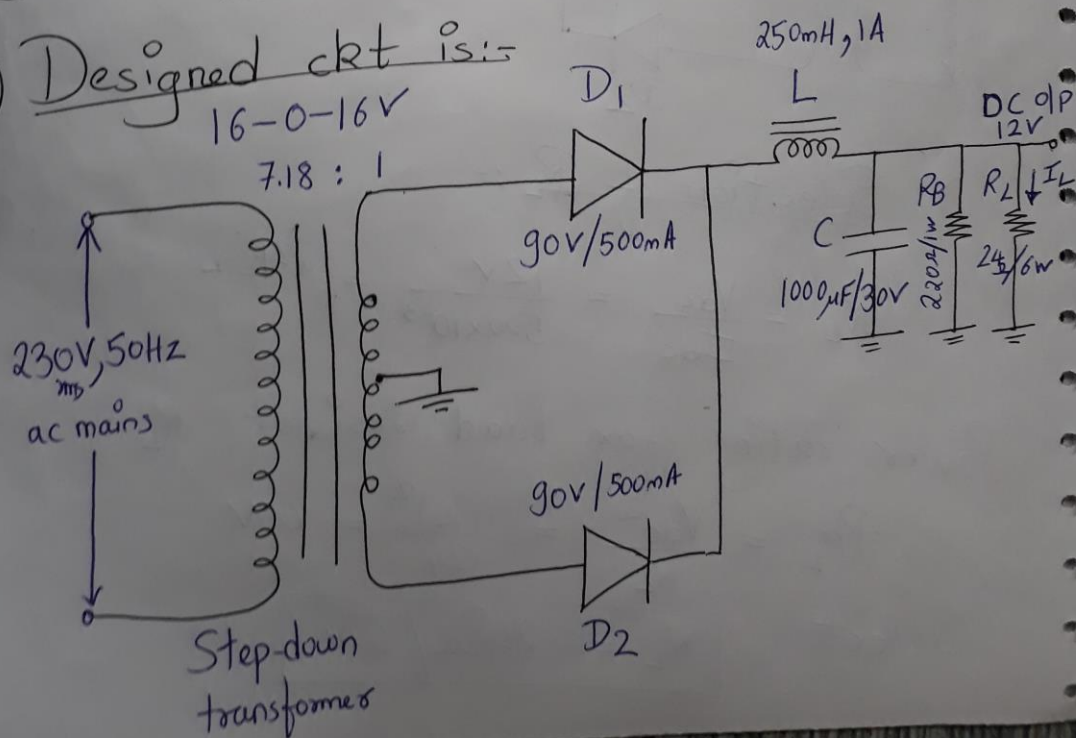

B] Design using  $\Pi$  filters :-

08


1) Given data:-

$$V_{dc} = 12V$$

$$I_{dc} = I_L = 500mA$$

$$V_{ac\,rms} = 60mV$$

2) Circuit diagram:-

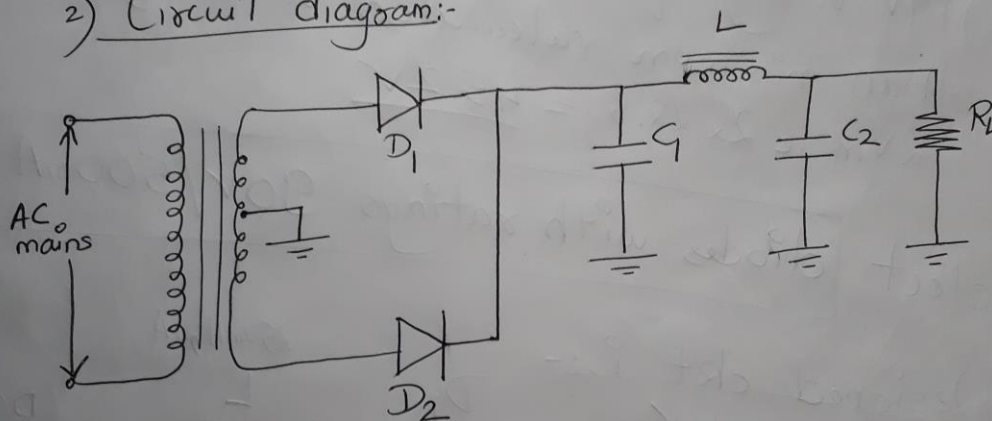

3) Selection of  $R_L$  :-

$$R_L = \frac{V_{dc}}{I_{dc}} = \frac{12V}{500 \times 10^{-3}} = 24\Omega$$

Power rating for load resistor  $R_L$  :

$$P_{R_L} = \frac{V_{dc}^2}{R_L} = \frac{(12)^2}{24} = 6W$$

Select  $R_L = 24\Omega / 6W$



4) Selection of L and C :-

09

Ripple factor for a pi filter is,

$$\gamma = \frac{1}{4\sqrt{2} \omega^3 L C_1 C_2 R_L}$$

$$\gamma = \frac{1}{4\sqrt{2} (2\pi \times 50)^3 L C_1 C_2 R_L}$$

$$\gamma = \frac{5.7 \times 10^{-9}}{L C_1 C_2 R_L} \quad \text{--- (1)}$$

$$\text{Now, } \gamma = \frac{V_{ac, \text{rms ripple}}}{V_{dc}} = \frac{60 \text{ mV}}{12} = 0.005$$

$$\text{Assuming } L = 250 \text{ mH} / 1 \text{ A}$$

and let  $C_1 = C_2 = C$

$$\text{From (1), } 0.005 = \frac{5.7 \times 10^{-9}}{C^2 \times 24 \times 250 \times 10^{-3}}$$

$$C = 436 \mu\text{F}$$

$$\text{Select } C_1 = C_2 = 470 \mu\text{F}_{(\text{std})} / 40 \text{ V}$$

↗ shd be  $> V_m$

5) Selection of transformer:-

10

Output dc voltage of  $\pi$  filter is given by,

$$V_{dc} = V_m - \frac{I_{dc}}{4fC} \quad \left( \because I_{dc} = \frac{V_{dc}}{R_L} \right)$$

$$V_{dc} = V_m - \frac{V_{dc}}{4fCR_L}$$

$$\therefore V_m = V_{dc} \left( 1 + \frac{1}{4fCR_L} \right)$$

$$V_m = 12 \left( 1 + \frac{1}{4 \times 50 \times 470 \mu F \times 24} \right)$$

$$\underline{V_m \approx 17.32 \text{ V}}$$

Allowing for 20% drop across  $R_s$ ,  $R_f$  and  $R_{choke}$ 

$$V_m = 1.2 \times 17.32 = \underline{20.78 \text{ V}}$$

$$\therefore V_{rms(sec)} = \frac{V_m}{\sqrt{2}} = \underline{14.69 \text{ V}}$$

Select transformer with 15-0-15V/1A and  
turn ratio 7.66:1

$$\left. \begin{array}{l} \text{Transformer} \\ 230\text{V} : 32\text{V} \\ \text{ie } 7.66:1 \\ N_p : N_{sec} \end{array} \right\}$$

6) Selection of diodes:-

$$PIV \approx 2V_m = 2 \times 20.78V = 41.56V$$

Current flowing through both diodes is 500mA in a complete cycle, so current flowing through each diode is  $I_D = \frac{I_L}{2} = \frac{500mA}{2} = 250mA$

Select diodes with ratings 80V/500mA

7) Designed circuit is:-

