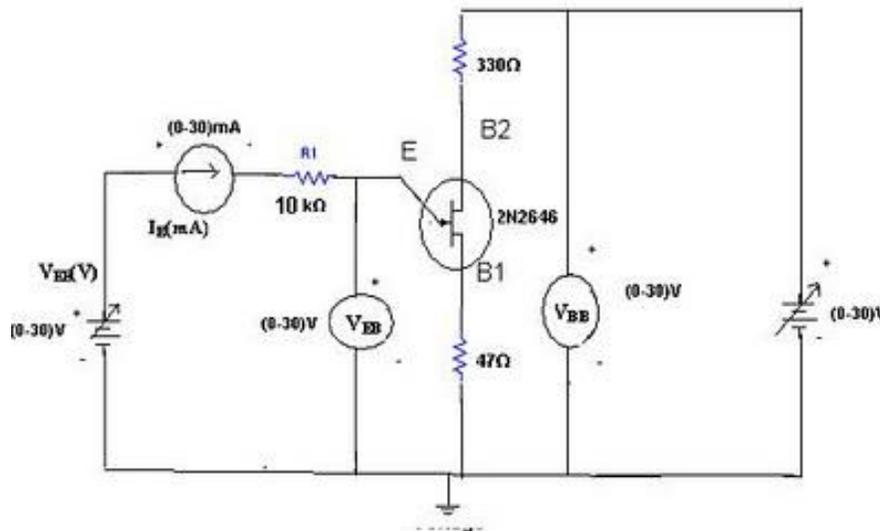


EXPERIMENT 11: Uni-junction transistor (UJT) CHARACTERISTICS

AIM : To observe the characteristics of UJT and to calculate the Intrinsic Stand-Off Ratio (η).

APPARATUS: Regulated Power Supply (2Nos) (0-30V, 1A) , UJT 2N2646, Resistors 10k Ω , 47 Ω , 330 Ω , Multimeters ,Breadboard and Connecting Wires


CIRCUIT DIAGRAM:



THEORY:

A Unijunction Transistor (UJT) is an electronic semiconductor device that has only one junction. It has three terminals an emitter (E) and two bases (B1 and B2). The base is formed by lightly doped n-type bar of silicon. Two ohmic contacts B1 and B2 are attached at its ends. The emitter is of p-type and it is heavily doped. The resistance between B1 and B2, when the emitter is open-circuit is called interbase resistance. The original UJT, is a simple device that is essentially a bar of N type semiconductor material into which P type material has been diffused somewhere along its length.

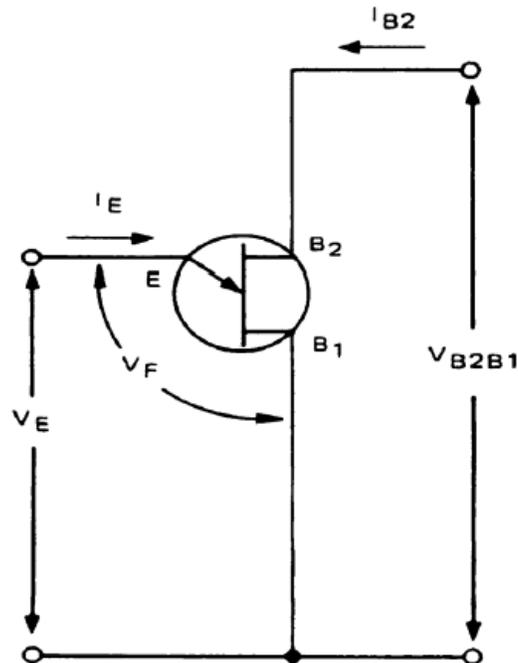
**UNIUNCTION TRANSISTOR SYMBOL
AND NOMENCLATURE**



The UJT is biased with a positive voltage between the two bases. This causes a potential drop along the length of the device. When the emitter voltage is driven approximately one diode voltage above the voltage at the point where the P diffusion (emitter) is, current will begin to flow from the emitter into the base region. Because the base region is very lightly doped, the additional current (actually charges in the base region) causes (conductivity modulation) which reduces the resistance of the portion of the base between the emitter junction and the B2 terminal. This reduction in resistance means that the emitter junction is more forward biased, and so even more current is injected. Overall, the effect is a negative resistance at the emitter terminal.

This is what makes the UJT useful, especially in simple oscillator circuits. When the emitter voltage reaches V_p , the current starts to increase and the emitter voltage starts to decrease. This is represented by negative slope of the characteristics which is referred to as the negative resistance region, beyond the valley point, V_{EB} proportional to I_E .

UJT Characteristic Curve

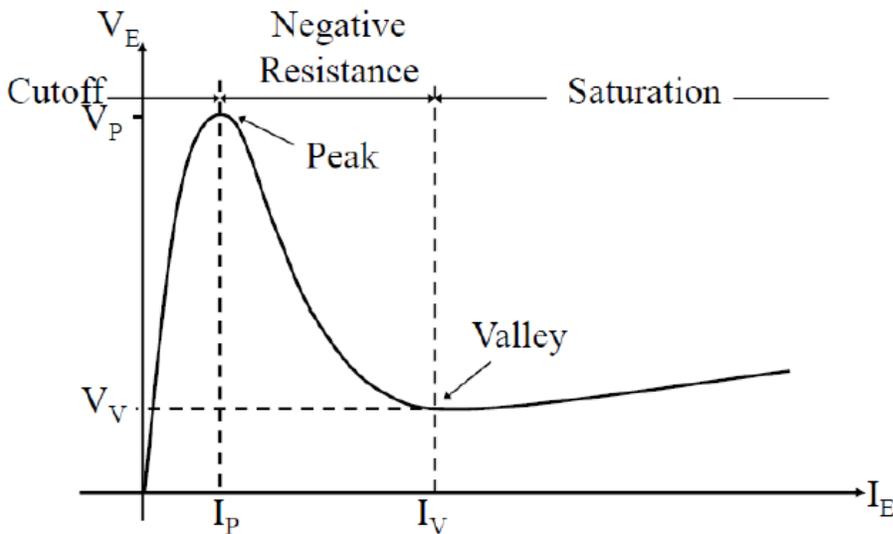

PROCEDURE:

1. Connection is made as per circuit diagram.
2. Output voltage is fixed at a constant level and by varying input voltage corresponding emitter current values are noted down.
3. This procedure is repeated for different values of output voltages.
4. All the readings are tabulated and Intrinsic Stand-Off ratio is calculated using

$$\eta = (V_p - V_D) / V_{B2B1}$$
5. A graph is plotted between V_E and I_E for different values of V_{B2B1} .

OBSEVATIONS:

$V_{B2B1}=2V$		$V_{B2B1}=3V$	
$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$

CALCULATIONS:

$$V_P = \eta V_{B2B1} + V_D$$

$$\eta = (V_P - V_D) / V_{B2B1}$$

$$\eta = (\eta_1 + \eta_2) / 2$$

APPLICATION: UJT can be used as trigger device for SCR's. traics and other applications including sawtooth generator , phase control and timing circuits.

CONCLUSION:

DISCOFELEX