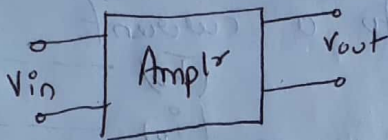


JFET amplifiers

01
16/10/19

Module 5.1 : Understanding concept of amplification with reference to transfer / o/p characteristics of JFET

• Amplifier requirements :



1) Gain should be high
eg voltage gain of a voltage amplifier \rightarrow high

2) I/P impedance


3) O/P impedance

4) Linearity (o/p should be linear w.r.t I/P)

• JFET as a device should amplify \rightarrow small time-varying signals.

This condition must be satisfied for JFET amplifiers to be Linear


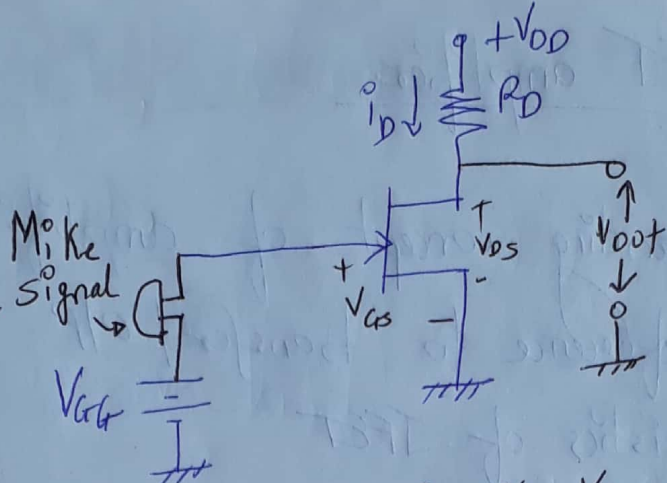
• Next, we need to superimpose small AC sig with DC? why DC biasing is required \rightarrow So that JFET wakes up & works in proper mode i.e. saturation \rightarrow so that it is used as amplifier.



It acts a small time-varying ΔI_D $(V_{mike} \approx V_m \sin \omega t)$

→ JFET acts as: voltage-dependent current source

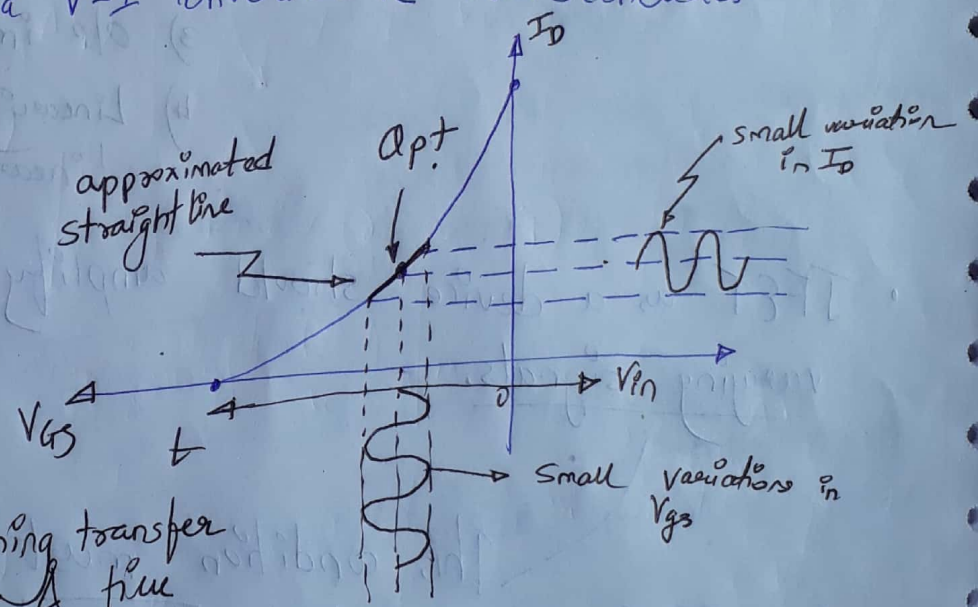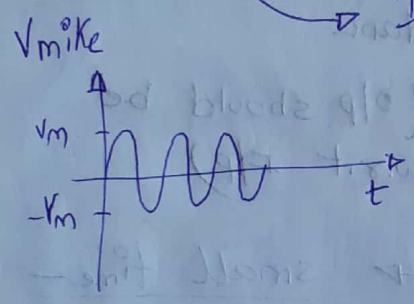"converts" a voltage to a current
 (V_{gs}) — DC quantity
 (I_D) — DC quantity
 (i_D) — AC quantity
 It's a V-I converter i.e. Transconductor




→ Here, the idea is to consider small segment of exponential curve to be

Linear

Combining transfer curve & time response.

i.e.

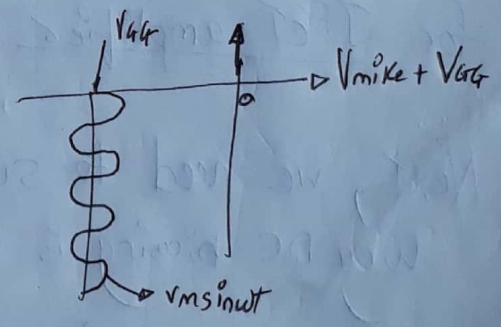

So, our ΔI_D should be within this linear segment → Hence, called as small sig

• Concept of transconductance


From graph,

$$g_m = \left. \frac{dI_D}{dV_{GS}} \right|_{opt}$$

slope of I_D vs V_{GS} characteristics

Unit: $\frac{1}{\Omega}$ or $\frac{mA}{V}$

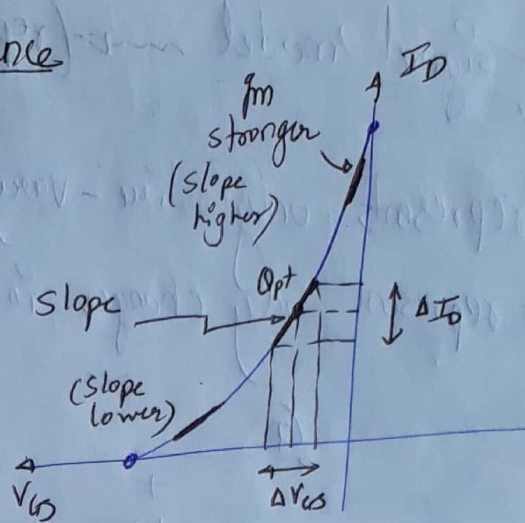ie $g_m = \frac{\Delta I_D}{\Delta V_{GS}}$



Powerful

--- Concept

$$\Delta I_D = g_m \Delta V_{GS}$$

small changes in I_D

slope a constant

small changes in V_{GS}

It suggests that gate to source voltage controls the drain to source current in a JFET

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\frac{dI_D}{dV_{GS}} = -\frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

--- Mathematically


$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

ie


$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$V_{GS} \approx \Delta V_{GS}$
--- here varying

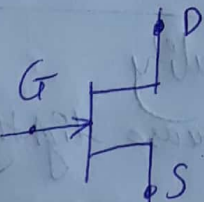Now, we are ready to draw small-signal model of JFET



⇒

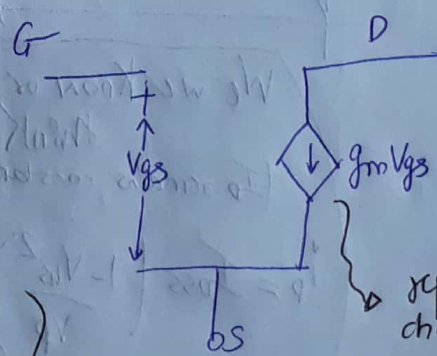


→ Gate to source is open ckt!

{ I/P impedance of a JFET is high, hence $I_G \approx 0$, since G-S junction of a JFET is always reverse-bias }

represents change in I_D
ie $\Delta I_D \approx g_m \Delta V_{GS}$

Small-signal model \rightarrow (represents only time-varying quantities) Δ


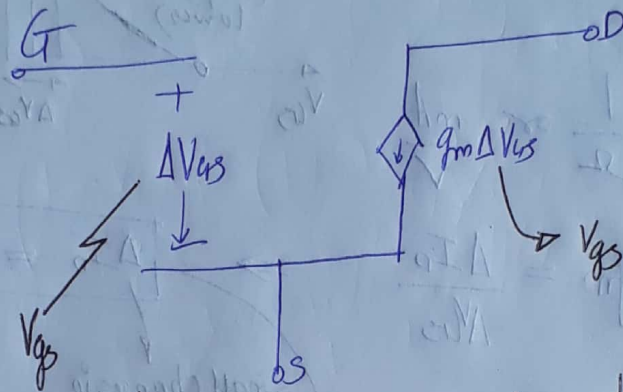
\rightarrow represents only time-varying components
 \rightarrow represent only changes in parameters (voltage V_{GS} , current i_D)



Small-sig model of JFET suggests that the drain current fluctuations (Δi_D) is equal to V_{GS} fluctuation (ΔV_{GS}) times the slope (g_m)

• Small-sig op resistance/impedance (r_o or r_d):

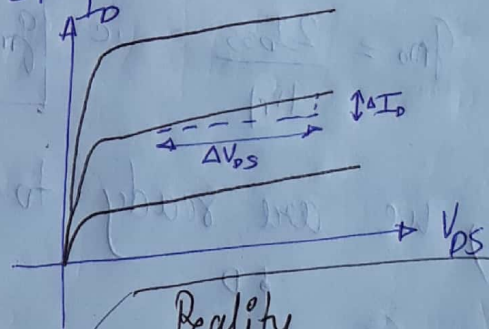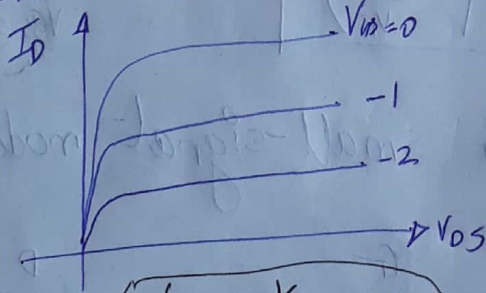Let's consider op characteristics of JFET



We we know or think (I_D remains constant)

$$i_D = I_{DSS} \left(1 - \frac{V_{GS}^2}{V_P^2} \right)$$

Reality (I_D increase slightly with V_{GS})

$$i_D = I_{DSS} \left(1 - \frac{V_{GS}^2}{V_P^2} \right) (1 + \lambda V_{GS})$$

λ - channel length modulation parameter

From graph, ($I_D - V_{DS}$)

Slope = $\frac{\Delta I_D}{\Delta V_{DS}}$

$$\frac{1}{\text{slope}} = \frac{\Delta V_{DS}}{\Delta I_D} = r_o \text{ or } r_d$$

small-sig o/p resistance of a JFET biased in saturation region.

ie $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 (1 + \lambda V_{DS})$

$\frac{dI_D}{dV_{DS}} = \lambda I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$\frac{dI_D}{dV_{DS}} = \lambda I_{DQ}$


ie $\frac{dV_{DS}}{dI_D} = \frac{1}{\lambda I_{DQ}}$

ie $r_o \text{ or } r_d = \frac{1}{\lambda I_{DQ}}$

small-sig o/p resistance

We need to include this in small-sig model, (We connect r_d betⁿ o&s)

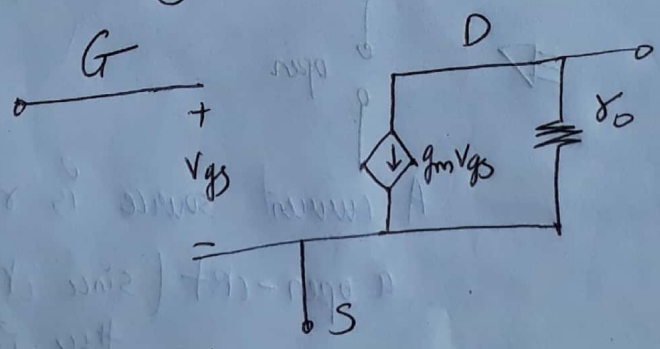Complete small-sig model of n-JFET ----- long calculation




We have small-sig model of JFET finally!

→ Small-signal model of constant sources

(they don't change with time)

(ie their variation in time is zero)

1) Constant voltage source

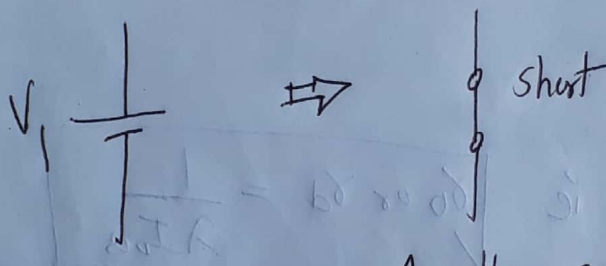

A voltage source (DC) is represented by a short (since changes in voltage with time is zero)

2) Constant current source




A current source is represented by an open-circuit (since changes in current with time is zero)

AC Analysis of JFET amplifiers:-

01
11/10/19

1. Common Source amplifier

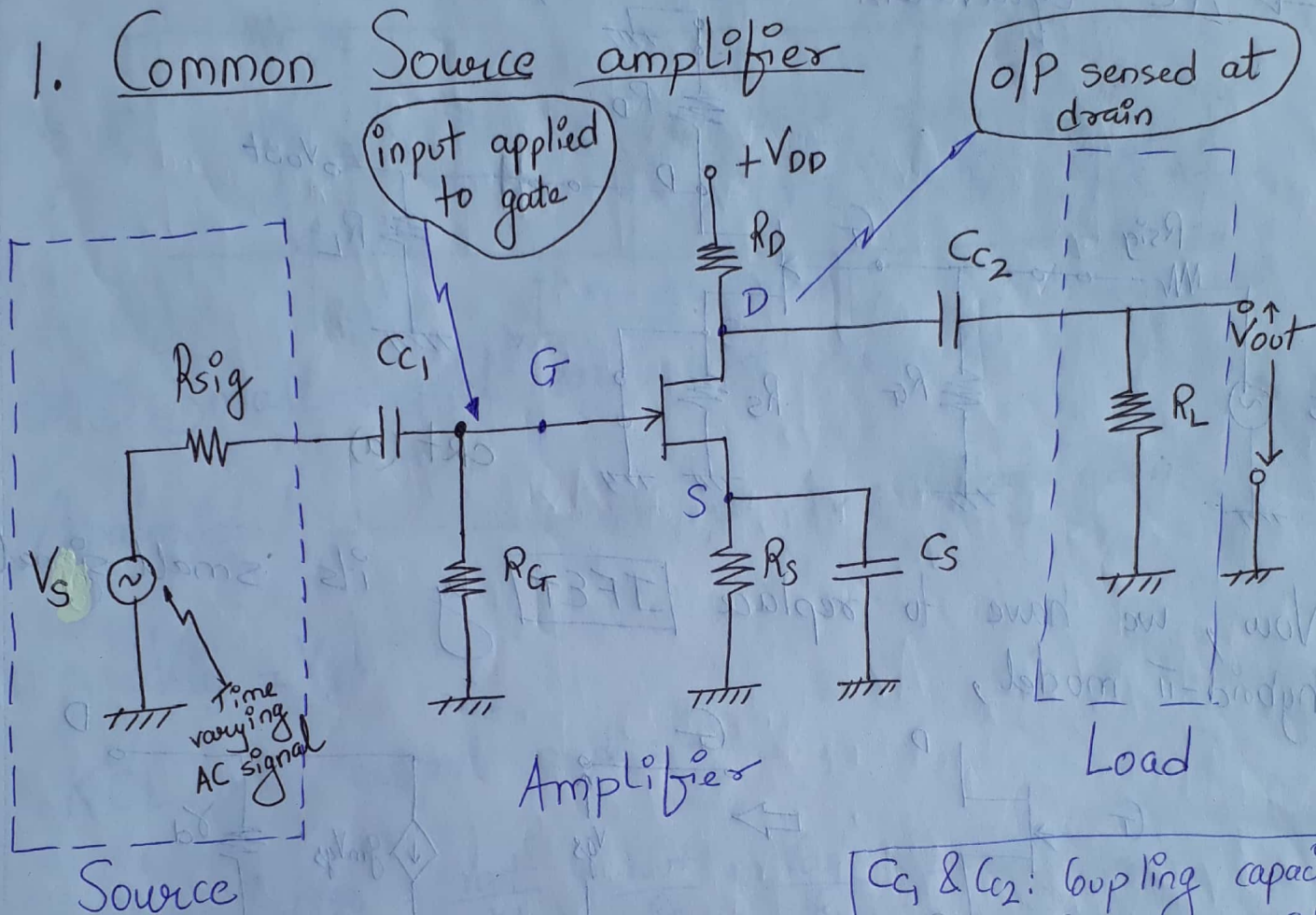


C_1 & C_2 : Coupling capacitors
 C_S : Bypass capacitors


Observations:-

1. In CS amplifier, i/p signal is applied to "gate" terminal and o/p is sensed at the "drain" terminal.
2. For AC analysis, all the capacitors are replaced by a short circuit \rightarrow as the capacitive impedances ($X_C = \frac{1}{2\pi f C}$) are very low at mid-frequencies.
3. DC supply is also replaced by a short circuit for small signal (AC) analysis.

→ AC equivalent circuit is,

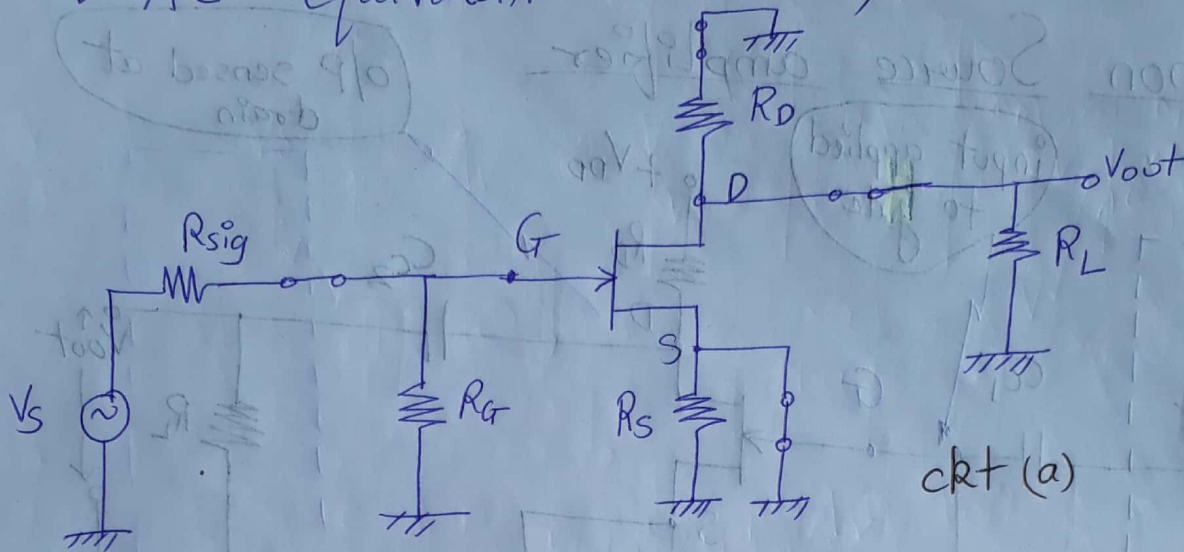

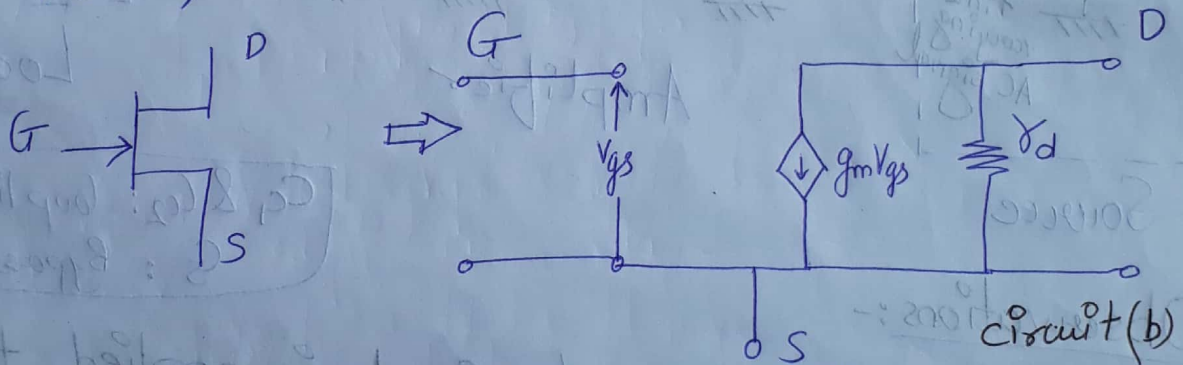
→ Now, we have to replace **JFET** by its small signal hybrid- π model,



→ Small-signal equivalent ckt is drawn next by combining ckt (a) & ckt (b)

Note: V_s → IP the varying signal

V_{out} → OP the varying signal

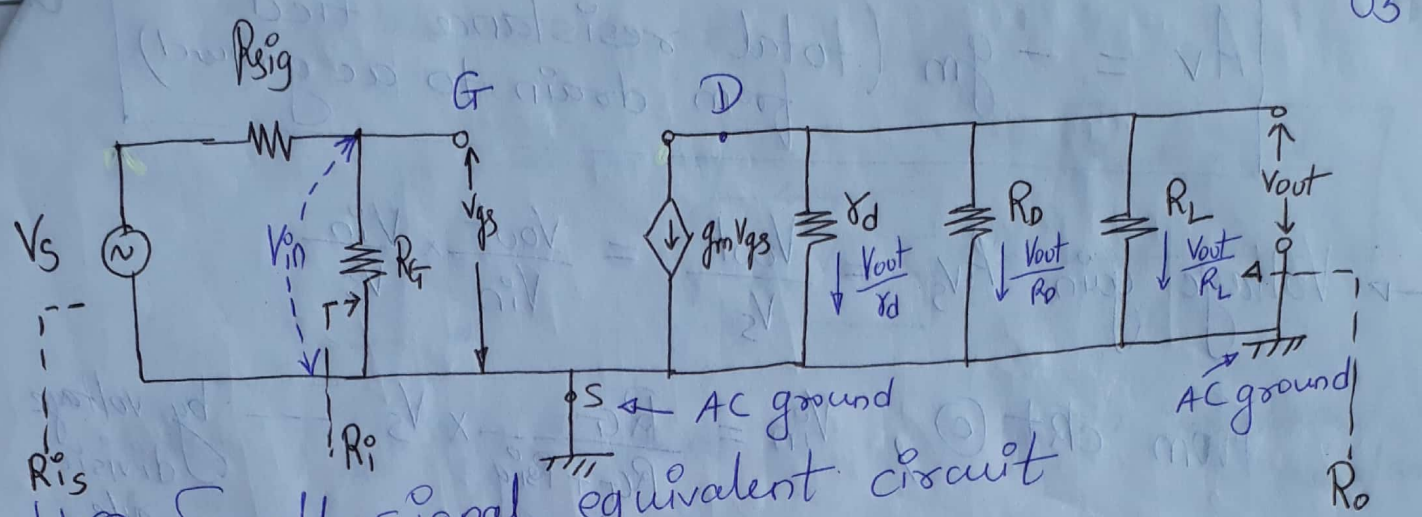

kt ©: Small-signal equivalent circuit

Analysis:- \longrightarrow Find A_v : Voltage gain

$V_{in} = V_{gs}$

KCL at output node :-

$$g_m V_{gs} + \frac{V_{out}}{r_d} + \frac{V_{out}}{R_D} + \frac{V_{out}}{R_L} = 0$$

ie $g_m V_{in} + V_{out} \left(\frac{1}{r_d} + \frac{1}{R_D} + \frac{1}{R_L} \right) = 0$

$$g_m V_{in} = -V_{out} / (r_d \parallel R_D \parallel R_L)$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -g_m (r_d \parallel R_D \parallel R_L)$$

$$A_v = -g_m (r_d \parallel R_D \parallel R_L) \quad \text{--- (1)}$$

-ve sign indicates i/p & o/p signals are opposite in phase

$$A_v = -g_m \left(\text{total resistance tied from drain to ac ground} \right)$$

→ Voltage gain $A_{V_s} = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s}$

From ckt (c), $V_{in} = \frac{R_G}{R_G + R_{sig}} \times V_s$ --- by voltage division rule


i.e. $\frac{V_{in}}{V_s} = \frac{R_G}{R_G + R_{sig}}$

$$A_{V_s} = A_v \times \left(\frac{R_G}{R_G + R_{sig}} \right)$$

Voltage gain including signal source resistance R_{sig}

Quick refresher!

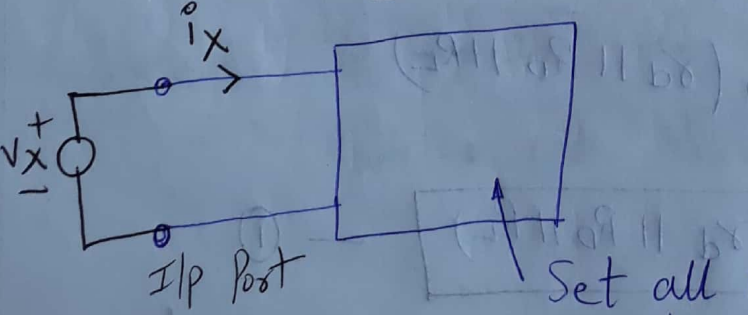
• Concept of port impedance :- I/P impedance/resistance of a ckt



$$R_{in}^o = \frac{V_x}{i_x}$$

Set all independent sources to zero

Looking at the o/p of ckt

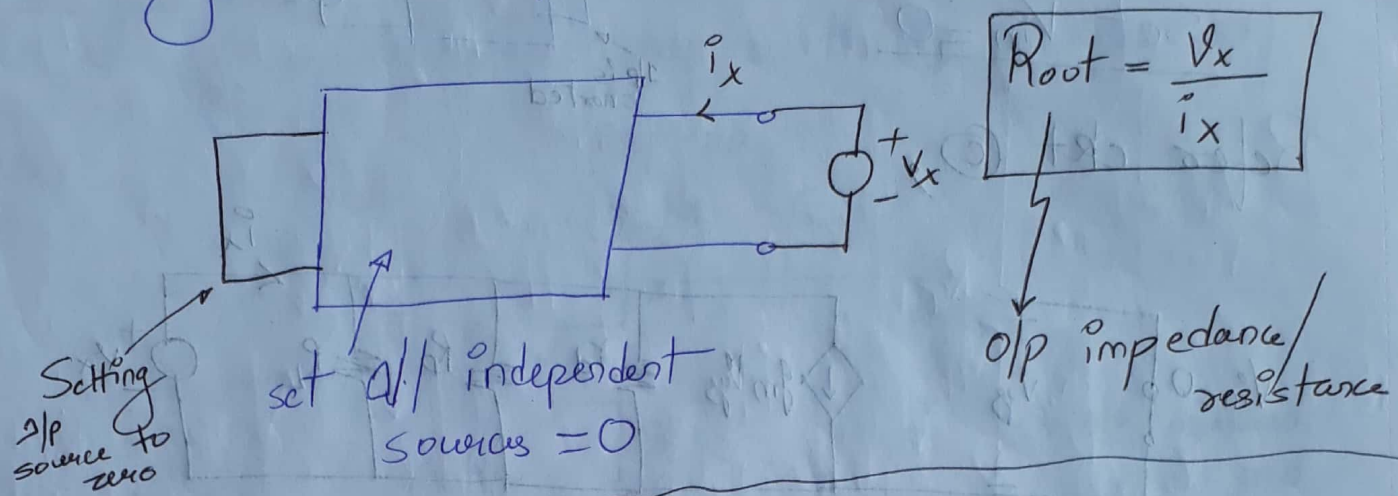


Input and o/p impedances :-

a) Input impedance :-

In ckt (c), gate & source terminal are open-circuited since gate current in JFET is v.v small ($I_g = 0$)
 → ckt reduces to,


i) without R_{sig}

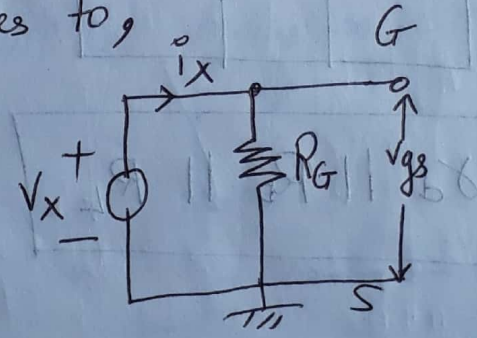

$$R_i = \frac{V_x}{i_x}$$

$$R_i = R_G$$

ii) with R_{sig}

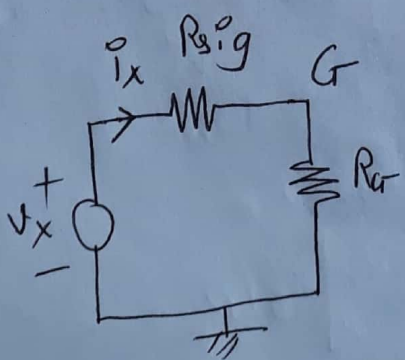


$$R_i = \frac{V_x}{i_x}$$


$$R_{is} = R_{sig} + R_G$$

Output impedance :-


Set $V_{in} = 0$

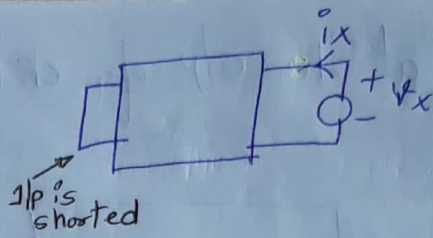

Refer ckt (c),

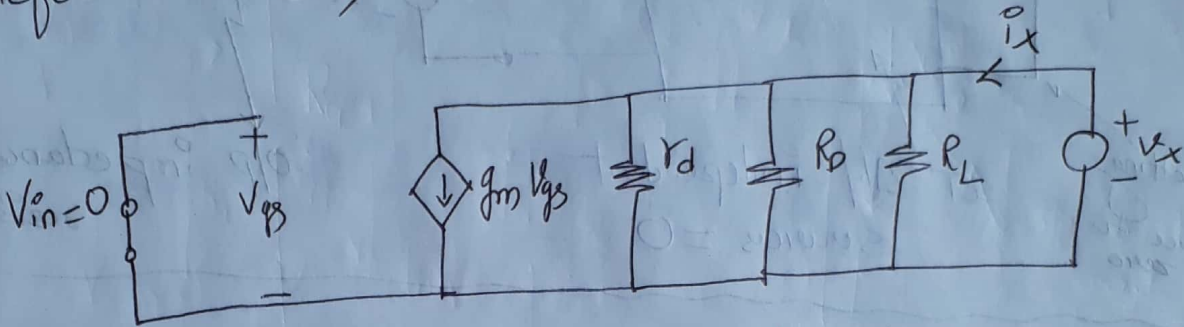

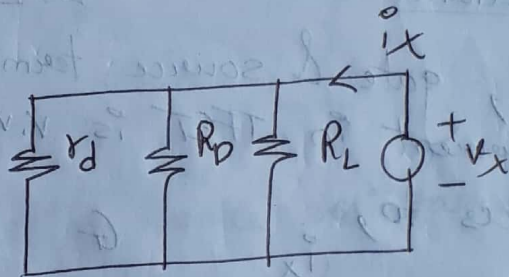→ Since $V_{in} = 0$; and $v_{gs} = V_{in} = 0$
 $g_m v_{gs} = 0 \rightarrow$ it becomes open ckt




$$\frac{v_x}{i_x} = r_d \parallel R_D \parallel R_L$$

$$R_o = r_d \parallel R_D \parallel R_L$$


o/p impedance

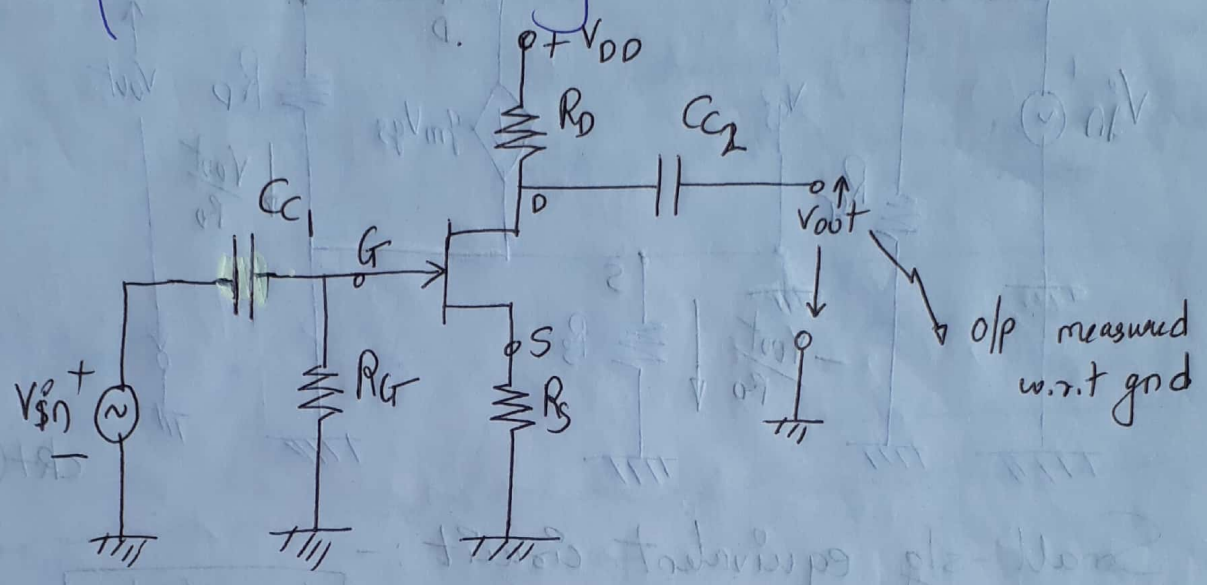2. Degenerated Common-Source amplifier :-
 (Common-source stage with R_S unbypassed)




AC analysis :-

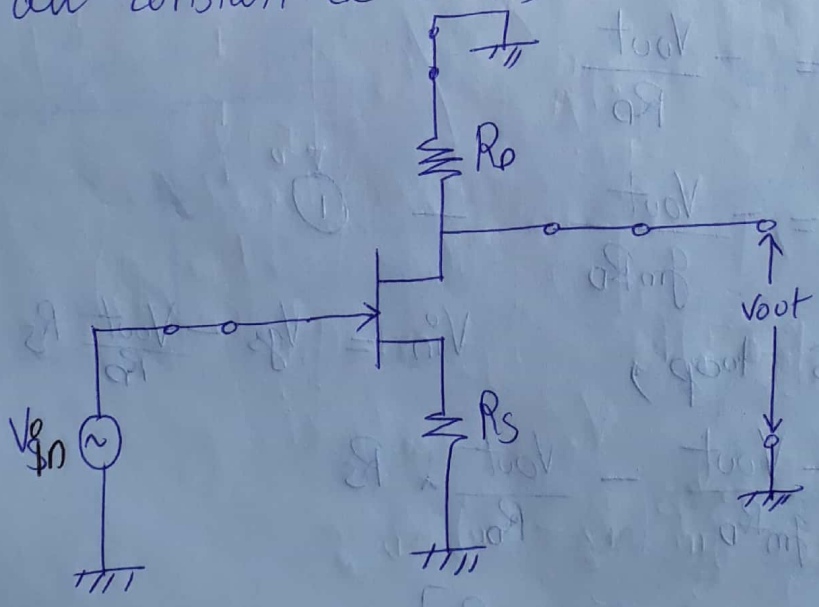- 1) Set all capacitors as short-ckt (assuming mid-freqⁿ)
- 2) Set all constant dc sources as short-ckt



Assuming $r_d = \infty$

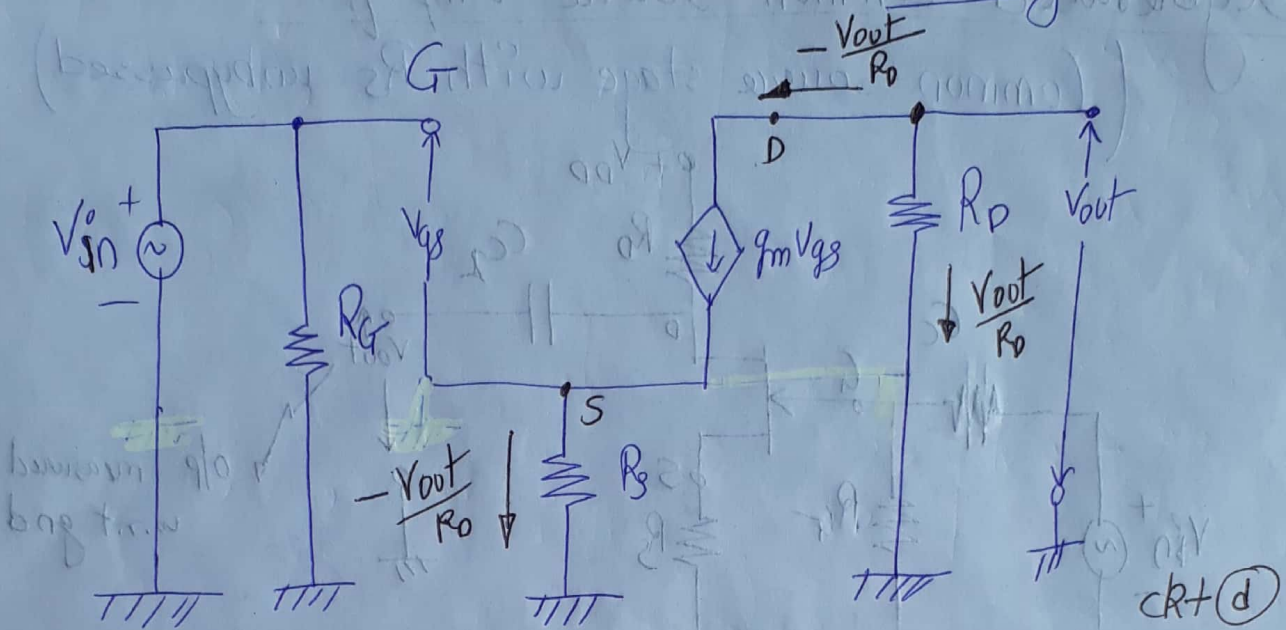

Small-sig equivalent circuit :-

i] Voltage gain (A_v):

$$A_v = \frac{V_{out}}{V_{in}}$$

Observations:-

$$g_m V_{gs} = -\frac{V_{out}}{R_D}$$

$$\text{i.e. } V_{gs} = -\frac{V_{out}}{g_m R_D} \quad \text{--- (1)}$$

KVL in G-S loop,

$$V_{in} = V_{gs} - \frac{V_{out}}{R_D} R_S$$

$$\rightarrow V_{in} = -\frac{V_{out}}{g_m R_D} - \frac{V_{out}}{R_D} R_S$$


$$V_{in} = \frac{V_{out}}{R_D} \left[\frac{1}{g_m} + R_S \right]$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{-R_D}{\frac{1}{g_m} + R_S}$$

$A_v = - \frac{\text{Resistance tied between drain and ac ground}}{\frac{1}{g_m} + \text{Resistance tied between source and ac ground}}$


Simplification, If $\frac{1}{g_m} \ll R_S \Rightarrow A_v \approx -\frac{R_D}{R_S}$

Input impedance:-

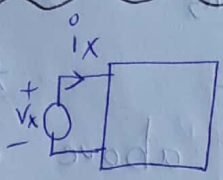

Refer ckt d,

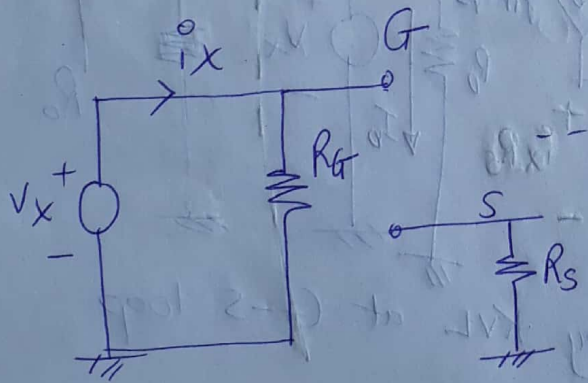→ Due to open-circuit betn G & S, we have



$$R_i = \frac{V_x}{i_x}$$


$$R_i = R_G$$

OR
 I/P impedance (Z_i)
 I/P resistance (R_i)


Output impedance :-

Refer ckt (d),

Set $V_{in} = 0$

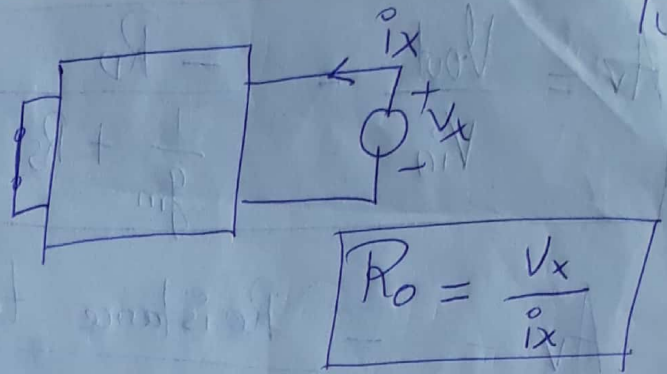

$$R_o = \frac{V_x}{i_x}$$

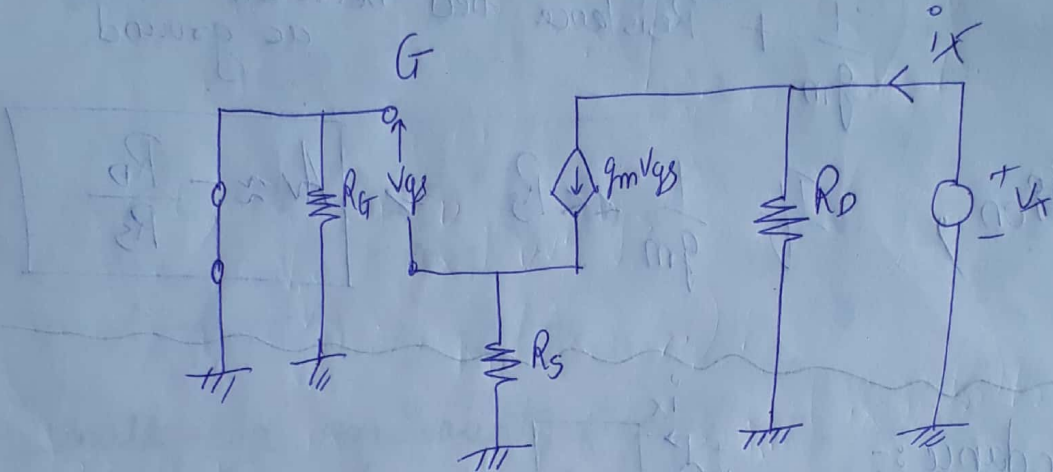

Redrawing the above ckt as

$$R_o' = \frac{V_x}{i_x}$$

KCL at 'D' node,

$$i_x + g_m V_{gs} = I_D$$

$$i_x - I_D = g_m V_{gs}$$

$$\rightarrow V_{gs} = - (i_x - I_D) R_S \quad \text{by KVL at G-S loop}$$

$$i_x - I_D = -g_m (i_x - I_D) R_S$$

$$i_x - I_D = -g_m i_x R_S + g_m I_D R_S$$

$$i_e \quad i_x (1 + g_m R_s) = +I_D (1 + g_m R_s)$$

$$i_e \quad \boxed{i_x = I_D}$$

This means $g_m V_{gs}$ source ≈ 0 for the applied conditions \rightarrow as no current flows through $g_m V_{gs}$ it is considered as open-circuited


$$i_e \quad V_x = i_x R_D$$

$$i_e \quad \frac{V_x}{i_x} = R_D$$


$$i_e \quad \boxed{R_o = R_D}$$

↓
o/p impedance of the ckt

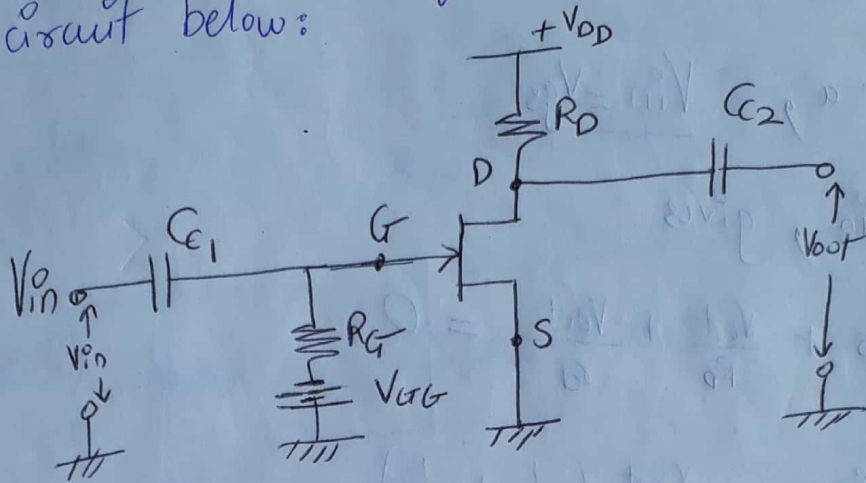
* Derive the expressions of A_v , R_i & R_o for the circuit below:



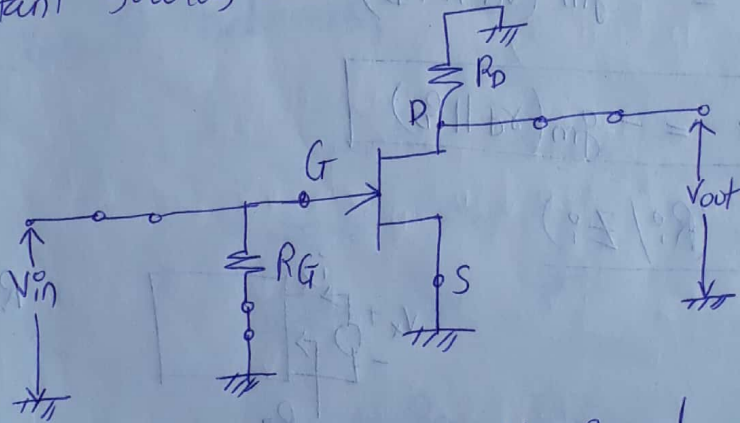Solⁿ: For small-signal AC analysis, all capacitances & constant sources are short-circuited



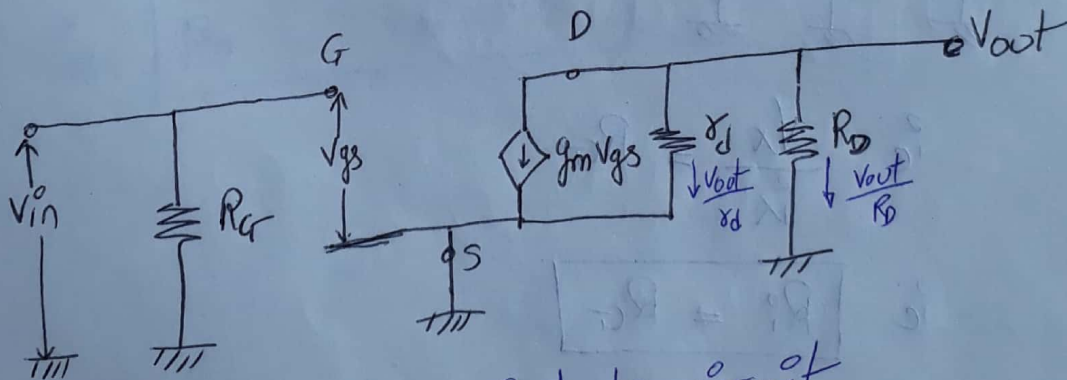Now, replacing JFET with small-signal equivalent model



ckt(a): Small-signal equivalent circuit

1. Voltage gain (A_v) :

From ckt a, $V_{in} = V_{gs}$

KCL at 'Drain', gives

$$g_m V_{gs} + \frac{V_{out}}{R_D} + \frac{V_{out}}{r_d} = 0$$



$$g_m V_{in} = -V_{out} \left(\frac{1}{R_D} + \frac{1}{r_d} \right)$$

$$\frac{V_{out}}{V_{in}} = -g_m (r_d \parallel R_D)$$

$$\text{ie } \boxed{A_v = -g_m (r_d \parallel R_D)}$$

2. I/P impedance (R_i / Z_i)

From ckt a,

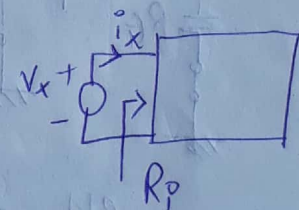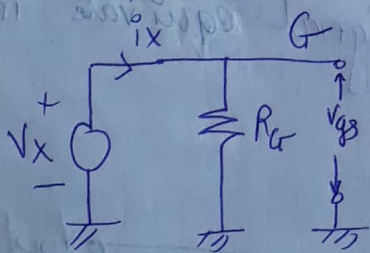

$$R_i = \frac{V_x}{i_x}$$


Since gate current is zero, entire current i_x flows through R_G

$$\text{ie } \frac{V_x}{i_x} = R_G$$


$$\text{ie } \boxed{R_i = R_G}$$

3. O/P impedance R_o / Z_o :

Refer ckt a,

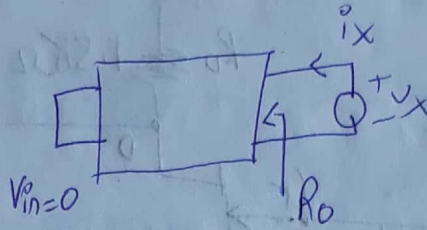


$$R_o = \frac{V_x}{i_x}$$

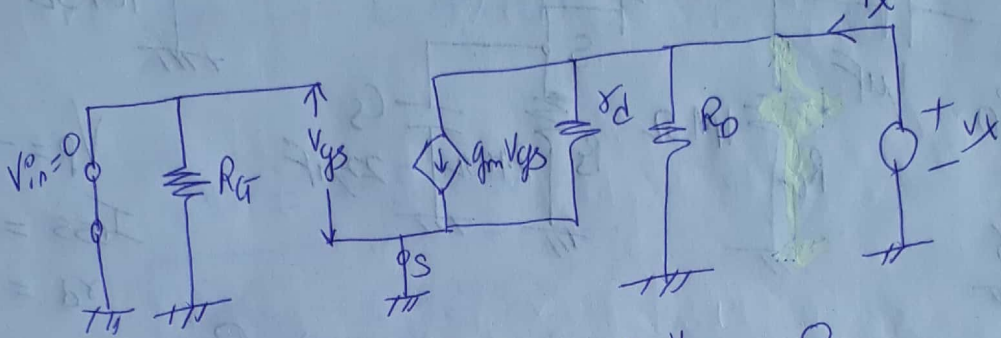

Since $v_{in} = 0$; $v_{gs} = 0$; $g_m v_{gs} = 0$


Circuit becomes,

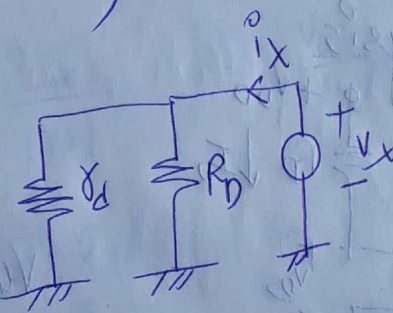

$$i_x \frac{V_x}{i_x} = R_D \parallel R_L$$


$$R_o = R_D \parallel R_L$$

Numerical 01:

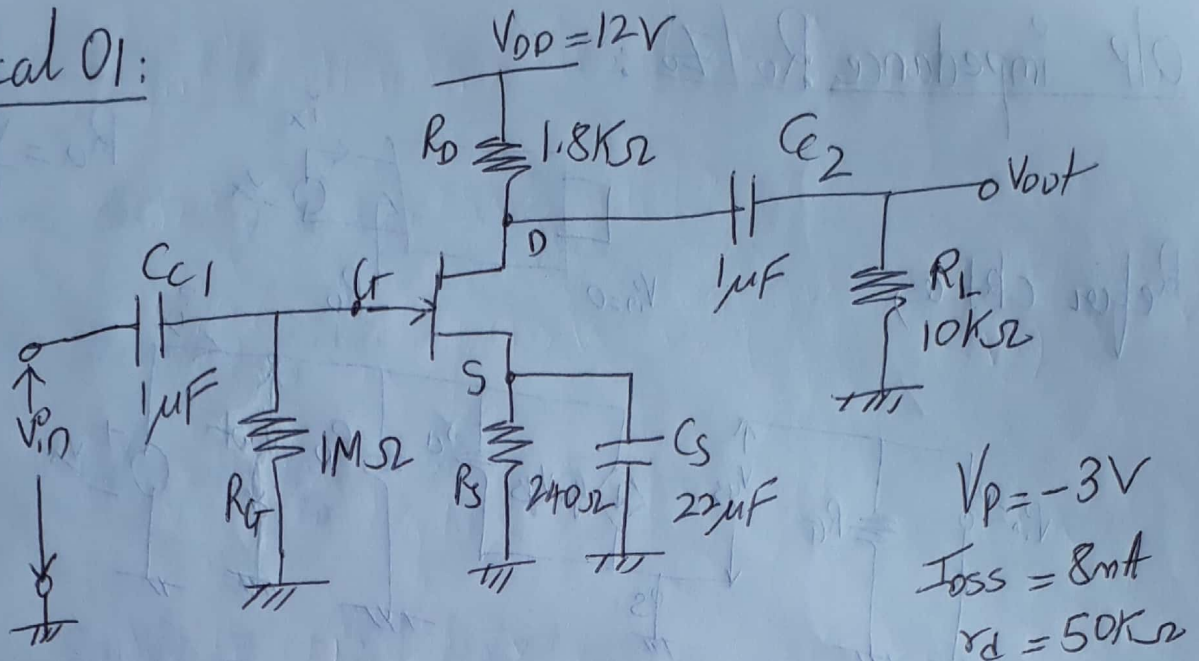

Find 1) g_m 2) A_v 3) R_i & 4) R_o

Solⁿ: 1) DC Analysis

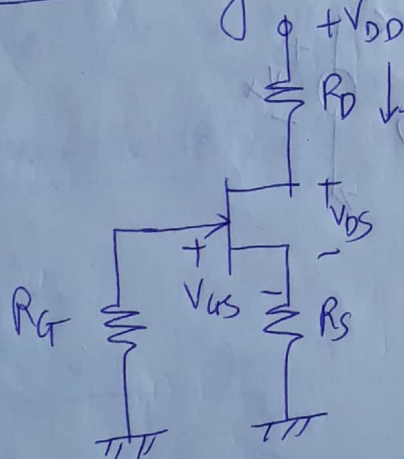

$$V_G = 0$$

$$V_S = I_D R_S$$

$$V_{GS} = -I_D R_S$$

$$V_{GS} = -I_D (240) \quad \text{--- (1)}$$

Assuming that JFET is working in saturation region,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 8\text{mA} \left(1 + \frac{V_{GS}}{3} \right)^2 \quad \text{--- (2)}$$

Put (2) in (1), we get

$$V_{GS} = -1.92 \left(1 + \frac{2}{3} V_{GS} + \frac{V_{GS}^2}{9} \right)$$

$$V_{GS} = -1.92 - 1.28 V_{GS} - 0.2133 V_{GS}^2$$

ie $0.2133 V_{GS}^2 + 2.28 V_{GS} + 1.92 = 0$

$$V_{GS} = -0.9215 V \quad \checkmark \quad \left(\begin{array}{l} \text{We select this as} \\ V_{GS} > V_P \end{array} \right)$$

OR

$$V_{GS} = -9.76 V$$

$$\therefore \boxed{V_{GS} = -0.9215 V}$$

2) Find small-signal parameters


g_m :

$$g_m = \frac{2 I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$= \frac{2 \times 8 \text{ mA}}{3} \left(1 - \frac{(-0.9215)}{(-3)} \right)$$

$$\boxed{g_m = 3.693 \frac{\text{mA}}{\text{V}}}$$

3) Small-signal AC analysis:

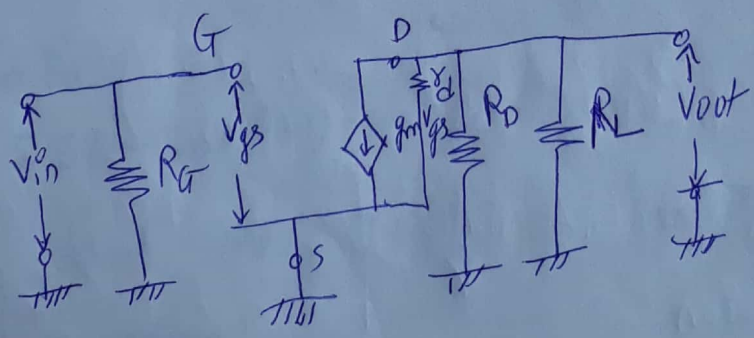

$$\rightarrow A_v = -g_m (r_d \parallel R_D \parallel R_L)$$

$$= -g_m (1.48 \text{K}\Omega)$$


$$\boxed{A_v = -5.46}$$

$$\rightarrow \boxed{R_i = R_G = 1 \text{M}\Omega}$$

$$\rightarrow R_D = r_d \parallel R_D \parallel R_L$$


$$\boxed{R_D = 1.48 \text{K}\Omega}$$

Numerical Q2 :

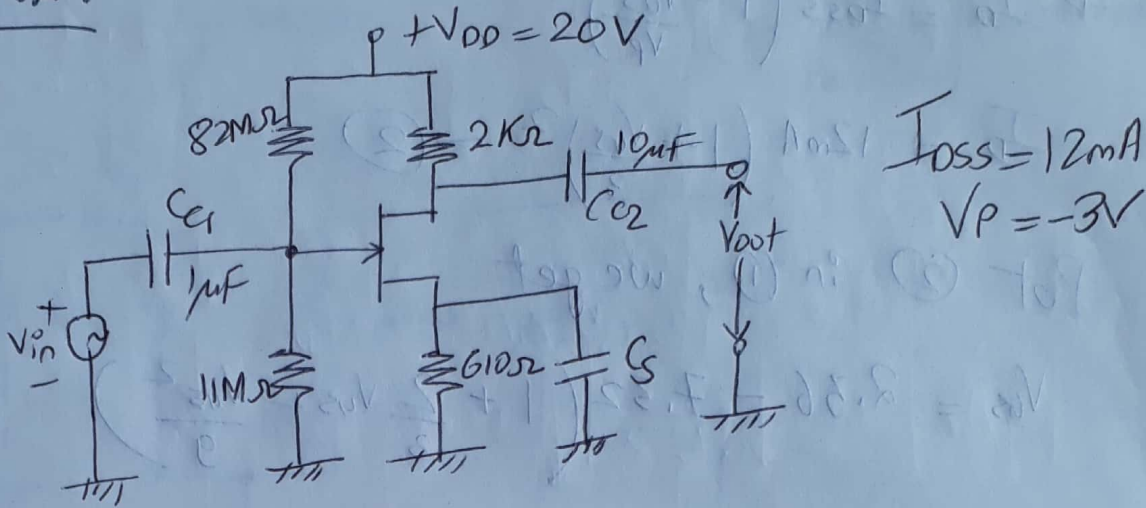

- Find
- 1) g_m
 - 2) A_v , R_i & R_o with R_S bypassed
 - 3) A_v with R_S unbypassed

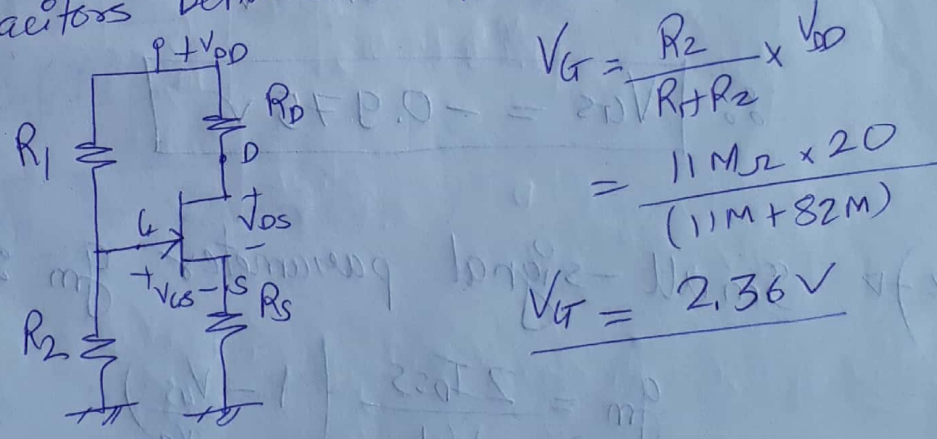Solⁿ:- 1) DC Analysis
 All capacitors behaves as open-ckt



$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$= \frac{11M\Omega \times 20}{(11M + 82M)}$$

$$V_G = 2.36V$$

- $V_S = I_D R_S$
- $V_{GS} = 2.36 - I_D (610) \quad \text{--- (1)}$

Assuming that the JFET is working in saturation region

$$\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 12 \text{ mA} \left(1 + \frac{V_{GS}}{3}\right)^2 \quad \text{--- (2)}$$

Put (2) in (1), we get

$$V_{GS} = 2.36 - 7.32 \left(1 + \frac{2}{3} V_{GS} + \frac{V_{GS}^2}{9}\right)$$

$$V_{GS} = 2.36 - 7.32 - 4.88 V_{GS} - 0.8133 V_{GS}^2$$

$$\text{i.e. } 0.8133 V_{GS}^2 + 5.88 V_{GS} + 4.96 = 0$$

$$V_{GS} = -0.975 \text{ V} \quad \checkmark \quad \left(\text{Since } V_{GS} > V_P, \text{ we use this value}\right)$$

OR

$$V_{GS} = -6.25 \text{ V}$$

$$\boxed{V_{GS} = -0.975 \text{ V}}$$

2) Small-signal parameter g_m :


$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$= \frac{2 \times 12 \text{ mA}}{3} \left(1 - \frac{-0.975}{-3}\right)$$

$$\boxed{g_m = 5.4 \frac{\text{mA}}{\text{V}}}$$

Case ①: R_S is bypassed

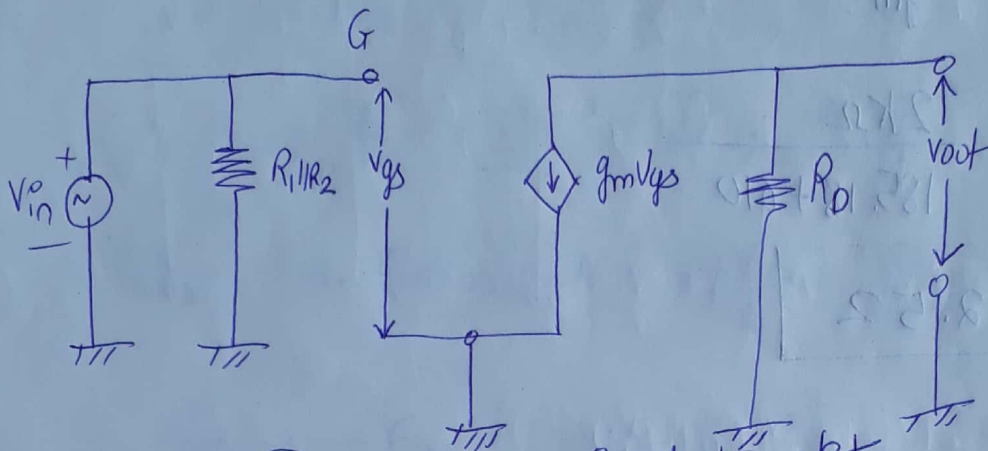09
(r_d not given, so assume $r_d = \infty$)



Small-sig equivalent ckt

$$\rightarrow A_v = -g_m R_D = -5.4 \frac{\text{mA}}{\text{V}} \times 2\text{K}\Omega$$


$$A_v = -10.8$$

$$\rightarrow R_i = R_1 \parallel R_2 = 82\text{M}\Omega \parallel (11\text{M}\Omega)$$

$$R_i = 9.69\text{M}\Omega$$

$$\rightarrow R_o = R_D = 2\text{K}\Omega$$

Case ②: R_S is unbypassed

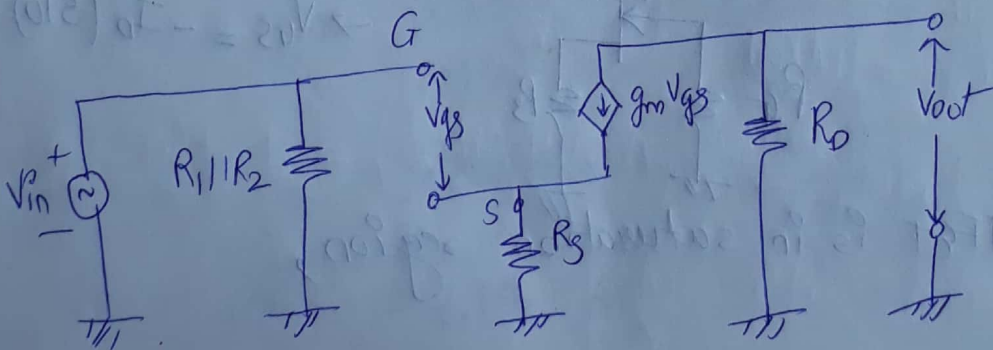


$$A_v = \frac{R_D}{1 + R_S + g_m R_S}$$

$$= - \frac{2 \text{ K}\Omega}{185.18 + 610}$$


$$A_v = -2.52$$

Numerical 03 :

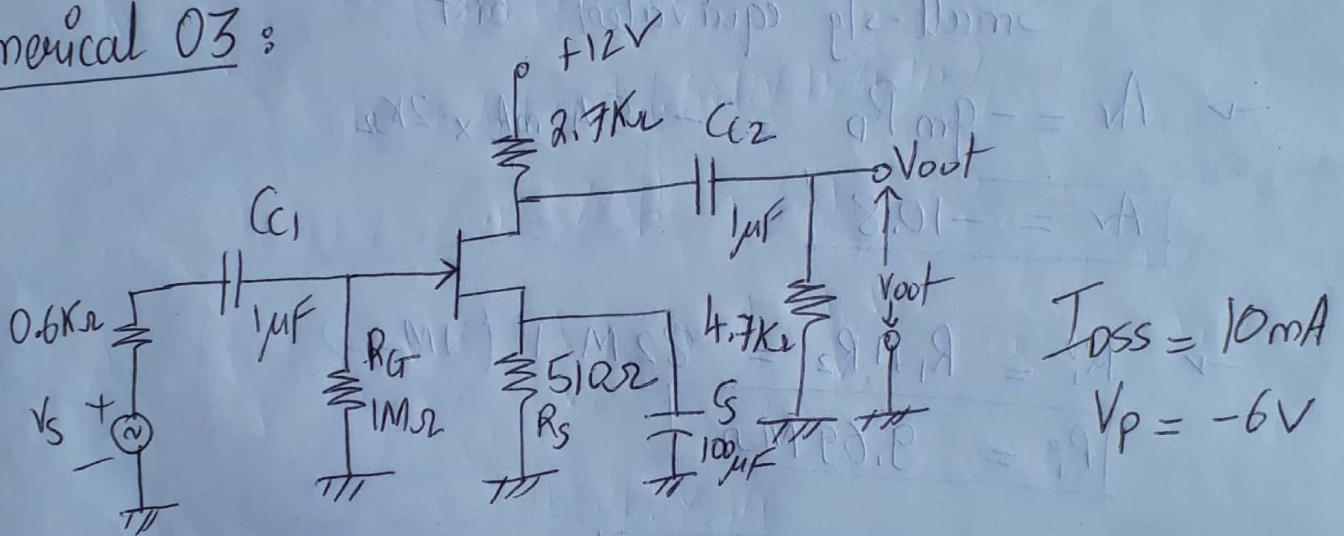

Find A_v , R_i & R_o

Solⁿ :- 1) DC Analysis

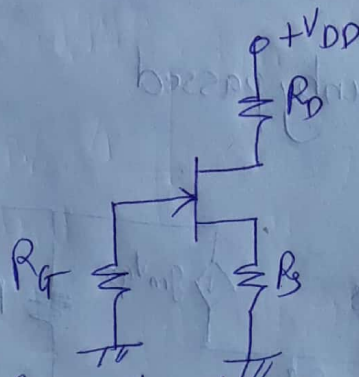

$$V_G = 0$$

$$V_S = I_D R_S$$

$$\rightarrow V_{GS} = -I_D (510) \text{ --- (1)}$$

Assuming JFET is in saturation region,

$$\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 10\text{mA} \left(1 + \frac{V_{GS}}{6}\right)^2 \quad \text{--- (2)}$$

$I_D \Rightarrow$ Put (2) in (1), we get

$$V_{GS} = -510 \times 10\text{mA} \left(1 + \frac{2V_{GS}}{6} + \frac{V_{GS}^2}{36}\right)$$

$$V_{GS} = -5.1 \left(1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36}\right)$$

$$V_{GS} = -5.1 - 1.7V_{GS} - 0.1417V_{GS}^2$$

$$\rightarrow 0.1417V_{GS}^2 + 2.7V_{GS} + 5.1 = 0$$

ie $V_{GS} = -2.12 \text{ V}$ (We select this value since $V_{GS} > V_P$)

OR

$$V_{GS} = -16.92 \text{ V}$$


$$\boxed{V_{GS} = -2.12 \text{ V}}$$

2) Small-signal parameter g_m :

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$= \frac{2 \times 10\text{mA}}{6} \left(1 - \frac{-2.12}{-6}\right)$$
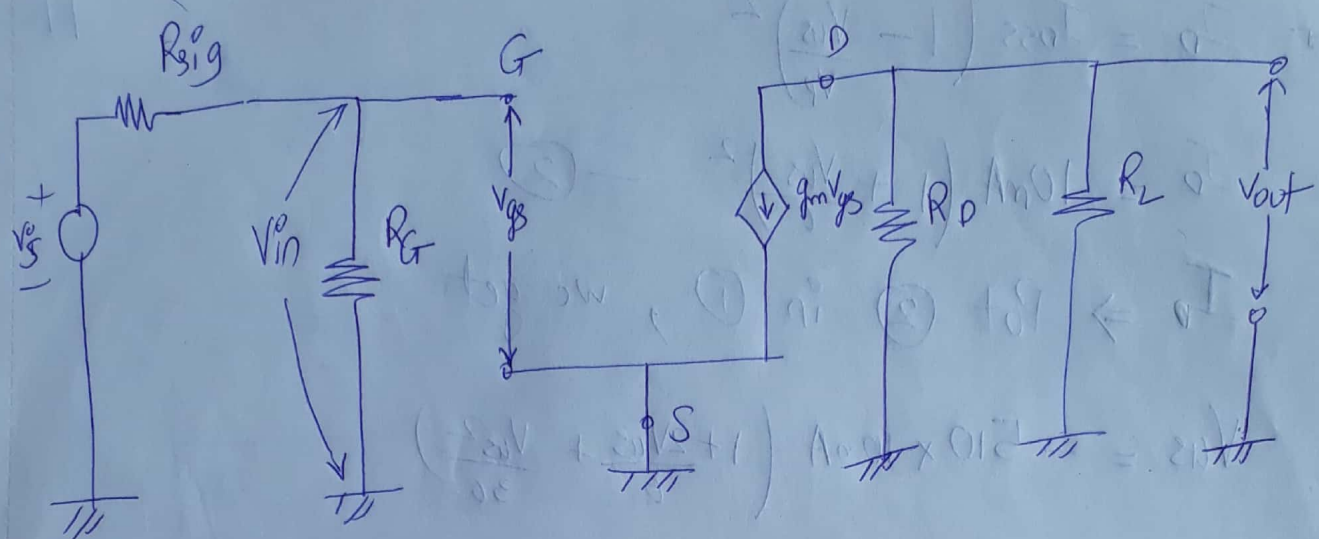
$$\boxed{g_m = 2.15 \frac{\text{mA}}{\text{V}}}$$



$$\rightarrow A_v = \frac{V_{out}}{V_{in}} = -(g_m (R_D || R_L) + 1) \cdot 1.0 = -2.15 \text{ mA} (2.7 \text{ K} || 4.7 \text{ K})$$

$$\boxed{A_v = -3.687}$$

$$\rightarrow A_{v_s} = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s} = A_v \frac{V_{in}}{V_s}$$

$$\frac{V_{in}}{V_s} = \frac{R_G}{R_G + R_{sig}} = 0.9994$$

$$\text{ie } A_{v_s} = A_v \times 0.9994 = -3.687 \times 0.9994$$

$$\boxed{A_{v_s} = -3.684}$$

$$\rightarrow R_i = R_G = 1 \text{ M}\Omega$$

$$\rightarrow R_o = R_D || R_L = 2.7 \text{ K} || 4.7 \text{ K} = 1.714 \text{ K}\Omega$$