

Design Rules for NMOS and CMOS



- Design Rules
- Stick Diagrams
- Layout Diagram
- Examples

Design Rules: Introduction

- ❑ Design rules are a set of geometrical specifications that **dictate the design** of the layout
- ❑ Layout is top view of a chip
- ❑ Design process are aided by stick diagram and layout
- ❑ Stick diagram gives the placement of different components and their connection details
- ❑ But the dimensions of devices are not mentioned
- ❑ Circuit design with all dimensions is Layout

Design Rules: Introduction

- ❑ Fabrication process needs different masks, these masks are prepared from layout
- ❑ Layout is an Interface between circuit designer and fabrication engineer
- ❑ Layout is made using a set of design rules.
- ❑ Design rules allow translation of circuit (usually in stick diagram or symbolic form) into actual geometry in silicon wafer
- ❑ These rules usually specify the minimum allowable line widths for physical objects on-chip
- ❑ Example: metal, polysilicon, interconnects, diffusion areas, minimum feature dimensions, and minimum allowable separations between two such features.


NEED FOR DESIGN RULES

- Better area efficiency
- Better yield
- Better reliability
- Increase the probability of fabricating a successful product on Si wafer

If design rules are not followed:

- Functional or non-functional circuit.
- Design consuming larger Si area.
- The device can fail during or after simulation.

Colour Codes :

 Layer	Color	Representation
N+ Active	Green	
P+ Active	Yellow	
PolySi	Red	
Metal 1	Blue	
Metal 2	Magenta	
Contact	Black	X
Buried contact	Brown	X
Via	Black	X
Implant	Dotted yellow	
N-Well	Dotted <small>Darshana Sankhe</small> Green/Black	


Stick Diagrams :

- ❑ A stick diagram is a symbolic representation of a layout.
- ❑ In stick diagram, each conductive layer is represented by a line of distinct color.
- ❑ Width of line is not important, as stick diagrams just give only wiring and routing information.
- ❑ Does show all components/vias, relative placement.
- ❑ Does not show exact placement, transistor sizes, wire lengths, wire widths, tub boundaries.

Stick Diagrams: Basic Rules

- Poly crosses diffusion forms transistor
- Red (poly) over Green(Active), gives a FET.


L:W

 

nFET/
nMOS

- Aspect Ratio

L:W

 

pFET/pMOS


Stick Diagrams: Basic Rules

- Blue may cross over red or green, without connection.
- Connection between layers is specified with **X**.
- Metal lines on different layer can cross one another, connections are done using via.

Stick Diagrams(NMOS): Basic Steps


- Normally, the first step is to draw two parallel metal (**blue**) V_{DD} and GND rails.
- There should be enough space between them for other circuit elements.
- Next, Active (**Green**) paths must be drawn for required transistors.
- Do not forget to mark contacts as **X**, wherever required.
- Remember, Poly (**Red**) crosses Active (**Green/yellow**), where transistor is required.
- For depletion mode FET, draw required implants (**yellow**).
- Label each transistor with L:W ratio.

Enhancement-Mode MOSFET :

 

Enhancement-Mode MOSFET :

 - When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



Inverter Using MOSFET

- ❑ Enhancement-Mode MOSFETs act as switches.
- ❑ They are switched OFF, when the input to gate is low.
- ❑ So, they can be used to pull the output down.
- ❑ Now, for pull-up, we can use a resistor.
- ❑ But resistors consume larger area.
- ❑ Another alternative is using MOSFET as pull-up.


Inverter Using MOSFET

- The pull-up MOSFET can be Enhancement-mode or Depletion mode.
- Enhancement-mode as pull-up:
 - To use Enhancement-mode FET as active load, the gate should be connected to a separate gate bias voltage.
 - $V_{o(max)} = V_{DD} - V_{th}$


Inverter Using MOSFET

- Depletion mode as pull-up:
 - Depletion-Mode FET has a channel with zero gate-bias.
 - They will not turn-off until sufficient reverse bias is applied to its gate.
 - To be used as a load, the gate should be connected to source.
 - $V_{o(max)} = V_{DD}$


Inverter Using MOSFET

 


NMOS Inverter: Enhancement load

 

 
NMOS Inverter: Enhancement load (Stick diagram)




NMOS Inverter: Depletion load

 

 
NMOS Inverter: Depletion load (Stick Diagram)




NMOS 2 I/P NAND Gate :

 


NMOS NAND (Stick Diagram) :

 



NMOS 2 I/P NOR Gate :

 

NMOS NOR (Stick Diagram)

 

MOSFET

  

A silicon wafer

Aspect Ratio For Pull-up and Pull-down

- The size of a MOSFET depends on the reference inverter design.
- The reference inverter for nMOS logic design is the inverter with depletion mode load.
- $Z_{PD} = \text{Aspect Ratio of pull-down} = L_{PD}/W_{PD}$
- $Z_{PU} = \text{Aspect Ratio of pull-up} = L_{PU}/W_{PU}$
- The ratio of aspect ratio of Pull-up and Pull-down is known as Inverter Ratio i.e. $R_{INV} = Z_{PU} / Z_{PD}$
- When we draw a stick diagram, inverter ratio should be mentioned for that gate.
- When a we draw a stick diagram, aspect ratio should be mentioned for all the MOSFETS.

Aspect Ratio For Pull-up and Pull-down

- For example, if we say, the reference design has $R_{inv} = 4:1$, then, ratio of effective Z_{PU} and effective Z_{PD} , should be equal to 4:1.
- $R_{channel} = (L/W)R_{sc}$
- Therefore:
 - if MOSFETs are connected in series, the effective $L/W = (L/W)_1 + (L/W)_2 + \dots$
 - if MOSFETs are connected in parallel, the effective $L/W = (L/W)_1 = (L/W)_2$

Aspect Ratio For Pull-up and Pull-down

For NMOS:

- There are two values of R_{inv} , that are sufficient for all NMOS basic gates:
 - $R_{inv} = 4:1$
 - To save space.
 - $R_{inv} = 8:1$
 - When input is taken from a pass transistor.

Inverter Ratio for NMOS Gates :

Gates	R_{inv}	Z_{PU}	Z_{PD}
Inverter	4	2:1	1:2
		4:1	1:1
	8	8:1	1:1
		4:1	1:2
		2:1	1:4
NAND (2 I/P)	4	4:1	1:2 (Each)
		2:1	1:4 (Each)
NOR (2 I/P)	4	2:1	1:2 (Each)
		4:1	1:1 (Each)

NMOS NAND and NOR :

NMOS NAND

- ❑ Two nmos in series.
- ❑ Gate delay and area increases with increase in no of inputs.
- ❑ Length also increases with increase in no of input.
- ❑ NMOS NAND is slower for same no of inputs and power dissipation.

NMOS NOR

- ❑ Two nmos in parallel.
- ❑ NOR works quite well for any no of inputs.
- ❑ Width is proportional to number of inputs.
- ❑ NMOS NOR is faster for same no of inputs and power dissipation.

Types of Layout Design Rules

- Industry Standard: Micron Rule
- λ Based Design Rules

Types of Design Rules (Contd...)

- Industry Standard: Micron Rule
 - All device dimensions are expressed in terms of absolute dimension($\mu\text{m}/\text{nm}$)
 - These rules will not support proportional scaling

Types of Design Rules (Contd...)

□ λ Based Design Rules :

- Developed by Mead and Conway.
- All device dimensions are expressed in terms of a scalable parameter λ .
- $\lambda = L/2$; $L =$ The minimum feature size of transistor
- $L = 2 \lambda$
- These rules support proportional scaling.
- They should be applied carefully in sub-micron CMOS process.

Types of Design Rules (Contd...)

□ λ Based Design Rules

- In MOS, the minimum feature size of Tr is:

$$(L/W)_n = 1/1 = 2 \lambda/2 \lambda$$

$$\text{Active area} = L * W = 4 \lambda^2$$

- In CMOS, the minimum feature size of Tr is:

$$(L/W)_n = 1/1.5 = 2 \lambda/3 \lambda$$

$$\text{Active area} = L * W = 6 \lambda^2$$

Design Rules


- Minimum **length or width** of a feature on a layer is **2λ**
 - To allow for shape contraction
- Minimum **separation** of features on a layer is **2λ**
 - To ensure adequate continuity of the intervening materials.

Design Rules :

- Two Features on different mask layers can be misaligned by a maximum of 2λ on the wafer.
- If the overlap of these two different mask layers can be catastrophic to the design, they must be separated by at least 2λ
- If the overlap is just undesirable, they must be separated by at least λ


Design Rules: NMOS

 - Minimum width of PolySi and diffusion line 2λ
- Minimum width of Metal line 3λ as metal lines run over a more uneven surface than other conducting layers to ensure their continuity




Design Rules: NMOS

 - PolySi – PolySi spacing 2λ
- Metal - Metal spacing 3λ
- Diffusion – Diffusion spacing 3λ To avoid the possibility of their associated regions overlapping and conducting current




Design Rules: NMOS

 - **Diffusion – PolySi spacing λ To prevent the lines overlapping to form unwanted capacitor.**
- **Metal lines can pass over both diffusion and polySi without electrical effect. Where no separation is specified, metal lines can overlap or cross.**




Design Rules: NMOS

 - **Metal lines can pass over both diffusion and polySi without electrical effect**
- **It is recommended practice to leave λ between a metal edge and a polySi or diffusion line to which it is not electrically connected**




Contact Cut :

 - Metal connects to polySi/diffusion by contact cut.
- Contact area: $2\lambda * 2\lambda$
- Metal and polySi or diffusion must overlap this contact area by λ so that the two desired conductors encompass the contact area despite any misalignment between conducting layers and the contact hole



Contact Cut

 - **Contact cut – contact cut: 2λ apart**
- **Why? To prevent holes from merging.**










Design Rules: NMOS



- Minimum diff width 2λ
- Minimum poly width 2λ
- Minimum metal width 3λ
- poly-poly spacing 2λ
- diff-diff spacing 3λ
(depletion regions tend to spread outward)
- metal-metal spacing 3λ
- diff-poly spacing λ

Design Rules: NMOS

       - Poly gate extend beyond diff by 2λ
- Diff extend beyond poly by 2λ
- Contact size $2\lambda * 2\lambda$
- Contact diff/poly/metal overlap 1λ
- Contact to contact spacing 2λ
- Contact to poly/diff spacing 2λ
- Buried contact to active device spacing 2λ
- Buried contact overlap in diff direction 2λ
- Buried contact overlap in poly direction 1λ
- Implant gate overlap 2λ



1:1

  


Interlayer Contacts :

- ❑ Interconnection between poly and diffusion is done by contacts.
- ❑ Metal contact
- ❑ Butting contact
- ❑ Buried contact

Metal contact :

 - Contact cut of $2\lambda * 2\lambda$ in oxide layer above poly and diffusion
- Metal used for interconnection
- Individual contact size becomes $4\lambda * 4\lambda$




Butting Contact

- The gate and diffusion of NMOS device can be connected by a **butting contact**.
- **Two contact cuts are adjacent to each other**
- **Therefore effective contact area is less**
- Here metal makes contact to both the diffusion forming the drain of the transistor and to the polySi forming this device's gate.



Butting Contact

Disadvantages:

 - Metal descending the hole has a tendency to fracture at the polySi corner, causing an open circuit.
- Requires a metal cap.



Butting Contact :

  


Butting Contact

- Metallization is required only over the butting contact holes which are $2\lambda \times 4\lambda$ in size
- A border of width λ around all four sides is added to allow for mis-registration and to ensure proper contact.
- This brings the metallization size to $4\lambda \times 6\lambda$


Advantage:

- No buried contact mask required and avoids associated processing.


NMOS INVERTER- Enhancement load

 

NMOS INVERTER: Enhancement Load

 


NMOS INVERTER- Enhancement load

 


Buried Contact

 - The buried contact window defines the area where oxide is to be removed so that polySi connects directly to diffusion.
- Contact Area must be a min. of $2\lambda * 2\lambda$ to ensure adequate contact area.




- **Advantages: No metal cap required.**
- **Disadvantage: An extra mask is required.**

Buried contact :

 




Buried Contact

 

Buried Contact

 
- The **buried contact window** surrounds this contact by λ in all directions to avoid any part of this area forming a transistor.
- Separated from its **related transistor gate** by 2λ to prevent gate area from being reduced.



  


NMOS INVERTER

Depletion load

 


NMOS INVERTER


Depletion Load

 

NMOS NAND

 


NMOS NOR

 

Darshana Sankhe

NMOS NOR: Layout

 


Darshana Sankhe

(c)

CMOS :

 - ❑ Pull-up is PMOS
- ❑ Pull-down is NMOS
- ❑ The channel mobility of electrons is approximately twice of that of holes.
- ❑ Conductivity of NMOS is twice, that of identical PMOS.
- ❑ But in case of CMOS inverters, one of the devices is always switched off and has very high impedance.
- ❑ The noise margin of CMOS circuits is larger than those of NMOS gate operating between same supply rails.



Aspect Ratio :

For CMOS:

□ $R_{inv} = 1:1$ (Ratioless)

- As one of the device is always off.
- 1:1 inverter ratio gives more symmetric layout

Stick Diagram (CMOS): Basic Steps


- ❑ Steps for CMOS are similar to NMOS
- ❑ But one difference is that depletion mode FETs are not used.
- ❑ Here, yellow/ brown is used to identify PMOS.
- ❑ The two types of FET, n and p, are separated in the diagram by the demarcation line.
- ❑ This line represents the well (n/p-well).
- ❑ Above this line are all p-type MOSFETs.
- ❑ Below this line n-type MOSFET are present.

Stick Diagram (CMOS): Basic Steps


- ❑ No Diffusion can cross demarcation line.
- ❑ Only poly and metal can cross demarcation line
- ❑ N-diffusion and p-diffusion are joined using a metal wire.
- ❑ First step is to draw two parallel rails for VDD and GND.
- ❑ Next draw a demarcation line (brown)
- ❑ Place all PMOS above and NMOS below this line.
- ❑ Connect them using wires (metal).

PMOS :

 - Body tied to high voltage (V_{DD})
- Gate low: transistor ON
- Gate high: transistor OFF
- Bubble indicates inverted behavior





CMOS Inverter (Circuit Diagram)

 


Darshana Sankhe



CMOS Inverter :

  

CMOS Inverter (Stick Diagram)

 


CMOS Inverter (Stick Diagram)

  


Well Biasing :

- ❑ The various N and P diffusions must be reverse biased to ensure that those wells are insulated from each other.
- ❑ This requires that the N- wells are connected to the most positive voltage, VDD.
- ❑ The P- substrate must be connected to the most negative voltage, ground.
- ❑ This assumes that all other nets are at a voltage between 0V and VDD.


CMOS INVERTER :

 


CMOS NAND (Circuit Diagram)

 


CMOS NAND:

 

 


Darshana Sankhe

CMOS NAND (Stick Diagram)

 


CMOS NOR (Circuit Diagram)

 

NOR gate in CMOS

CMOS NOR (Stick Diagram)

 

Design Rules: CMOS

- Line size and spacing:
 - **metal1:**
 - Minimum width= 3λ , Minimum Spacing= 3λ
 - **metal2:**
 - Minimum width= 3λ , Minimum Spacing= 4λ
 - **poly:**
 - Minimum width= 2λ , Minimum Spacing= 2λ
 - **ndiff/pdiff:**
 - Minimum width= 3λ , Minimum Spacing= 3λ ,


 - **wells:**
 - minimum width= 6λ ,
minimum n-well/p-well space = 6λ (They are at same potential)
= 9λ (They are at different potential)

Design Rules: CMOS


- Transistors:
 - Min width = 3λ
 - Min length = 2λ
 - Min poly overhang = 2λ

- Contacts (Vias)
 - Cut size: exactly $2\lambda \times 2\lambda$
 - Cut separation: minimum 2λ
 - Overlap: min 1λ in all directions



CMOS Inverter:

 

Darshana Sankhe



 


CMOS NAND

  

Scale 1cm = 2λ


CMOS NOR :

   


Darshana Sankhe

CMOS INVERTER

 (This layout does not have n-well and contacts for n-well and substrate)




CMOS NAND

 


CMOS NAND

 This layout does not have n-well and contacts for n-well and substrate)




Darshana Sankhe

CMOS NOR (Circuit Diagram)

 

CMOS NOR

 This layout does not have n-well and contacts for n-well and substrate)



Design of NMOS/CMOS Circuits:


- **PDN** – The Function to be implemented, must be expressed in a inverted form.

- $F = \overline{(A + BC)} D$

- $F = (AB + C) (D + E)$

- $\overline{F} = A + B + CD$

$$F' = A + B + CD$$

 

Thank you

Darshana Sankhe