

# # MOSFET Characteristics and Parameters:-

MOSFET → Unipolar device

Drain o/p current is controlled by an Electric field that depends on a gate control ( $V_{gs}$ ) voltages.

Voltage controlled non-linear device.

## MOSFETS

Enhancement type MOSFET

Depletion-type MOSFET

n-channel MOSFET  
"NMOS"-E

pchannel MOSFET  
"PMOS"-E

"NMOS"-D

"PMOS"-D

• MOSFET's are currently used for VLSI circuits such as microprocessors and memory chips.

INDERJIT SINGH

• MOSFET differs from the JFET in that (it has  $SiO_2$  gate of the MOSFET is insulated from the channel by a  $SiO_2$  layer), whereas in JFET, gate and channel are separated by a pn junction.

• It is the insulating layer of  $SiO_2$  in the MOSFET construction that accounts for the very desirable high  $\Delta p$  resistance of the device.

Note:  $R_i$  of MOSFET is higher than even JFET  $I_G \approx 0A$  for dc-biased configurations.

### 1] Depletion-mode MOSFET:-

↳ It has a physical channel between Drain and Source.

a] NMOS-D type:

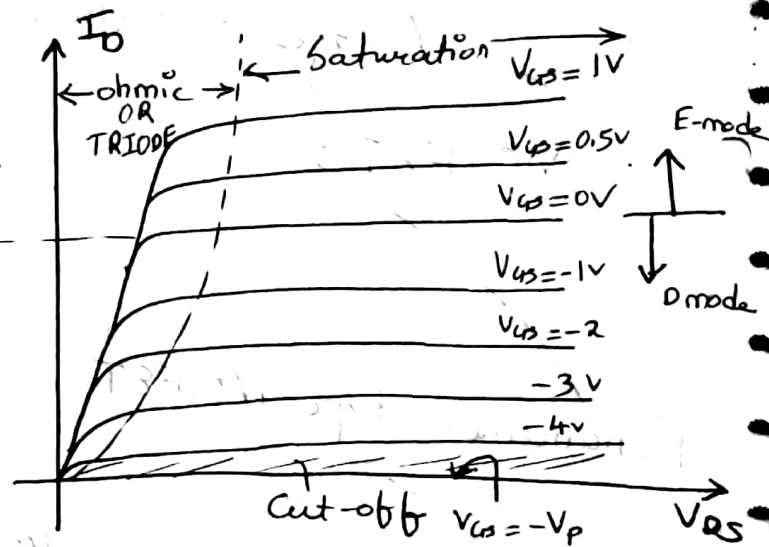
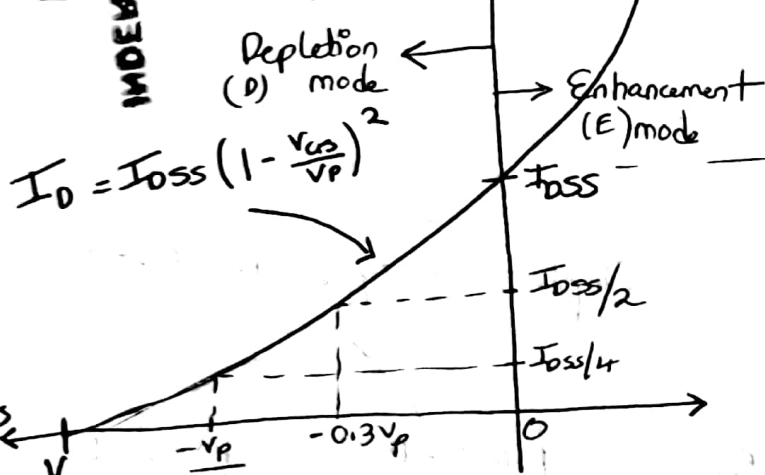


Fig 1: Transfer and drain characteristics of an NMOS-D type.


For  $V_{GS} = 0 \Rightarrow I_D = I_{DSS}$

For  $V_{GS} = -V_p \Rightarrow I_D = 0$

$V_p \rightarrow$  Pinch-off voltage (similar to one in JFET)

Primary difference between JFET and D-MOSFET is the fact that depletion-type MOSFETs permits Q-points with possible values of  $V_{GS}$  and levels of  $I_D$  that exceed  $I_{DSS}$  (Refer fig 1 & 2)

b] pmos - Depletion type:-

 

figa: Transfer and drain characteristics of an PMOS-D type



2] Enhancement - type MOSFET:-

**INDERJIT SINGH**

- ↳ It has no physical channel
- ↳ operates only in Enhancement-mode and has no depletion mode.

A channel is induced in an E-MOSFET by the application of a gate-to source voltage  $V_{GS} > V_T$ .

a) NMOS-Enhancement type:-

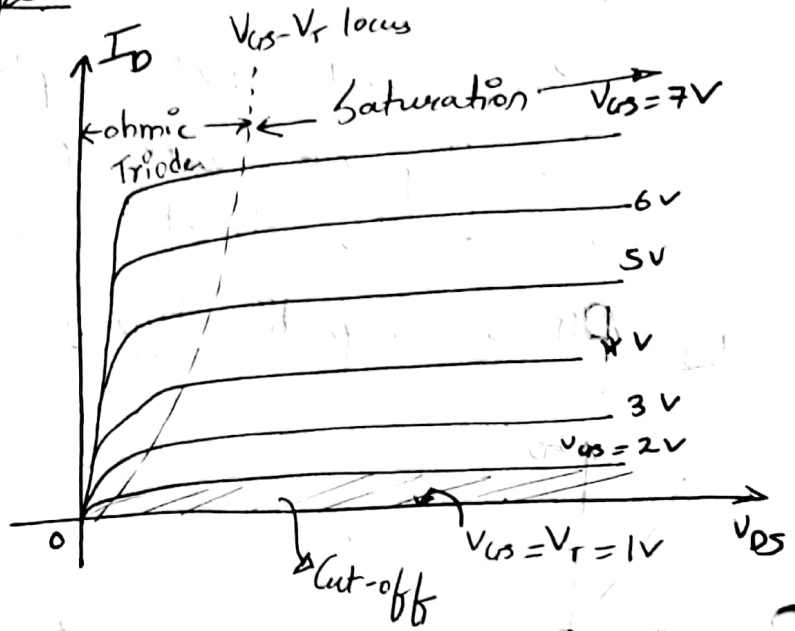 

Threshold voltage:

fig 3: Transfer and Drain characteristics of NMOS-E.

$$I_D = K_n (V_{GS} - V_{GS(th)})^2$$

$$V_{GS(th)} \approx V_t$$

$V_{GS} > V_T$

$K_n$  unit is  $\boxed{mA/V^2}$

For NMOS-E type, for values of  $V_{GS}$  less than  $V_T$ ,  $I_D \approx 0mA$ .

b) PMOS-Enhancement type:-


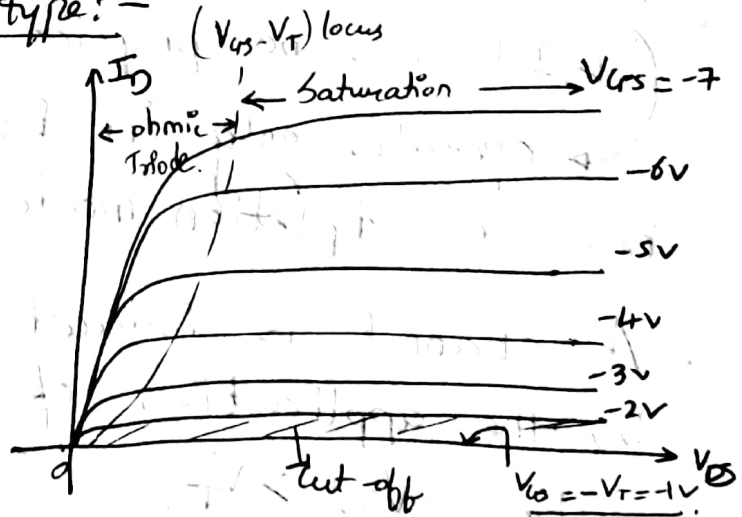
 


fig 4: Transfer and Drain characteristics of PMOS-E


In Enhancement type MOSFETs, there is no drain current when  $V_{GS} = 0$ .

∴ E-MOSFET does not have a  $I_{DSS}$  parameter, as do the JFET and D-MOSFET.

 \*  $I_D = K_n (V_{GS} - V_T)^2$  --- → Transfer curve expression for E-MOSFET.



NMOS-D (Symbolic Representations) PMOS-D

 

NMOS-E (Symbolic Representations) PMOS-E

INDERJIT SINGH

## MOSFET DC Biasing

01  
23/11/19

Biasing  $\rightarrow$  means applying appropriate voltages & current to the device such that it works in the region of operation of interest.

### • Depletion-MOSFET Biasing :-


- Biasing circuits for D-MOSFET are similar to the circuits used for JFET biasing.
- The primary difference between the two is that D-MOSFETs can be operated with either +ve or -ve value of  $V_{GS}$

### • D-MOSFET biasing types :-

- Zero-bias
- Self-bias
- Voltage-divider bias

a) Zero-bias circuit (NMOS-D type) :

02

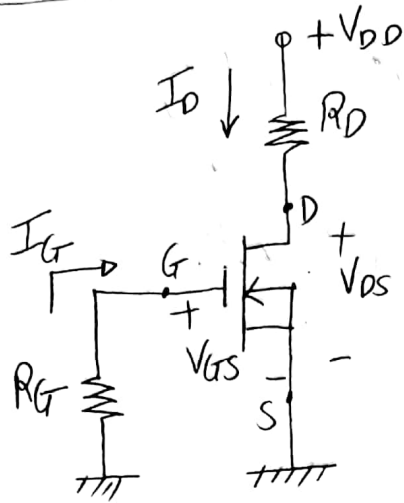

- Simplest biasing circuit  
which makes  $V_{GS} = 0$

→ KVL to G-S loop,

$$-I_G R_G - V_{GS} = 0$$

But for MOSFET,  $I_G \approx 0$

ie  $V_{GS} = 0$

(Because of presence of oxide layer bet<sup>n</sup> Gate & substrate)

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

For  $V_{GS} = 0$  ;  $I_D = I_{DSS}$

→ KVL to D-S loop,


$$V_{DD} - I_D R_D - V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

To find Q-point graphically :-

load line is  $V_{GS} = 0$

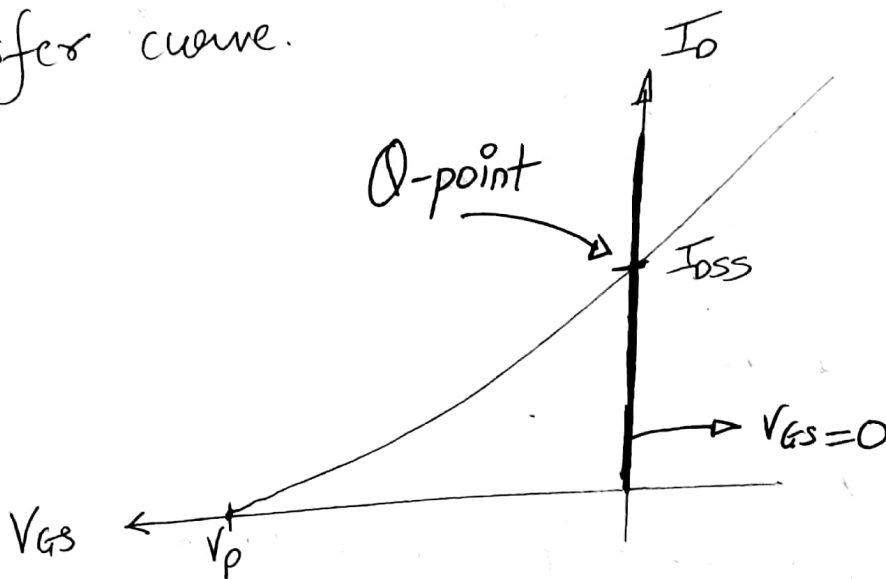→ Zero-bias circuit will bias NMOS-D at a point lying on the vertical axis of the transfer curve.



Q-point

$$\equiv (V_{GSQ}, I_{DQ})$$


$$\equiv (0, I_{DSS})$$

Note:- Zero-biasing is only possible for depletion-type MOSFETs.



Numerical Q1:-

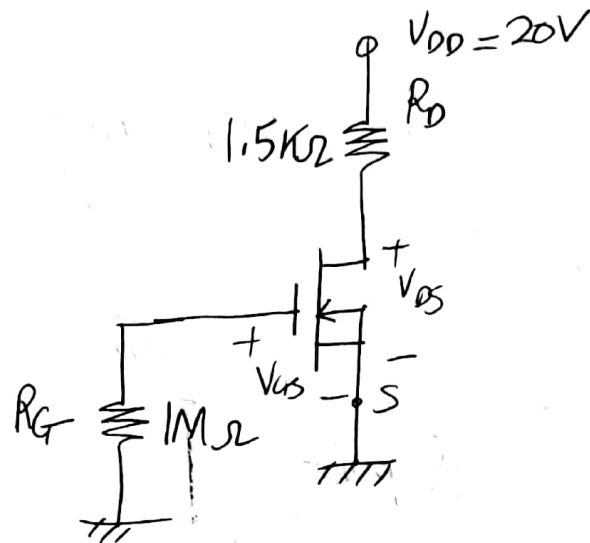Find the Q-point and  $V_{DS}$  for circuit below



$$I_{DSS} = 10 \text{ mA}$$

$$V_P = -4 \text{ V}$$

Sol<sup>n</sup>:-  $V_{GS} = V_G - V_S$

From ckt,  $V_S = 0$

Also,  $V_G = I_G R_G$  ( $I_G = 0$  for MOSFET)

$$V_G = 0$$

i.e.  $V_{GSQ} = 0$

$$\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = I_{DSS} (1 - 0)^2 = I_{DSS}$$

i.e.  $I_{DQ} = I_{DSS} = 10 \text{ mA}$


Q point  $\equiv (V_{GSQ}, I_{DQ}) \equiv (0, 10 \text{ mA})$

$$\rightarrow V_{DS} = V_{DD} - I_D R_D$$

$$= 20 - 10 \text{ mA} \times 1.5 \text{ k}\Omega$$

$V_{DS} = 5 \text{ V}$

b) Self-bias circuit (NMOS-D type) :-

 

$$\boxed{I_D \approx I_S} \text{ for MOSFET}$$

- This biasing ckt gives -ve value of  $V_{GS}$

→ KVL to G-S loop,

$$-I_G R_G - V_{GS} - I_D R_S = 0$$

For MOSFET,  $\underline{I_G = 0}$

$$\boxed{V_{GS} = -I_D R_S}$$

$$\boxed{I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2}$$

→ KVL to D-S loop,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$\boxed{V_{DS} = V_{DD} - I_D (R_D + R_S)}$$

• To determine the Q point graphically :-

For self bias, the eq<sup>n</sup> of load line is

$$\boxed{V_{GS} = -I_D R_S} \quad \text{--- (1)}$$


→ Draw transfer curve for NMOS-D type

a) In eq<sup>n</sup> (1), put  $I_D = 0 \rightarrow V_{GS} = 0$

1<sup>st</sup> point : (0, 0)

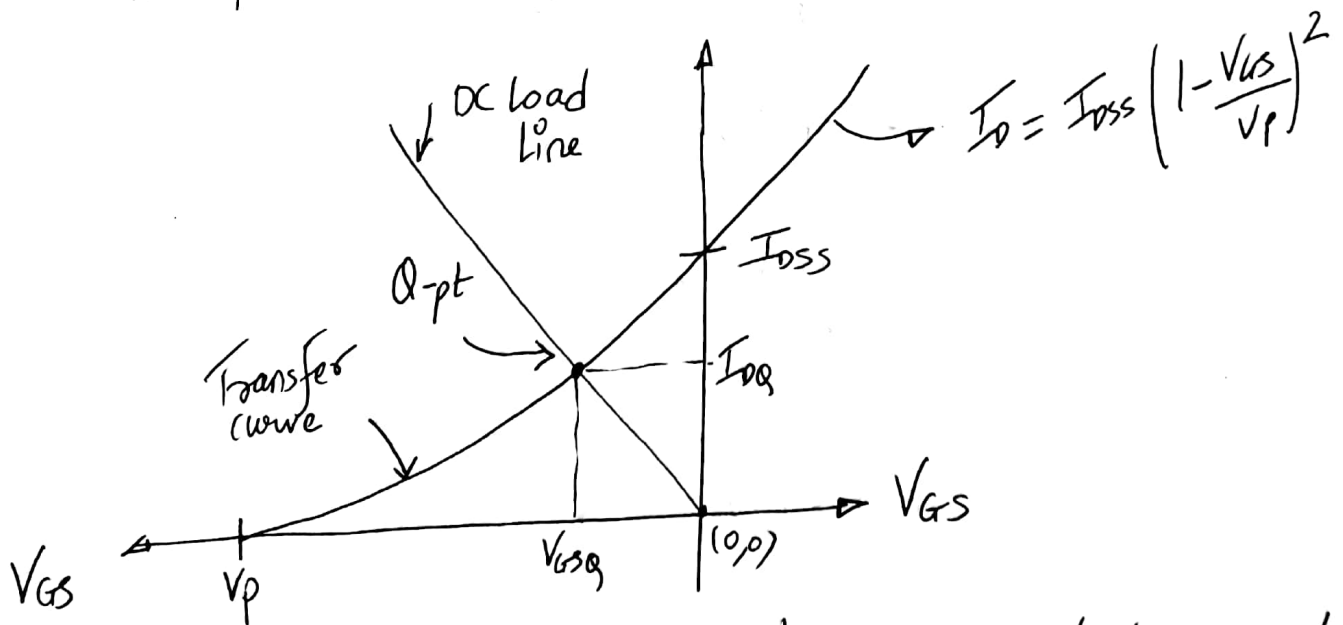
b) In eq<sup>n</sup> (1), put  $I_D = \frac{I_{DSS}}{4} \rightarrow V_{GS} = -\frac{I_{DSS}}{4} \times R_S$

2<sup>nd</sup> point :  $(-\frac{I_{DSS}}{4} \times R_S, \frac{I_{DSS}}{4})$




→ Q pt will be the intersection of DC load line and transfer curve

c) Voltage divider bias (NMOS-D) :

 

•  $R_1$  &  $R_2$  act as voltage divider network

 → Apply thevenin's equivalent to gate, we get



$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$R_G = R_1 \parallel R_2$$

KVL to G-S loop,

$$V_G - I_G R_G - V_{GS} - I_D R_S = 0$$

But  $I_G = 0$  for MOSFET

$$\text{ie } V_{GS} = V_G - I_D R_S$$

$$\text{Also, } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

KVL to D-S loop,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

To determine the Q-point graphically:-

$$V_{GS} = V_G - I_D R_S \quad \text{----- load line eq}^n \text{ for voltage-dividers bias}$$


1) Put  $V_{DS} = 0 \rightarrow I_D = \frac{V_G}{R_S}$

1st point  $\equiv (0, \frac{V_G}{R_S})$

2) Put  $I_D = 0 \rightarrow V_{GS} = V_G$

2nd point  $\equiv (V_G, 0)$

- Draw transfer curve for NMOS-D device

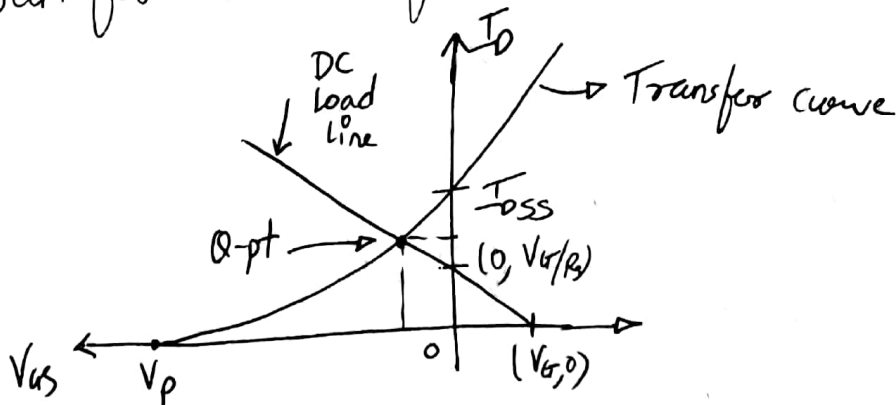


→ Q-point will be the intersection of DC load line and transfer curve
 
## Numerical 02

09

Find  $V_G$ ,  $V_{GS}$ ,  $I_D$  and  $V_{DS}$  for circuit below:-



$$I_{DSS} = 6\text{mA}$$
$$V_p = -3\text{V}$$

• Above ckt is NMOS-D type voltage-divider bias

Solution:

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \underline{1.5\text{V}}$$

$$V_S = I_D R_S$$

$$\rightarrow V_{GS} = V_G - V_S = V_G - I_D(750)$$

$$\text{i.e. } V_{GS} = 1.5 - I_D(750) \quad \text{--- (1)}$$

Now, we assume that given NMOS-D device is working in saturation region.

$$\therefore I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = 6\text{mA} \left(1 + \frac{V_{GS}}{3}\right)^2 \quad \text{--- (2)}$$

Put (2) in (1), we get

$$V_{GS} = 1.5 - 750 \times 6\text{mA} \left(1 + \frac{V_{GS}}{3}\right)^2$$

$$V_{GS} = 1.5 - 4.5 \left( 1 + \frac{2}{3} V_{GS} + \frac{V_{GS}^2}{9} \right)$$

10

$$\text{ie } V_{GS} = 1.5 - 4.5 - 3V_{GS} - 0.5V_{GS}^2$$

$$\rightarrow 0.5V_{GS}^2 + 4V_{GS} - 3 = 0$$

Solving, we get

$$V_{GS} = -0.8377V \quad \text{or} \quad -7.16V$$

(As  $V_{GS} > V_P$ )

$$\rightarrow \boxed{V_{GS} = -0.8377V}$$

$$\rightarrow I_D = 6mA \left( 1 - \frac{(-0.8377)}{(-3)} \right)^2 = 3.11mA$$

$$\text{ie } \boxed{I_D = 3.11mA}$$

KVL to D-S loop,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$\text{ie } V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$= 18 - 3.11 \times 10^{-3} (1.8K + 750)$$

$$\boxed{V_{DS} = 10.07V}$$

## • Enhancement-type NMOS Biasing :-

11

- E-MOSFET (n-channel) requires  $V_{GS}$  value greater than threshold value ( $V_T$ )

- So, a self-bias cannot be used since it makes  $V_{GS}$  negative.

- Also, a zero-bias cannot be used since it makes  $V_{GS}$  zero.

- Types of E-NMOS biasing


a) Drain feedback bias

b) Voltage-divider bias

- In NMOS-E type biasing,  $V_{GS}$  can only take +ve values (as  $V_{GS} > V_T$ )



a) Drain-feedback biasing (NMOS-E)

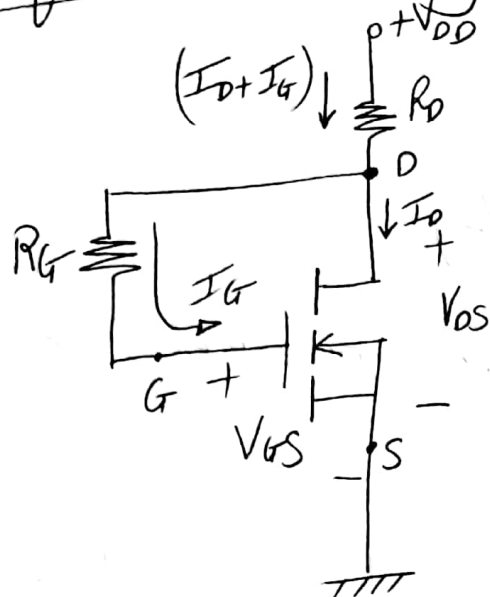

KVL to G-S loop,

$$V_{DD} - (I_D + I_G)R_D - I_G R_G - V_{GS} = 0$$

For MOSFET,  $I_G \approx 0$

ie  $V_{DD} - I_D R_D - V_{GS} = 0$

$$\boxed{V_{GS} = V_{DD} - I_D R_D}$$

For E-type NMOS,

$$\boxed{I_D = K_n (V_{GS} - V_T)^2}$$

→ KVL to D-S loop,

$$V_{DD} - I_D R_D - V_{DS} = 0$$

ie  $\boxed{V_{DS} = V_{DD} - I_D R_D}$

For Drain-feedback bias, we can write

$$V_{DS} = V_{GS} = V_{DD} - I_D R_D$$

To determine Q-point graphically.

$$V_{GS} = V_{DD} - I_D R_D \text{ --- load line eq}^n$$


a) Put  $V_{GS} = 0 \rightarrow I_D = \frac{V_{DD}}{R_D}$

1st point  $\equiv (0, \frac{V_{DD}}{R_D})$

b) Put  $I_D = 0 \rightarrow V_{GS} = V_{DD}$

2nd point  $\equiv (V_{DD}, 0)$

→ Draw transfer curve of NMOS-E :

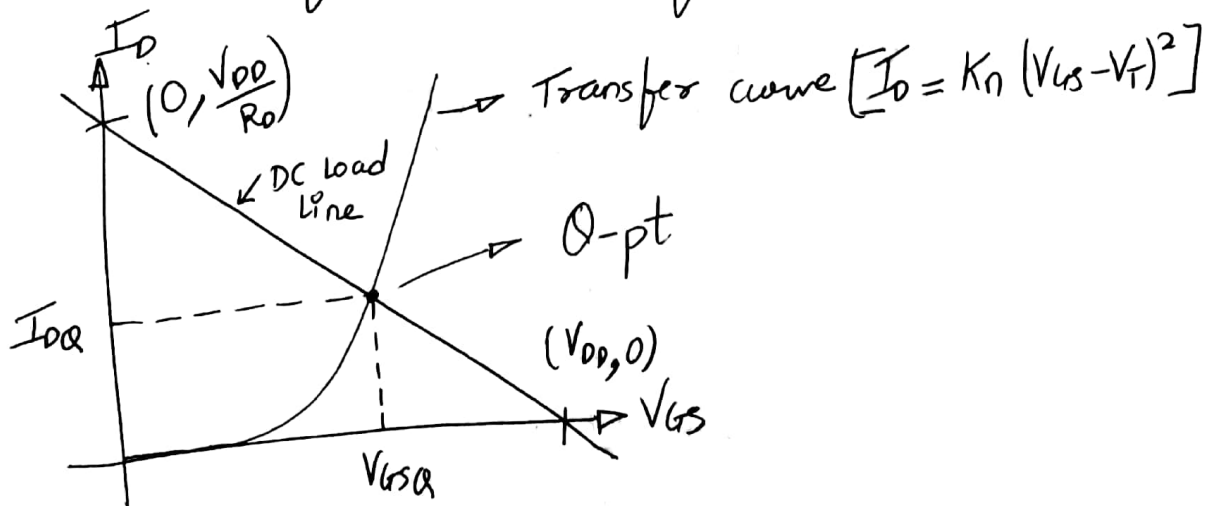


→ Intersection of DC load line & transfer curve gives us the Q-point

Note: Drain feedback bias provides a stable Q-point, because it tends to compensate for any changes in device parameter variations.

Numerical 03:

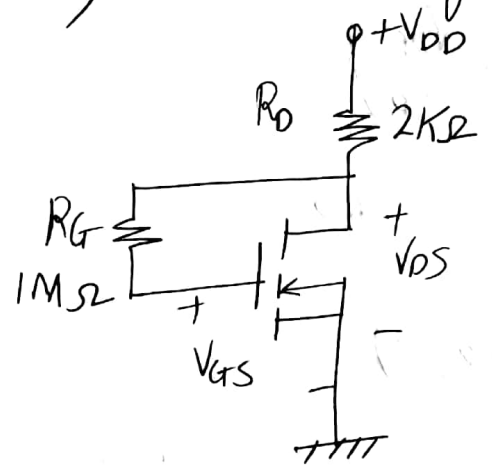Find  $V_{GS}$ ,  $I_D$  &  $V_{DS}$  for the circuit below



$$I_{D(on)} = 6\text{mA}$$

$$V_{GS(on)} = 8\text{V}$$

$$V_{GS(th)} = 3\text{V}$$

Sol<sup>n</sup>:-

$$1) K_n = \frac{I_{D(on)}}{[V_{GS(on)} - V_{GS(th)}]^2}$$

$$= \frac{6\text{mA}}{(8-3)^2}$$

$$K_n = 0.24 \frac{\text{mA}}{\text{V}^2}$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$\text{i.e. } V_{GS} = 12 - I_D (2000) \quad \text{--- (1)}$$

Assume the given NMOS-E is in saturation region,

$$I_D = K_n (V_{GS} - V_{GS(th)})^2$$

$$\text{i.e. } I_D = 0.24 \times 10^{-3} (V_{GS} - 3)^2 \quad \text{--- (2)}$$

Put (2) in (1), we get

$$\rightarrow V_{GS} = 12 - 0.48 (V_{GS} - 3)^2$$

$$V_{GS} = 12 - 0.48 (V_{GS}^2 - 6V_{GS} + 9)$$

$$\text{i.e. } V_{GS} = 12 - 0.48V_{GS}^2 + 2.88V_{GS} - 4.32$$

$$\text{i.e. } 0.48V_{GS}^2 - 1.88V_{GS} - 7.68 = 0$$

$$V_{GS} = 6.41 \text{ V. or } V_{GS} = -2.49 \text{ V}$$

(✓)
(X)

( $V_{GS} > V_{GS(th)}$ )


$$\text{i.e. } \boxed{V_{GS} = 6.41 \text{ V}}$$

$$\text{i.e. } \boxed{V_{DS} = V_{GS} = 6.41 \text{ V}}$$


$$I_D = K_n (V_{GS} - 3)^2 = 0.24 \times 10^{-3} (6.41 - 3)^2$$

$$\boxed{I_D = 2.79 \text{ mA}}$$

b) Voltage-divider bias (NMOS-E) :-

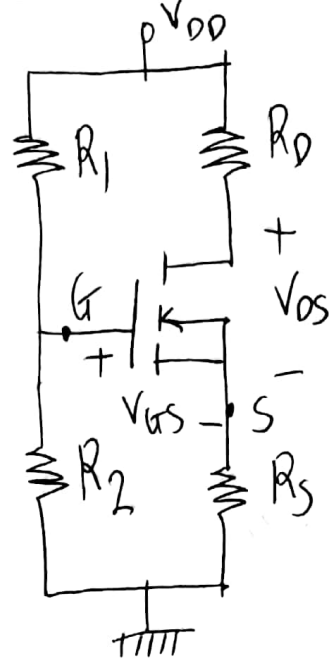

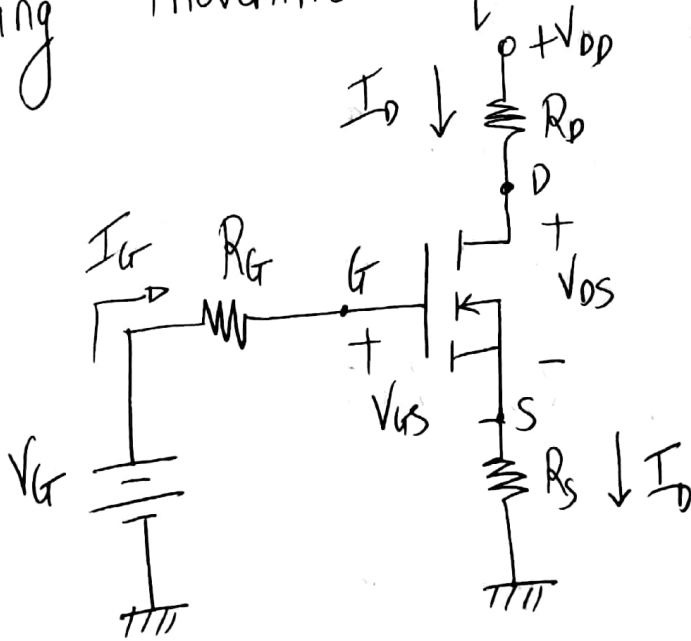Applying thevenin's equivalent at the gate terminal,



$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$R_G = R_1 \parallel R_2$$

Apply KVL to G-S loop,

$$V_G - I_G R_G - V_{GS} - I_D R_S = 0$$

For MOSFET,  $I_G = 0$

$$V_{GS} = V_G - I_D R_S$$

$$I_D = K_n (V_{GS} - V_T)^2$$

KVL to D-S loop,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

• To determine Q-point graphically :

$$V_{GS} = V_G - I_D R_S \quad \text{--- Load Line eq}^n$$

① Put  $V_{GS} = 0 \rightarrow I_D = \frac{V_{DD}}{R_S}$


1<sup>st</sup> point  $\equiv (0, \frac{V_{DD}}{R_S})$

② Put  $I_D = 0 \rightarrow V_{GS} = V_G$

2<sup>nd</sup> point  $\equiv (V_G, 0)$

Now, we draw the transfer curve of NMOS-E type device using,

$$I_D = K_n (V_{GS} - V_T)^2$$

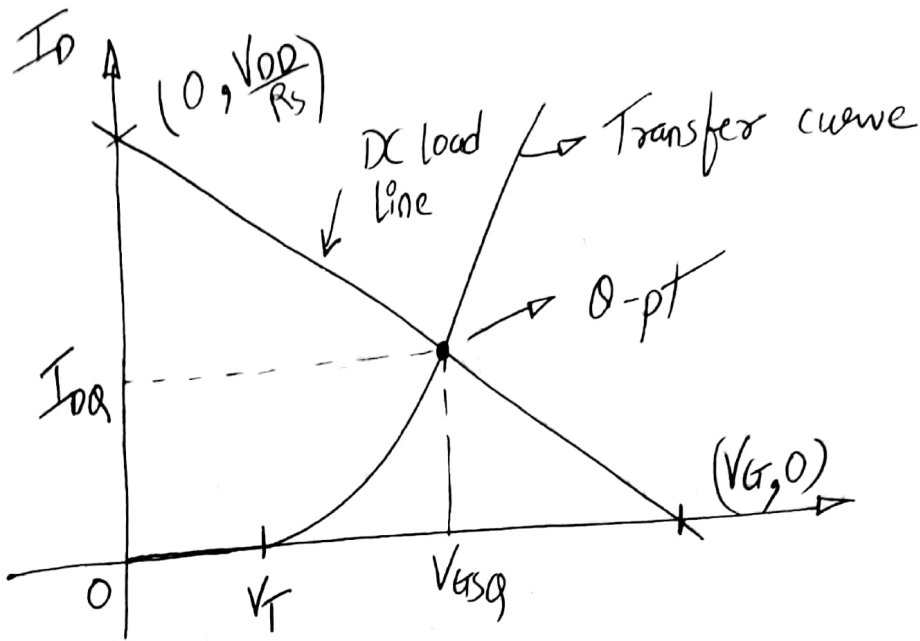


→ Q-point is the intersection of DC load line & transfer curve

Numerical 04:

Find  $V_G$ ,  $I_D$ ,  $V_{GS}$  and  $V_{DS}$  for circuit shown below

 Also, determine region of operation of given device



Given data

$$V_{GS(th)} = 5V$$

$$V_{GS(on)} = 10V$$

$$I_D(on) = 3mA$$

Sol<sup>n</sup>:

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{18M}{18M + 22M} \times 40 = \underline{18V}$$

For E-NMOS transistor,

19

$$K_n = \frac{I_D(\text{on})}{[V_{GS(\text{on})} - V_{GS(\text{th})}]^2}$$
$$= \frac{3\text{mA}}{[10 - 5]^2}$$

$$K_n = 0.12 \frac{\text{mA}}{\text{V}^2}$$

$$\rightarrow V_{GS} = V_G - V_S = V_G - I_D R_S$$

$$V_{GS} = 18 - I_D (820) \quad \text{--- (1)}$$

Assuming that given NMOS-E transistor is working in saturation region,

$$I_D = K_n (V_{GS} - V_{GS(\text{th})})^2$$

$$I_D = 0.12 \times 10^{-3} (V_{GS} - 5)^2 \quad \text{--- (2)}$$

Put (2) in (1), we get

$$V_{GS} = 18 - 820 \times 0.12 \times 10^{-3} (V_{GS} - 5)^2$$

$$V_{GS} = 18 - 0.0984 (V_{GS}^2 - 10V_{GS} + 25)$$



$$V_{GS} = 18 - 0.0984 V_{GS}^2 + 0.984 V_{GS} - 2.46$$

$$\text{i.e. } 0.0984 V_{GS}^2 + 0.016 V_{GS} - 15.54 = 0$$

Solving, we get

$$V_{GS} = 12.48V \quad \text{or} \quad -12.64V$$

(as  $V_{GS} < V_{GS(th)}$ )

$$\therefore \boxed{V_{GS} = 12.48V}$$

$$\text{i.e. } I_D = K_n (V_{GS} - 5)^2$$

$$= 0.12 \times 10^{-3} (12.48 - 5)^2$$

$$\boxed{I_D = 6.72 \text{ mA}}$$

$$\text{Now, } V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$= 40 - 6.72 \text{ mA} (3K + 820)$$

$$\boxed{V_{DS} = 14.32V}$$

$$V_{GS(th)} = V_T$$

Since,  $[V_{GS} > V_{GS(th)}]$  &  $V_{DS} > V_{GS} - V_T$   
 $V_{DS} > (12.48 - 5)$

$\therefore$  Given NMOS-E device is working in the saturation region.

# Design of MOSFET biasing circuits

21


## Design 01

Design a NMOS-E DC Biasing circuit to give  
 $I_D = 0.25 \text{ mA}$ ,  $V_{DSQ} = 4 \text{ V}$ ,  $V_{R_S} = 1 \text{ V}$

MOSFET parameters:  $K_n' = 80 \mu\text{A}/\text{V}^2$ ,  $\frac{W}{L} = 4$ ,  $V_{TN} = 1.2 \text{ V}$

The current in the bias resistors ( $R_1$  &  $R_2$ ) should be approximately  $20 \mu\text{A}$

 $V_{DD}$  and  $V_{SS} = +5 \text{ V}$  and  $-5 \text{ V}$



Sol<sup>n</sup>:  $V_{R_S} = R_S I_{DQ}$

$$R_S = \frac{V_{R_S}}{I_{DQ}} = \frac{1 \text{ V}}{0.25 \text{ mA}} = 4 \text{ K}\Omega$$

Select  $R_S = 3.9 \text{ K}\Omega$  (std),  $\frac{1}{4} \text{ W}$  (L.S.V)

KVL to D-S loop,

22

$$V_{DD} - I_{DQ} R_D - V_{DS} - I_{DQ} R_S + V_{SS} = 0$$

$$5 - I_{DQ} (R_D + R_S) - 4 + 5 = 0$$

$$\underline{I_{DQ} = 0.25 \text{ mA}} \quad \text{--- given}$$

$$\& \underline{R_S = 3.9 \text{ k}\Omega}$$

$$R_D = 20.1 \text{ k}\Omega$$

Select  $R_D = 22 \text{ k}\Omega, \frac{1}{4} \text{ W (std)}$  (H.S.V)

$$I_D = K_n (V_{GS} - V_T)^2$$

$$I_D = \frac{K_n'}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$0.25 \text{ mA} = \frac{80 \mu \times 4^2}{2} (V_{GS} - 1.2)^2$$

$$1.5625 = (V_{GS} - 1.2)^2$$

$$\boxed{V_{GS} = 2.45 \text{ V}}$$

Since, current through bias resistors is  $20\mu A$  23

$$R_1 + R_2 = \frac{V_{DD} + V_{SS}}{I_{(R_1+R_2)}} = \frac{5+5}{20\mu A} = \frac{500K\Omega}{20\mu A}$$

$$\bullet V_G = \left[ \frac{R_2}{R_1 + R_2} (5+5) \right] - 5$$

$$\bullet V_G = \frac{R_2 \times 10}{500K} - 5$$

$$\bullet V_S = I_D R_S - 5$$

$$\rightarrow V_{GS} = V_G - V_S$$

$$2.45 = \left[ \frac{R_2 \times 10}{500K} - 5 \right] - \left[ \underset{\substack{\downarrow \\ 0.25mA}}{I_D R_S} - 5 \right]$$

$\nearrow 3.9K\Omega$

$$2.45 = \frac{R_2}{50K} - \cancel{5} - 0.975 + \cancel{5}$$

$$3.425 = \frac{R_2}{50K\Omega}$$

$$\Rightarrow R_2 = 171.25K\Omega$$

Select  $R_2 = 150K\Omega$  (std),  $1/4W$   
L.S.V


$$R_1 = 328.75K\Omega \quad (\because R_1 + R_2 = 500K)$$

Select  $R_1 = 330K\Omega$  (std),  $1/4W$

H.S.V

Designed circuit,

24

 

Design 02:


Design an N-channel E-type MOSFET using voltage-divider bias for following specifications:-

$$I_{DQ} = 5\text{mA}, V_{DSQ} = 5\text{V}$$

MOSFET parameters:  $K_n = 25 \frac{\text{mA}}{\text{V}^2}$ ,  $V_{TN} = 1\text{V}$

Sol<sup>n</sup>:

 1) Since we want Q point on center of DC load Line, we select  $V_{DD} = 2V_{DSQ} = 10\text{V}$



2) Assume  $V_G = 25\%$  of  $V_{DD}$

$$V_G = 0.25 \times 10 = \underline{2.5\text{V}}$$

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$2.5 = \frac{R_2}{R_1 + R_2} \times 10$$

Assume  $R_2 = 100\text{K}\Omega, \frac{1}{4}\text{W}$

$$2.5 = \frac{100\text{K}}{R_1 + 100\text{K}} \times 10$$

$$R_1 = 300\text{K}\Omega$$

Select  $R_1 = 330\text{K}\Omega, \frac{1}{4}\text{W (std)}$

$$3) I_D = K_n (V_{GS} - V_T)^2$$

$$5\text{mA} = 25\text{mA} (V_{GS} - 1)^2$$

$$V_{GS} = 1.447\text{V}$$

$$\cdot V_{GS} = V_G - I_D R_S$$

$$1.447 = 2.5 - I_D R_S$$

$$I_D R_S = 1.053$$

$$R_S = \frac{1.053}{5\text{mA}} = 210.6\Omega$$

Select  $R_S = 180\Omega, \frac{1}{4}\text{W (std)}$

4) KVL to D-S loop gives,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$I_D R_D = V_{DD} - V_{DS} - I_D R_S$$


$$R_D = \frac{V_{DD} - V_{DS} - I_D R_S}{I_D}$$

$$= \frac{10 - 5 - 5\text{mA} \times 180}{5\text{mA}}$$

$$R_D = 820\ \Omega$$

Select  $R_D = 820\ \Omega, 1/4\text{W}$

5) Designed ckt is,

 




Design 03: Design an NMOS-E drain-feedback bias circuit for following specifications

$V_{DSQ} = 5V$  ,  $I_{DQ} = 5mA$

MOSFET parameters :  $K_n = \frac{25mA}{V^2}$  ,  $V_{TN} = 1.2V$

Sol<sup>n</sup>: 1) Circuit Diagram

 

2) Since, we want the Q-point at center of DC load line

$V_{DD} = 2V_{DSQ} = 10V$

3) Selection of  $R_G$  :-

To maintain high input impedance & to minimize loading effect,  $R_G$  value has to be kept high

Select  $R_G = 1M\Omega, 1/4W$  (std)

4) For drain-to feedback bias,

$$V_{DS} = V_{DD} - I_D R_D$$

$$5 = 10 - 5\text{mA} \times R_D$$

$$R_D = \frac{5\text{V}}{5\text{mA}} = 1\text{K}\Omega$$

Select  $R_D = 1.2\text{K}\Omega$  (std),  $1/4\text{W}$

5) Designed circuit is

