

### 3.6 MULTIPLE-FEEDBACK FILTERS

*Multiple-feedback* filters utilize more than one feedback path. Unlike their *KRC* counterparts, which configure the op amp for a *finite* gain  $K$ , multiple-feedback filters exploit the full open-loop gain and are also referred to as *infinite-gain filters*. Together with *KRC* filters, they are the most popular single-op-amp realizations of the second-order responses.

#### Band-Pass Filters

In the circuit of Fig. 3.30, also called the *Delyiannis-Friend* filter, named after its inventors, the op amp acts as a differentiator with respect to  $V_1$ , so we write

$$V_o = -sR_2C_2V_1$$

Summing currents at node  $V_1$ ,

$$\frac{V_i - V_1}{R_1} + \frac{V_o - V_1}{1/sC_1} + \frac{0 - V_1}{1/sC_2} = 0$$


Eliminating  $V_1$ , letting  $s \rightarrow j\omega$ , and rearranging,

Eliminating  $V_1$ , letting  $s \rightarrow j\omega$ , and rearranging,

$$H(j\omega) = \frac{V_o}{V_i} = \frac{-j\omega R_2 C_2}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega R_1 (C_1 + C_2)}$$

To put this function in the standard form  $H(j\omega) = H_{0BP} H_{BP}(j\omega)$ , we impose  $\omega^2 R_1 R_2 C_1 C_2 = (\omega/\omega_0)^2$  to get

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad (3.70a)$$

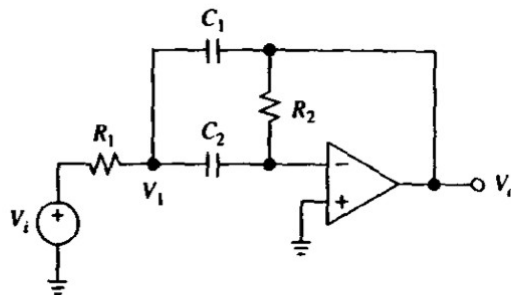

**FIGURE 3.30**  
Multiple-feedback band-pass filter.

and  $j\omega R_1(C_1 + C_2) = (j\omega/\omega_0)/Q$  to get

$$Q = \frac{\sqrt{R_2/R_1}}{\sqrt{C_1/C_2} + \sqrt{C_2/C_1}} \quad (3.70b)$$

Finally, we impose  $-j\omega R_2 C_2 = H_{0BP} \times (j\omega/\omega_0)/Q$  to get

$$H_{0BP} = \frac{-R_2/R_1}{1 + C_1/C_2} \quad (3.70c)$$

► Clearly, this filter is of the inverting type. It is customary to impose  $C_1 = C_2 = C$ , after which the above expressions simplify to

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2} C} \quad Q = 0.5\sqrt{R_2/R_1} \quad H_{0BP} = -2Q^2 \quad (3.71)$$

The corresponding design equations are

$$R_1 = 1/2\omega_0 Q C \quad R_2 = 2Q/\omega_0 C \quad (3.72)$$

Denoting resonance-gain magnitude as  $H_0 = |H_{0BP}|$  for simplicity, we observe that it increases quadratically with  $Q$ . If we want  $H_0 < 2Q^2$ , we must replace  $R_1$  with a voltage divider in the manner of Example 3.9. The design equations are then