 


Re-test 2 Solution


01
27/11/19

Q1. pnp transistor parameters:- $\beta = 100$, $V_A = \infty$




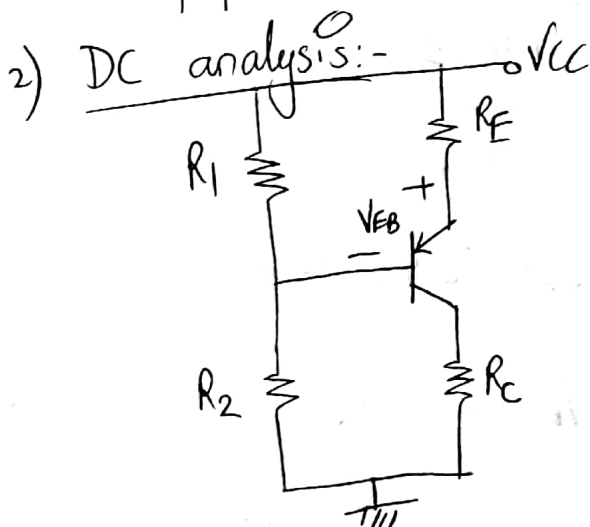- a) Design bias stable ckt such that Qpt is at center of load line
- b) Determine small-signal voltage gain of designed ckt.

Solⁿ:- A) 1) Above circuit is voltage-divider bias CE ckt with pnp transistor.



 Applying Thevenin's theorem & drawing equivalent ckt at base,



$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} \Rightarrow$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow$$

Given Q-pt is at center i.e. $V_{CEQ} = \frac{1}{2} V_{CC} = \underline{\underline{6V}}$

~~KVL to B-E loop gives,~~

~~$$V_{th} + I_B R_{th} + V_{BE} + I_E R_E - V_{CC} = 0$$~~

~~$$V_{th} + I_B R_{th} + V_{BE} + (1+\beta) I_B R_E - V_{CC} = 0$$~~

~~$$I_{BQ} = \frac{V_{CC} - V_{th} - V_{BE(on)}}{R_{th} + (1+\beta) R_E}$$~~

cannot do it
since R_1 & R_2
is unknown!

KVL to B-C loop gives

$$V_{CC} - I_E R_E - V_{CEQ} - I_C R_C = 0$$

$$V_{CC} - \left(\frac{1+\beta}{\beta}\right) R_E I_{CQ} - V_{CEQ} - I_{CQ} R_C = 0 \quad I_E = \left(\frac{1+\beta}{\beta}\right) I_C$$

$$I_{CQ} = \frac{V_{CC} - V_{CEQ}}{\left(\frac{1+\beta}{\beta}\right) R_E + R_C} = \frac{12 - 6}{\frac{101}{100} \times 1k + 2k} \Rightarrow$$

$$I_{CQ} = 1.99 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{1.99 \text{ mA}}{100} = \underline{19.93 \mu\text{A}}$$

$$; I_{EQ} = 2 \text{ mA}$$

03

→ For bias-stable ckt,

$$R_{th} = 0.1 \times (1 + \beta) R_E = 0.1 \times 101 \times 1 \text{ K}\Omega = \underline{10.1 \text{ K}\Omega}$$

(10%)

$$\rightarrow V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{R_{th}}{R_1} V_{CC} = \frac{10.1 \text{ K}\Omega \times 12}{R_1} \quad \text{--- (1)}$$

KVL to B-E loop gives,

$$V_{th} + I_{BQ} R_{th} + V_{EB(on)} + I_{EQ} R_E - V_{CC} = 0$$

$$V_{CC} = \underbrace{\frac{121.2 \text{ K}}{R_1}}_{V_{th}} + I_{BQ} R_{th} + V_{EB(on)} + 2 \text{ mA} \times R_E$$

$$12 = \frac{121.2 \text{ K}}{R_1} + 19.93 \mu\text{A} \times 10.1 \text{ K}\Omega + 0.7 + 2 \text{ mA} \times 1 \text{ K}\Omega$$

$$R_1 = 13.3 \text{ K}\Omega$$


Select $R_1 = 12 \text{ K}\Omega$ (std), $\frac{1}{4} \text{ W}$ } L.S.V

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = 10.1K\Omega$$

$$10.1K\Omega = \frac{13.3K \times R_2}{R_2 + 13.3K} \Rightarrow R_2 = \underline{41.98K\Omega}$$

Select $R_2 = 42K\Omega_{(std)}, \frac{1}{4}W$

Bias-stable ckt is

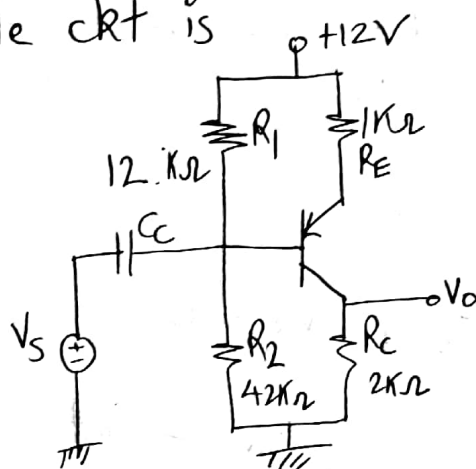

$$B) \quad r_{ii} = \frac{\beta V_T}{I_{CQ}} = \frac{V_T}{I_{BQ}} = \frac{26mV}{19.93\mu A} = \underline{1.3K\Omega}$$


$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.99mA}{26mV} = \underline{76.54 \frac{mA}{V}}$$

$$A_v \approx - \frac{R_c}{\frac{1}{g_m} + R_E} \approx - \frac{2K\Omega}{\frac{1}{76.54m} + 1K\Omega} \quad \text{--- Regenerated CE Stage}$$

$$A_v \approx - \frac{2K\Omega}{13.065 + 1K\Omega} \approx - \underline{1.97} \quad \text{--- small-sig voltage gain}$$

Q₁ Given: pnp transistor parameters $\beta = 100$,
 $V_{EB(on)} = 0.7V$, $V_A = \infty$


27/11/19

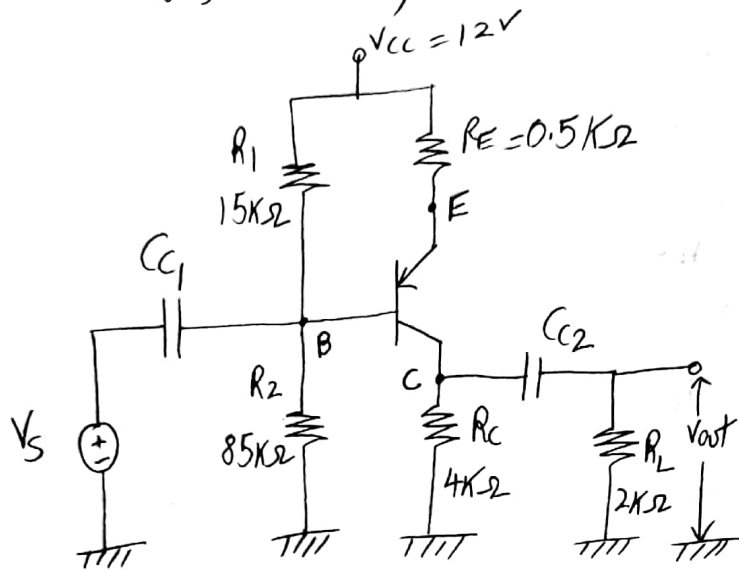

To find a) I_{CQ} , V_{ECQ}
 b) Small-signal voltage gain

Solⁿ:] DC Analysis :-

 Notes- DC circuit of pnp transistor is same as that of npn device, expect that all current directions and voltage polarities are reversed.




$$R_{Th} = R_1 \parallel R_2 = 15K \parallel 85K$$

$$R_{Th} = \underline{12.75 K\Omega}$$

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{85K \times 12}{85K + 15K} = \underline{10.2V}$$

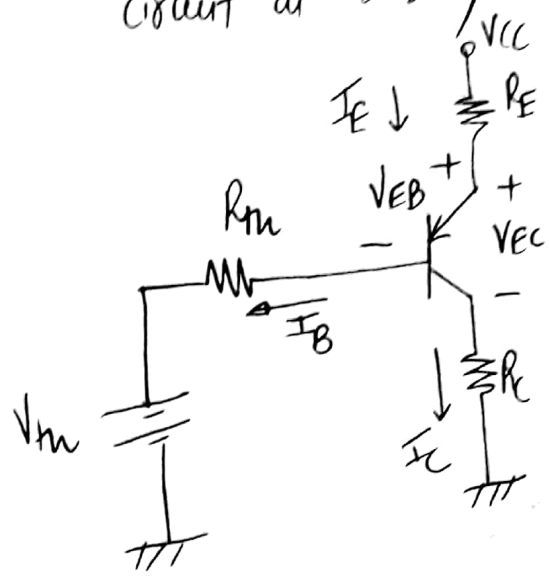Applying Thevenin's theorem and drawing equivalent circuit at base, we get



KVL to B-E loop gives,

$$V_{th} + I_B R_{th} - V_{EB} + I_E R_E - V_{CC} = 0$$

$$V_{th} + I_B R_{th} - V_{EB} + (1+\beta) I_B R_E - V_{CC} = 0$$

$$I_{BQ} = \frac{V_{CC} - V_{th} - V_{EB}}{R_{th} + (1+\beta) R_E}$$

$$= \frac{12 - 10.2 - 0.7}{12.75 + 101 \times 0.5K}$$

$$I_{BQ} = 17.39 \mu A$$

$$\therefore I_{CQ} = \beta I_{BQ} = 100 \times 17.39 \mu A$$

$$I_{CQ} = 1.74 \text{ mA}$$

KVL to (-E) loop gives,

$$V_{CC} - I_E R_E - V_{EC} - I_C R_C = 0$$

$$I_E = I_B + I_C = 1.757 \text{ mA}$$

$$V_{EC} = V_{CC} - I_E R_E - I_C R_C$$

$$= 12 - 1.757 \text{ mA} \times 0.5 \text{ K} - 1.74 \text{ mA} \times 4 \text{ K} \Omega$$

$$V_{EC} = 4.16 \text{ V}$$

2) Small-signal parameters:-

Note:- For pnp bjt, all small-sig parameters (g_m, r_{ii}, r_o) formula remains same.


$$a) r_{ii} = \frac{V_T}{I_{BQ}} = \frac{26 \text{ mV}}{17.39 \mu\text{A}} = 1.495 \text{ K} \Omega$$

$$b) g_m = \frac{I_{CQ}}{V_T} = \frac{1.74 \text{ mA}}{26 \text{ mV}} = 66.92 \frac{\text{mA}}{\text{V}}$$

$$c) r_o = \frac{V_A}{I_{CQ}} = \infty$$

 
3) Small-sig hybrid- π model (pnp transistor)

Hybrid- π model of pnp bjt is same as that of npn bjt; except that all current directions & voltage polarities are reversed.



Small-sig equivalent circuit :-

04

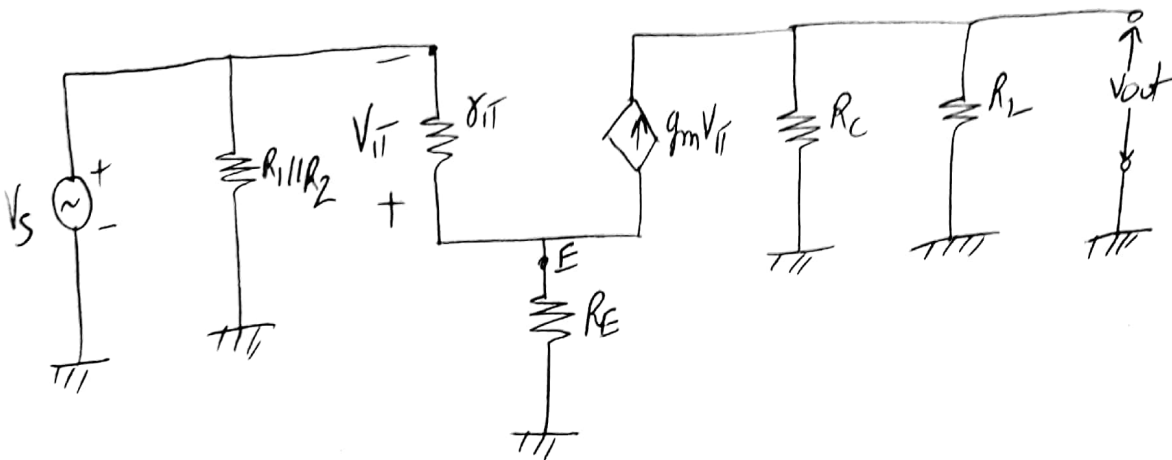

• The above equivalent ckt is similar to CE degenerated stage with npn transistor,

$$A_v \approx - \frac{(R_C \parallel R_L)}{\frac{1}{g_m} + R_E}$$

$$A_v \approx - \frac{(2K\Omega \parallel 4K\Omega)}{\frac{1}{66.92mA} + 0.5K\Omega}$$

$$\approx - \frac{1.33K\Omega}{14.94 + 0.5K}$$

$$A_v \approx - 2.58$$

→ Small-signal voltage gain

Retest 2 - BEC

Q2a) Circuit of Common source JFET amplifier ----- 1M

Small-signal equivalent ckt ----- 1M


Derivation for voltage gain ----- 3M

Q2b) Justification:

N-channel JFET is rarely operated with positive value of gate to source voltage

----- 2M

Q3)

 

$I_{DSS} = 10\text{mA}$
 $V_P = -8\text{V}$

Solⁿ → KVL to G-S loop,

$$-2 - I_G R_G - V_{GS} = 0$$

$I_G = 0$ for JFET

$$\boxed{V_{GSQ} = -2\text{V}} \text{ ----- } \boxed{2\text{M}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 10\text{mA} \left(1 - \frac{(-2)}{(-8)}\right)^2 = \underline{5.625\text{mA}} \text{ --- } \boxed{3\text{M}}$$

KVL to D-S loop, $V_{DD} - I_D R_D - V_{DS} = 0 \Rightarrow V_{DS} = V_{DD} - I_D R_D$
 $\boxed{V_{DS} = 4.75\text{V}} \text{ --- } \boxed{3\text{M}}$